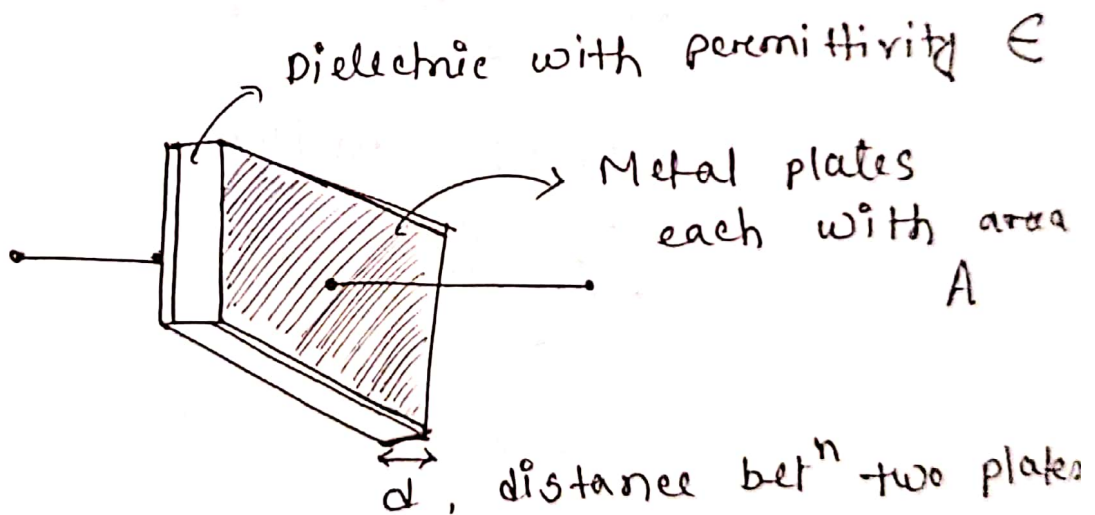


Week-8


- i) Capacitors
- ii) Inductors
- iii) Properties of both
- iv) Transient response

→ Topics
overview

Capacitors



Typical capacitor

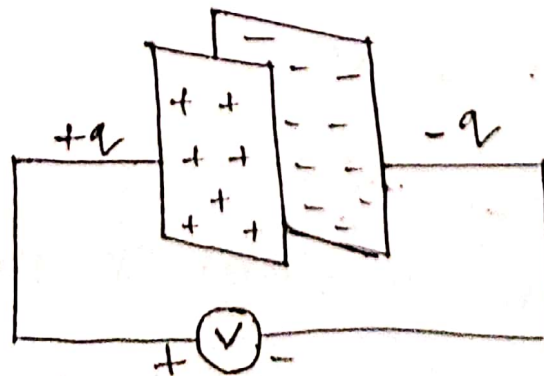

Capacitor with applied voltage, V


Properties \Rightarrow

i) Capacitor is a passive element


ii) It can store energy in its electric field.

(So, we can say it has MEMORY !!!)

Symbol \Rightarrow

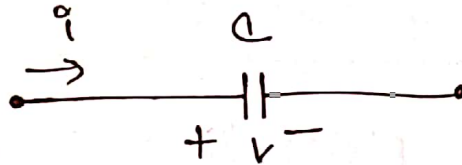

Fixed capacitor

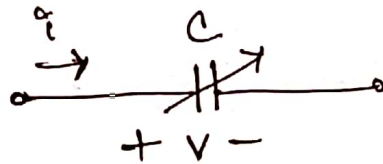

Variable capacitor

Component equation \Rightarrow

$$q \propto V$$

$$\Rightarrow q = CV$$

Here, C is the constant of proportionality called the CAPACITANCE.

Unit \rightarrow Farad (F)

So, $C = \frac{q}{V}$

$\therefore 1 \text{ Farad} = 1 \text{ coulomb/volt}$

On the contrary,

$$C = \frac{\epsilon A}{d}$$

Here, A = surface area of each plate

d = distance betⁿ two plates

ϵ = Permittivity of dielectric materials between plates.

How capacitance depends on these \Rightarrow

$$A \uparrow \quad C \uparrow$$

$$d \downarrow \quad C \uparrow$$

$$\epsilon \uparrow \quad C \uparrow$$

Current - Voltage relationship \Rightarrow

$$q = CV$$

$$\Rightarrow \frac{d(q)}{dt} = C \frac{dV}{dt}$$

$$\Rightarrow i = C \frac{dV}{dt}$$

Voltage-current relationship \Rightarrow

$$V = \frac{1}{C} \int_{-\infty}^t i \, dt$$

$$\Rightarrow V = \frac{1}{C} \int_{t_0}^t i \, dt + V(t_0)$$


$$\text{Here, } V(t_0) = \frac{q(t_0)}{C}$$





Shows capacitor voltage depends on past history.

$$\text{Power, } P = V i = C V \frac{dV}{dt}$$


$$W = P t = \frac{1}{2} C V^2 = \frac{q^2}{2C}$$

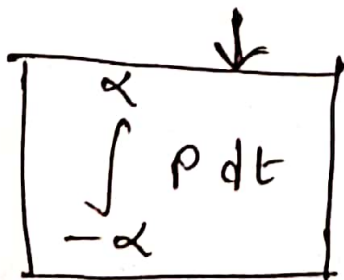
$$\int_{-\infty}^{\infty} P \, dt$$

Open circuit to DC \Rightarrow

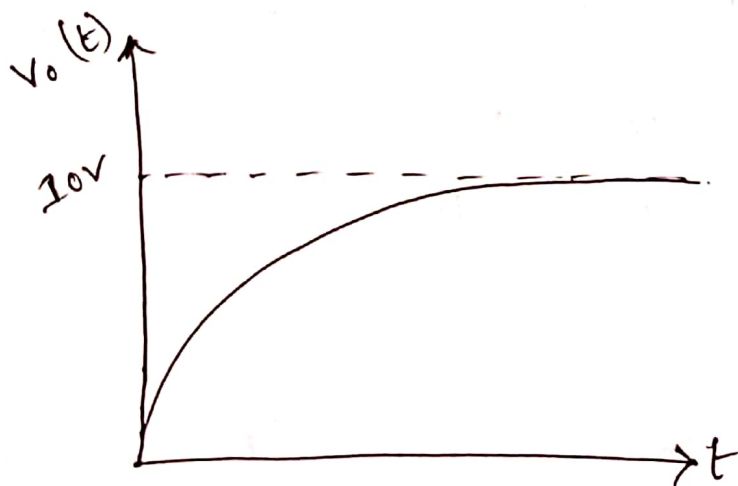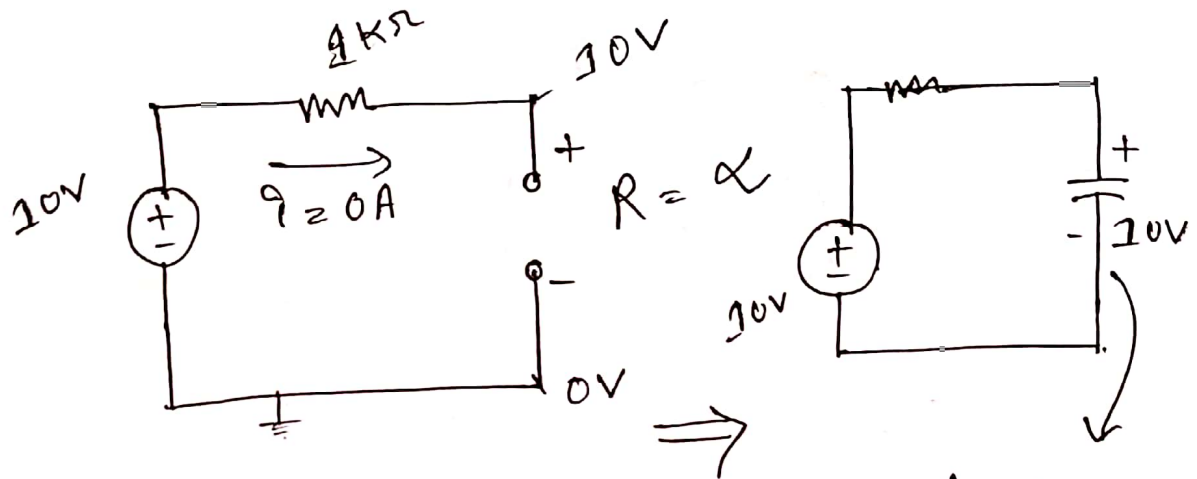

Inductors

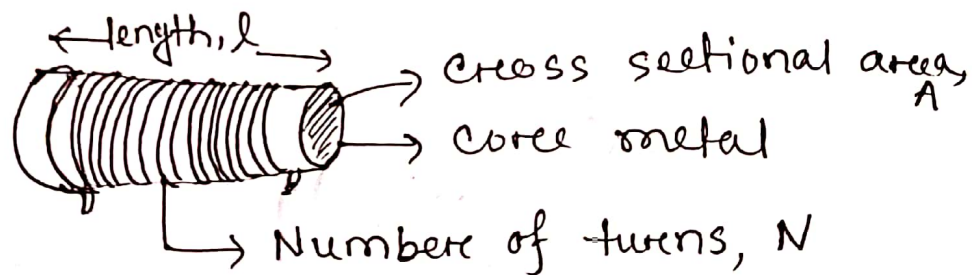

Typical form of Inductor

Properties \Rightarrow

- (i) Store energy
- (ii) Passive element

Inductor follows Henry's law.

$$\phi \propto i$$

$$\Rightarrow \frac{d\phi}{dt} = L \frac{di}{dt}$$

$$\therefore V = L \frac{di}{dt}$$

Here, L is the constant of proportionality called inductance.

$$L = \frac{N^2 \mu A}{l}$$

current-voltage relationship \Rightarrow

$$di = \frac{1}{L} V dt$$

$$\Rightarrow i = \frac{1}{L} \int_{-\infty}^t V(t) dt$$


$$\therefore i = \frac{1}{L} \int_{t_0}^t V(t) dt + i(t_0)$$

Inductor stores energy in its magnetic field.


$$P = Vi = L \left(\frac{di}{dt} \right) i$$

$$W = \frac{1}{2} Li^2$$

Symbols \Rightarrow

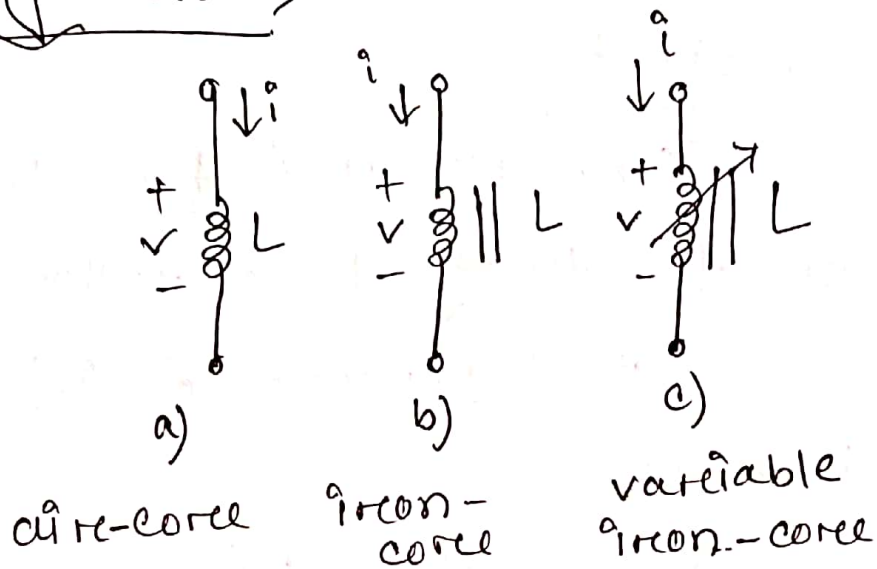

Short Circuit to DC \Rightarrow

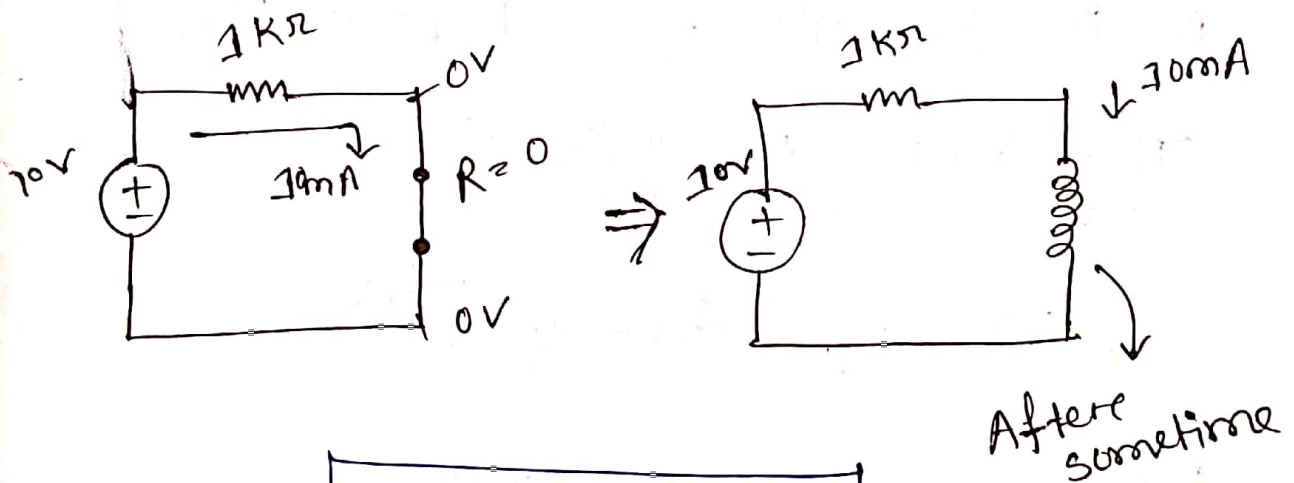

Transient Analysis

It determines a circuit's response over a period of time defined by the user. Since capacitor/inductor V/i cannot change abruptly, so.....

Time constant \Rightarrow

Time required for the response to decay to a factor of $1/e$ or 36.8 percent of its initial value.

For capacitor, $\tau = RC$
For Inductor, $\tau = L/R$ [unit-sec]

Basic formula for Exponential
Transient Analysis \Rightarrow

$$x(t) = x_f + (x_i - x_f) e^{-t/\tau}$$

Here, $x_i =$ initial value


$x_f =$ final "

$x(t) = v/i$ at time t

$t =$ given time

$\tau =$ time constant

Capacitor Example =)


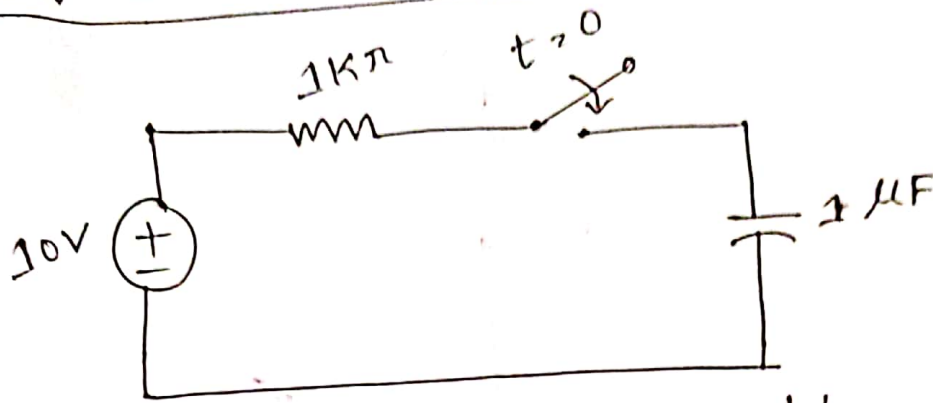


$$V(t) = ?$$

$$I(t) = ?$$

$$V(t) = V_f + (V_i - V_f) e^{-t/\tau}$$
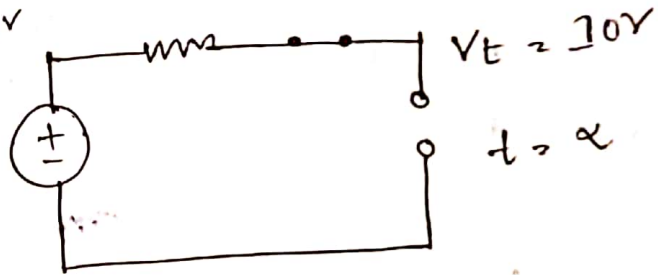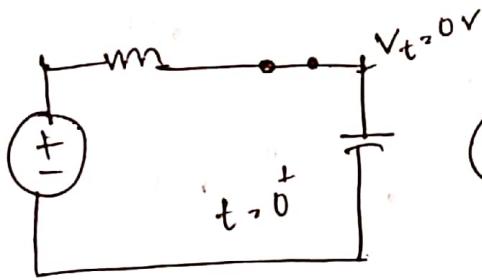
$$\text{Here, } \tau = RC = 1k\Omega \times 1\mu F \\ = 10^{-3} \text{ s}$$




$$I_i = \frac{10 - 0}{1k} \text{ A} = 10 \text{ mA}$$


$$I_f = 0 \text{ A}$$

$$\therefore V(t) = V_f + (V_i - V_f) e^{-t/10^{-3}} \\ = 10 + (0 - 10) e^{-1000t} \text{ V} \\ = 10 (1 - e^{-1000t}) \text{ V}$$
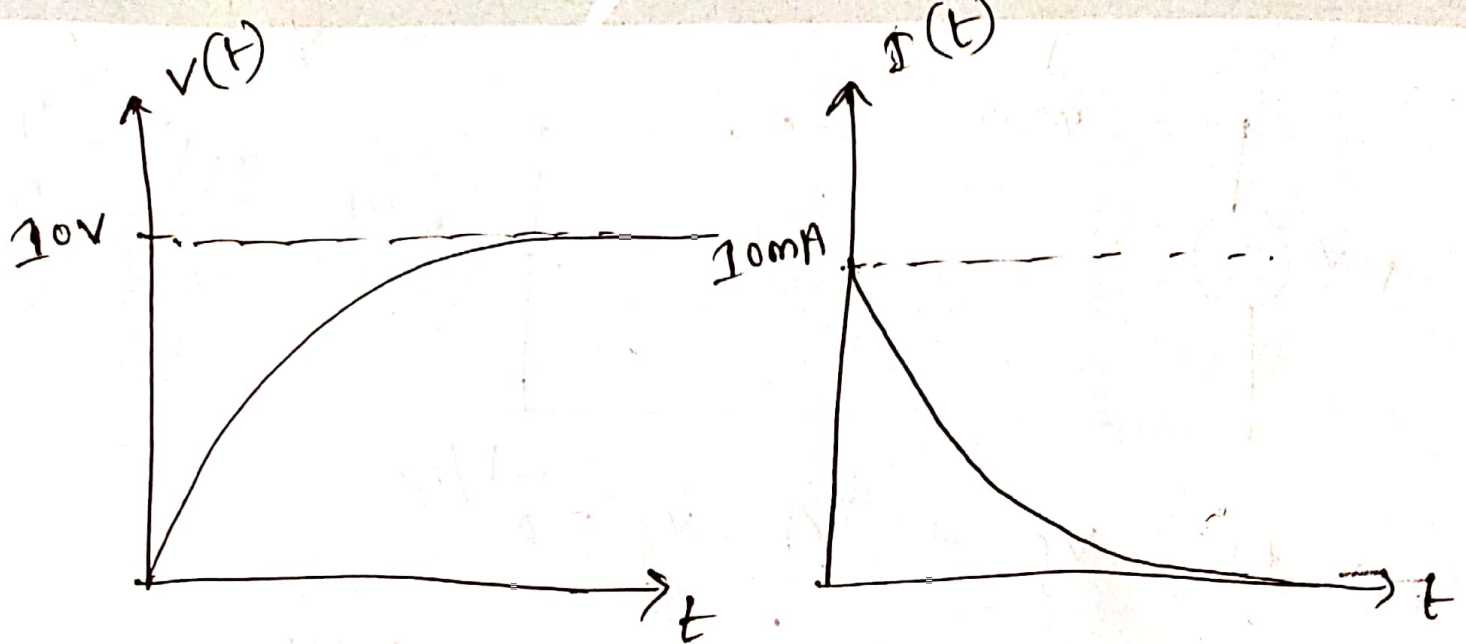
$$I(t) = I_f + (I_i - I_f) e^{-t/10^{-3}} \\ = 0 + (10 - 0) e^{-t/10^{-3}} \\ = 10 e^{-1000t} \text{ mA}$$



Inductor Example \Rightarrow

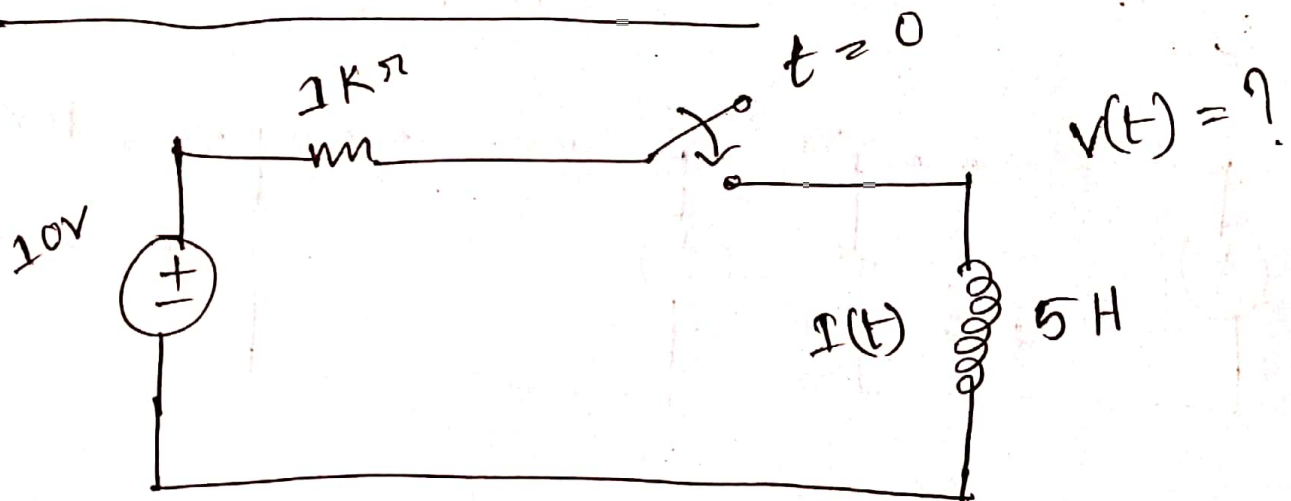

$$\tau = \frac{L}{R} = \frac{5}{1k} = 0.005s$$

