

CSE250

Name: Maruf Morshed

ID: 20101299

Section: 2

Experiment no: 3

Experiment name: Verification of KCL and KVL

Name of the experiment:

Verification of KCL and KVL.

KVL

Objective:

This experiment is intended to verify Kirchhoff's voltage law (KVL) with the help of series circuits.


Theory:

KVL states that around any closed circuit the algebraic sum of the voltage rises equals the algebraic sum of the voltage drops.

Apparatus:

- DC Ammeter.
- Multimeter
- Three resistors.
- DC power supply.

Circuit Diagram:

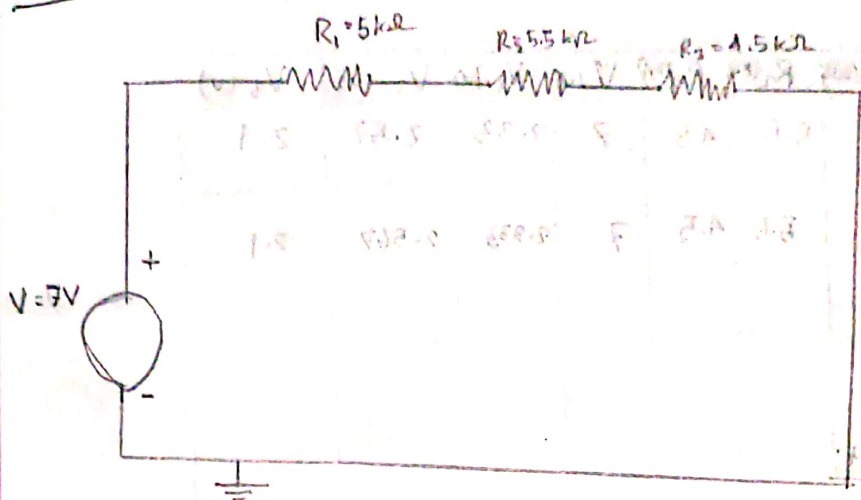

Result Analysis:

$$V = 7V$$

$$R_1 = 5k\Omega$$

$$R_2 = 5.5k\Omega$$

$$R_3 = 4.5k\Omega$$

$$R_1 + R_2 + R_3 = 15k\Omega$$

Now,

$$V_1 = \frac{R_1}{R} \times V_A$$

$$= \frac{5}{15} \times 7 = \left(\frac{7}{3}\right) V = 2.333V$$

$$V_2 = \frac{R_2}{R} \times V_A = \frac{5.5}{15} \times 7 = \left(\frac{77}{33}\right) V = 2.567V$$

$$V_3 = \frac{R_3}{R} \times V_A = \frac{4.5}{15} \times 7 = \left(\frac{21}{10}\right) V = 2.1V$$

$$\therefore V = \left(\frac{7}{3} + \frac{77}{33} + \frac{21}{10}\right) V = 7V$$

$$\therefore V = (2.333 + 2.567 + 2.1) = 7V$$

Table : 1:

Observation	$R_1 (\Omega)$	$R_2 (\Omega)$	$R_3 (\Omega)$	$V (\Omega)$	$V_1 (V)$	$V_2 (V)$	$V_3 (V)$
Experimental	5	5.5	4.5	7	2.33	2.57	2.1
Theoretical	5	5.5	4.5	7	2.333	2.567	2.1

Questions and report:

- 1) An ammeter is ~~connected~~ used to measure current and voltmeter is measured to used to measure the potential difference. An ammeter will be always connected in a series in a circuit as it have a low resistance while a voltmeter is connected in parallel as it have high resistance.
- 2) The results obtained in both experimental and theoretical observation is same. Therefore there is no discrepancies.


Objective:

This experiment is intended to verify Kirchhoff's law ΣI (KCL) with the help of a simple parallel circuit.

Apparatus:

- A DC Ammeter.
- Three resistors
- One Multimeter
- One DC supply.

Circuit Diagram:

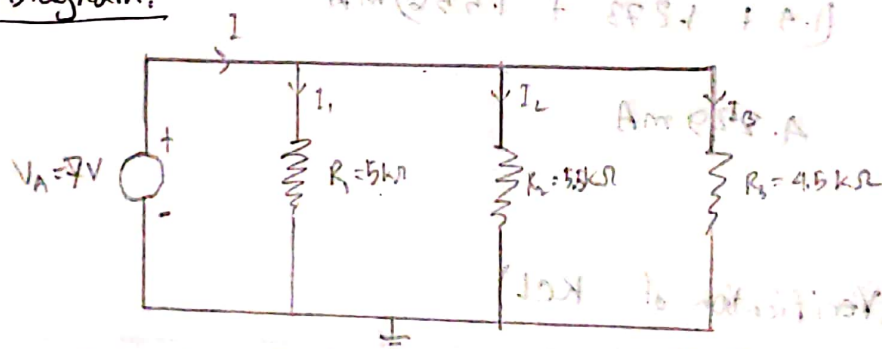

Result:

Given,

$$V_A = 7V$$

$$R_1 = 5k\Omega$$

$$R_2 = 5.5k\Omega$$

$$R_3 = 4.5k\Omega$$

Now,

$$R = \left(\frac{1}{5} + \frac{1}{5.5} + \frac{1}{4.5} \right)$$

$$= 1.6555 k\Omega$$

Now,

$$I = \frac{V_A}{R} = \frac{7}{1.6558} = 4.2228 \text{ mA}$$

$$I_1 = \frac{V_A}{R_1} = \frac{7}{5} = 1.4 \text{ mA}$$

$$I_2 = \frac{V_A}{R_2} = \frac{7}{5.5} = 1.273 \text{ mA}$$

$$I_3 = \frac{V_A}{R_3} = \frac{7}{4.5} = 1.556 \text{ mA}$$

$$\therefore I_0 = I_1 + I_2 + I_3$$

$$= (1.4 + 1.273 + 1.556) \text{ mA}$$

$$= 4.229 \text{ mA}$$

~~Q.10~~

Table : (Verification of KCL)

Observation	$R_1 (\text{k}\Omega)$	$R_2 (\text{k}\Omega)$	$R_3 (\text{k}\Omega)$	V	$I_1 (\text{mA})$	$I_2 (\text{mA})$	$I_3 (\text{mA})$	$I (\text{mA})$
Experimental	5	5.5	4.5	7	1.4	1.27	1.56	4.23
Theoretical	5	5.5	4.5	7	1.4	1.273	1.556	4.229

Report:

1) Here, the two ~~are~~ results ~~to~~ in experimental and theoretical setups are similar. Therefore, there is no ~~to~~ discrepancies.