


## Answer no-1 (Superposition)

Superposition principle: The principle states that, if there's more than one voltage or current source in a circuit, then each source are to act independently then to add current to it so ~~the~~ to find the voltage drops across each components. Each sub circuit has only one independent source. The principle is not applicable to power, because it is non-linear quantity

Answer no-2

'For the superposition method, some sources have to be ON and some have to be OFF while performing nodal analysis' While applying superposition principle each sub circuit has only one independent source the other independent sources are suppressed. So that some sources have to ON and some have to be OFF while performing nodal analysis.

(c) Keeping  $V_1 = 100V$  alive,

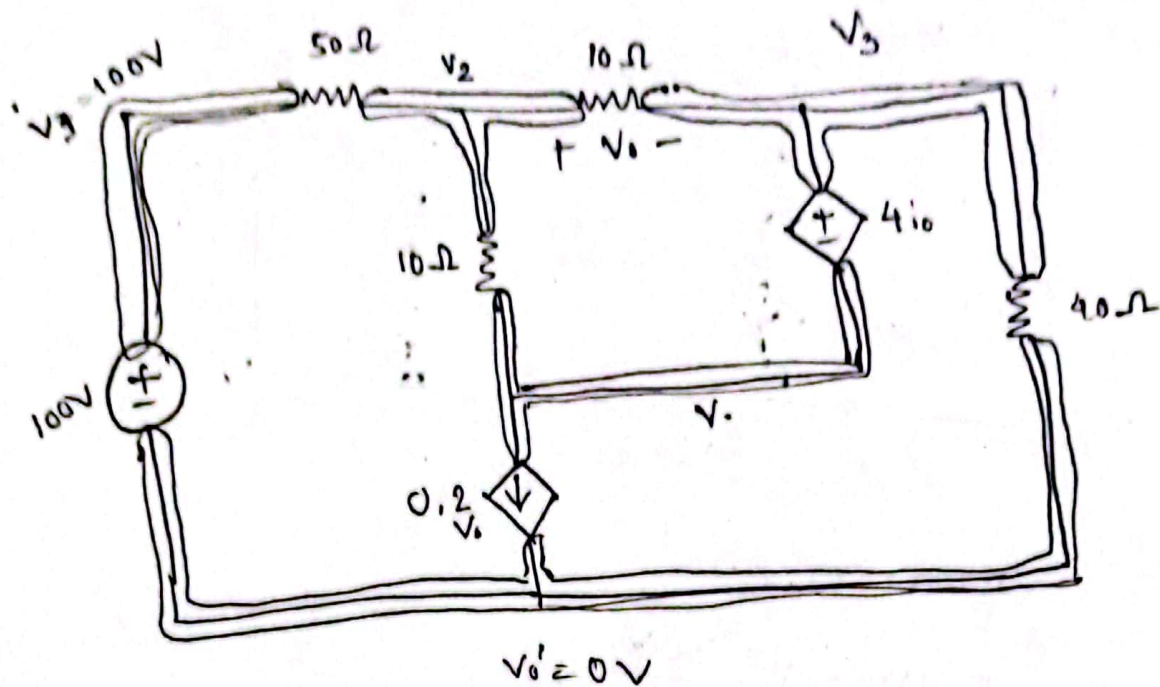

$$V_0 = V_2 - V_3 \quad \text{--- (i)}$$

$$V_1 = 100V \quad \text{--- (ii)}$$

$$V_2 = \left( \frac{1}{50} + \frac{1}{10} + \frac{1}{10} \right) \cdot \frac{V_4}{10} - \frac{V_3}{10} - \frac{V_1}{50} = 0 \quad \text{--- (iii)}$$

$$V_3 \left( \frac{1}{10} + \frac{1}{40} \right) - \frac{V_2}{10} + \frac{V_4}{10} - \frac{V_2}{10} + 0.2(V_2 - V_3) = 0 \quad \text{--- (iv)}$$

$$V_3 - V_4 - 4 \left( \frac{V_2 - V_4}{10} \right)$$

$$\Rightarrow 10V_3 - 10V_4 - 4V_2 + 4V_4 = 0$$

$$\Rightarrow 10V_3 - 6V_4 - 4V_2 = 0 \quad \text{--- (v)}$$

Solving the above eq<sup>n</sup> we get,

$$V_2 = 21.5686V$$


$$V_3 = 15.6863V$$

$$V_4 = 11.7647V$$

$$V_0 = V_2 - V_3 = 5.88235V$$

(d)

Keeping  $I = 2A$  alive

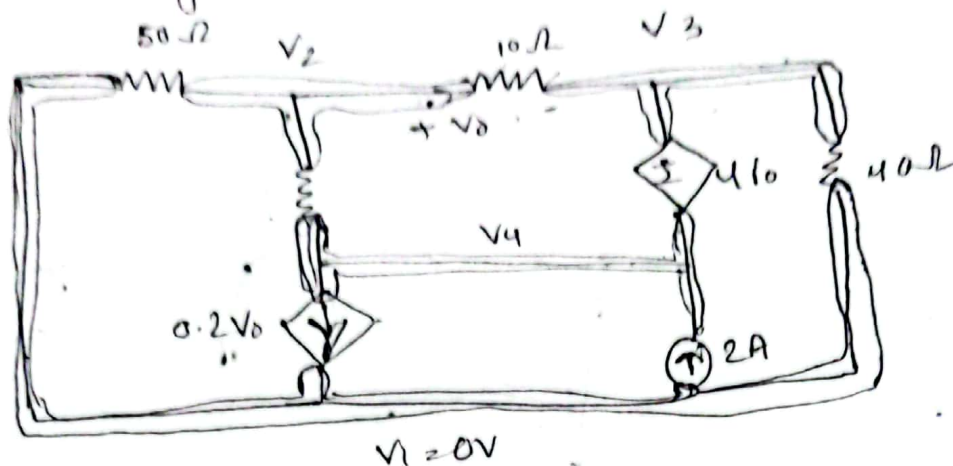

$$V_0' = V_2 - V_3 \quad \text{--- (iv)}$$

$$V_3 - V_4 = 4 \left( \frac{V_2 - V_4}{10} \right)$$

$$\Rightarrow 10V_3 - 6V_4 - 4V_2 = 0 \quad \text{--- (i)}$$

$$V_2 \left( \frac{1}{50} + \frac{1}{10} + \frac{1}{10} \right) - \frac{V_3}{10} - \frac{V_4}{10} = 0 \quad \text{--- (ii)}$$

$$V_3 \left( \frac{1}{10} + \frac{1}{40} \right) - \frac{V_2}{10} + V_4 \left( \frac{1}{10} \right) - \frac{V_2}{10} + 0.2(V_2 - V_3) = 0$$

$$V_1 = 0V \quad \text{--- (v)}$$

Solving we get,

$$V_2 = 62.7451V$$

$$V_3 = 67.451V$$

$$V_4 = 70.5882V$$

$$V_0' = -4.70586V$$










(e) we know according to superposition principle

$$\begin{aligned} V_{\text{total}} &= V_0 + V_0' \\ &= 5.88235 - 4.70588 \\ &= 1.176 \text{ V. (Ans).} \end{aligned}$$

# Transient Analysis

## Answer no-1

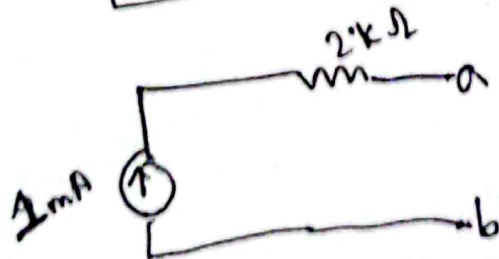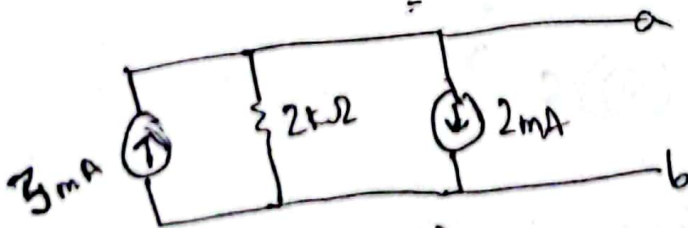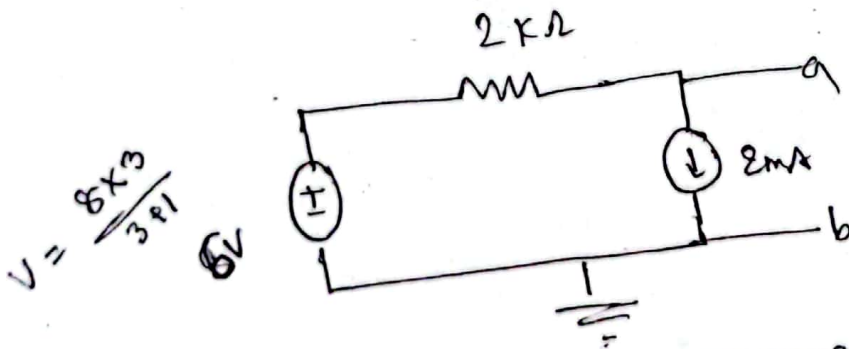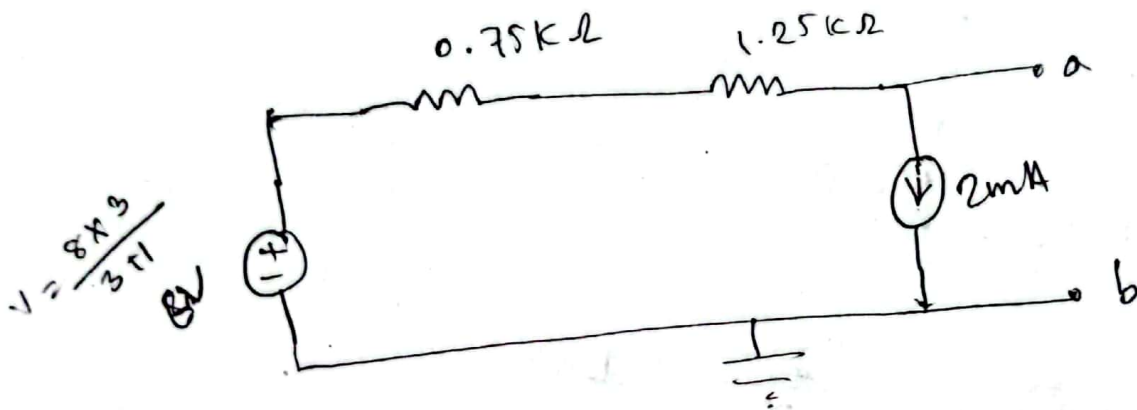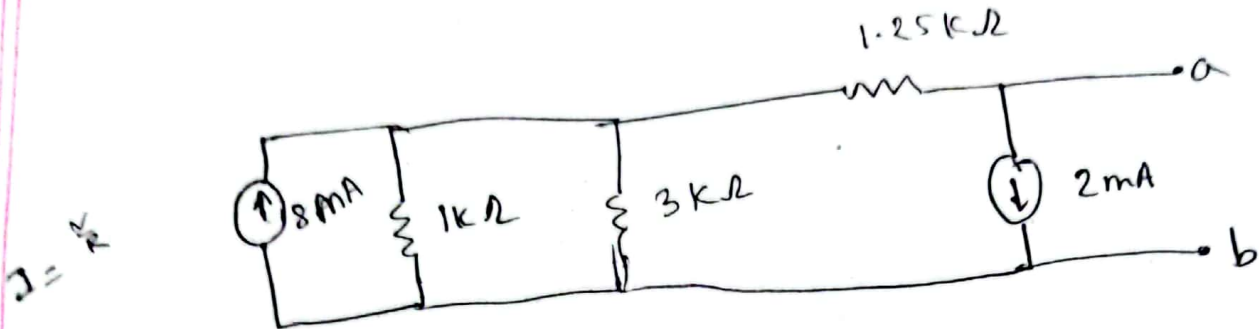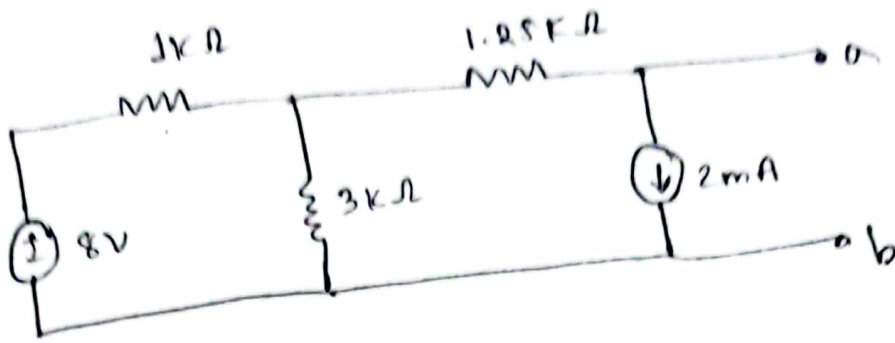


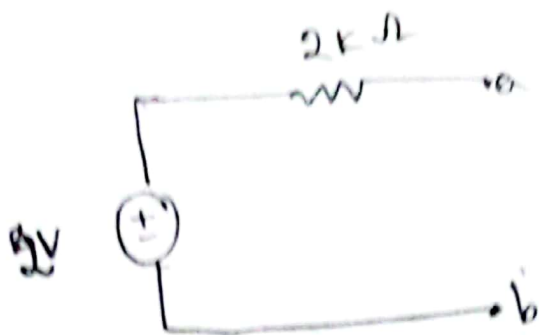

$$V_1 = 2V$$

$$R_1 = 2k\Omega$$

at  $t = 0$

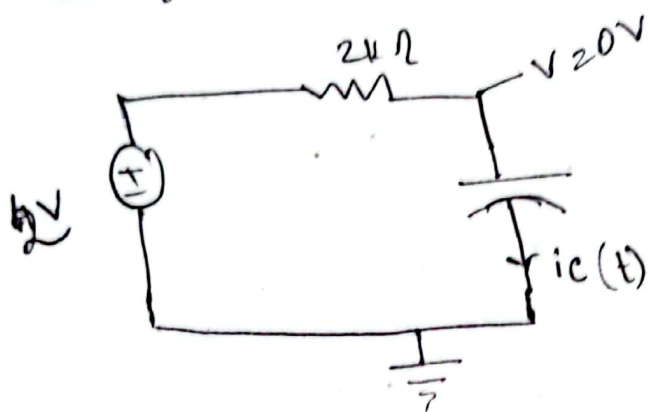

$$i_c(t) / i_c(0^+) = \frac{2}{2} = 1 \text{ mA}$$

$$\tau = R \times C$$

$$= 2 \times 1 \mu$$

$$= 2 \times 10^{-3} \text{ sec}$$







$$i(t) = i(\infty) + (i(0^+) - i(\infty)) e^{-\frac{t}{\tau}}$$

$$= 0 + (1 - 0) e^{-\frac{t}{2 \times 10^{-3}}}$$


$$= 1 \times e^{(-t \times 500)}$$

$$= e^{-500t}$$

2

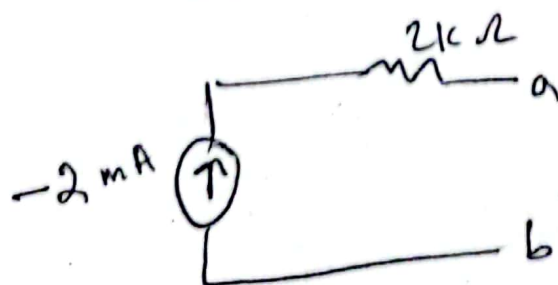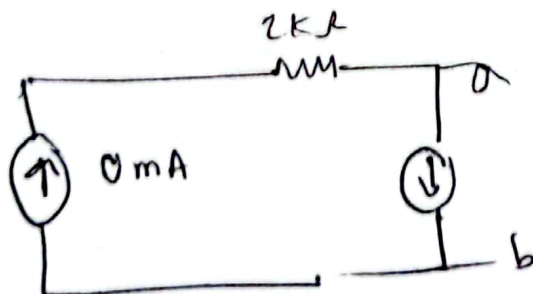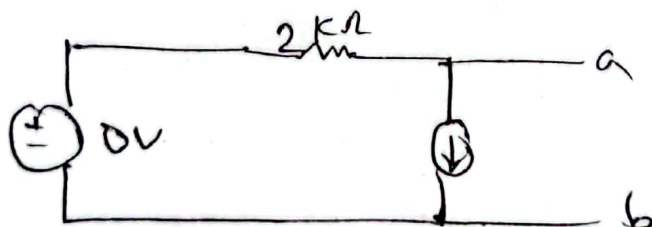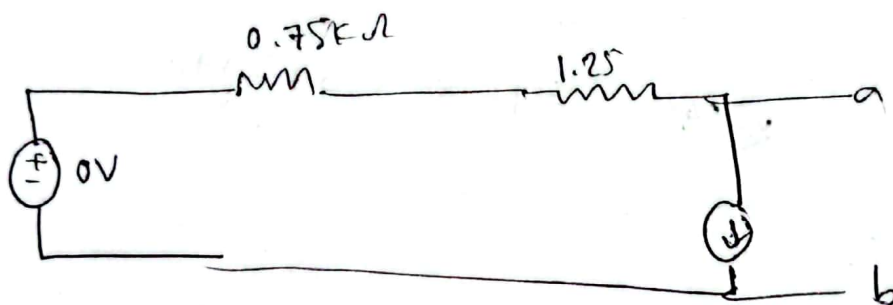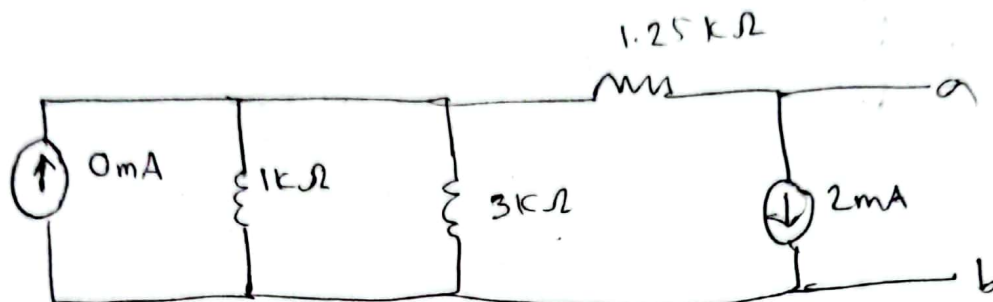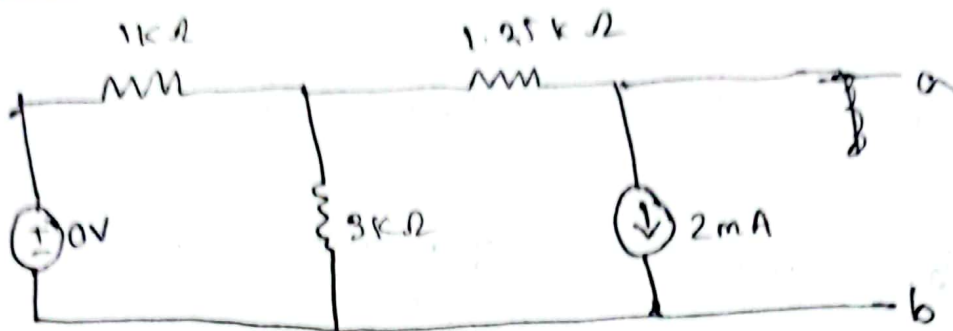



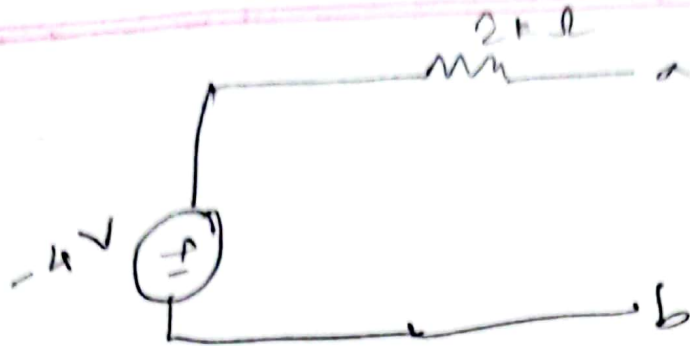

at  $t = 0$

$$i_C(0^+)/i_C(t) = \frac{-4}{2} = -2 \text{ mA}$$

$$\tau = RC$$

$$= 2 \times 10^3 \times 100 \times 10^{-6} = 2 \times 10^{-3} \text{ sec}$$







$$i_C(t) = i(\infty) + (i(0^+) - i(\infty)) \cdot e^{-t/\tau}$$


$$= 0 + (-2 - 0) e^{-\frac{t}{2 \times 10^{-3}}}$$

$$= -2 \times e^{-\frac{t}{2 \times 10^{-3}}}$$

$$= -2 e^{-500t}$$

3

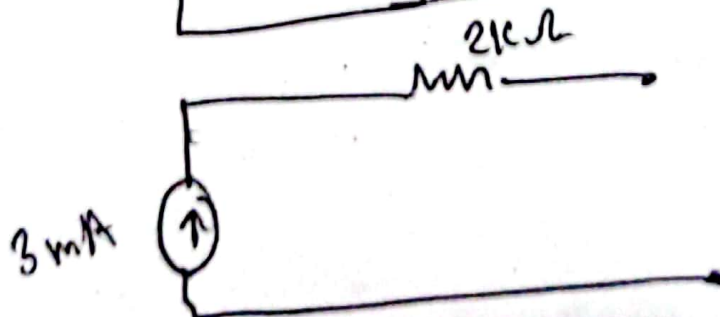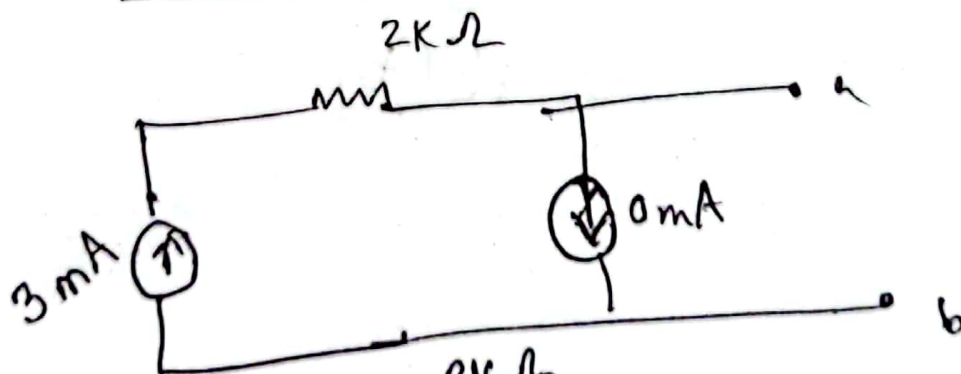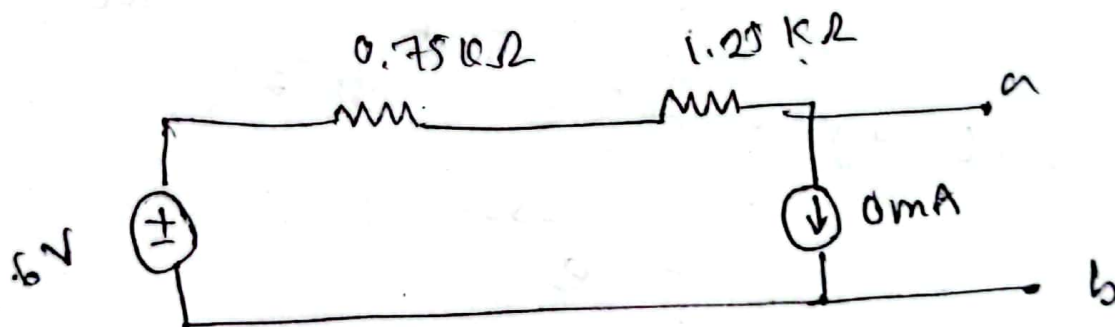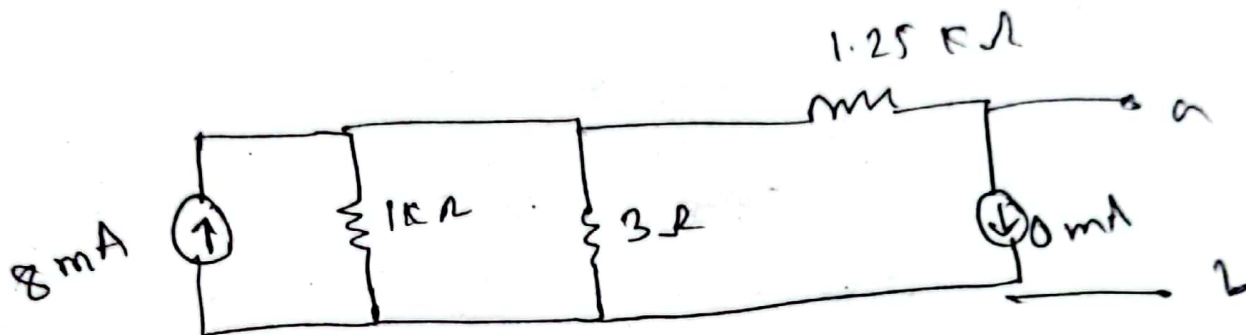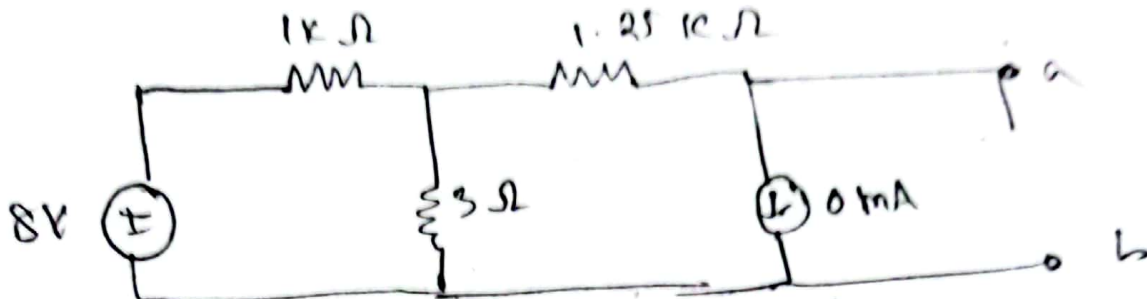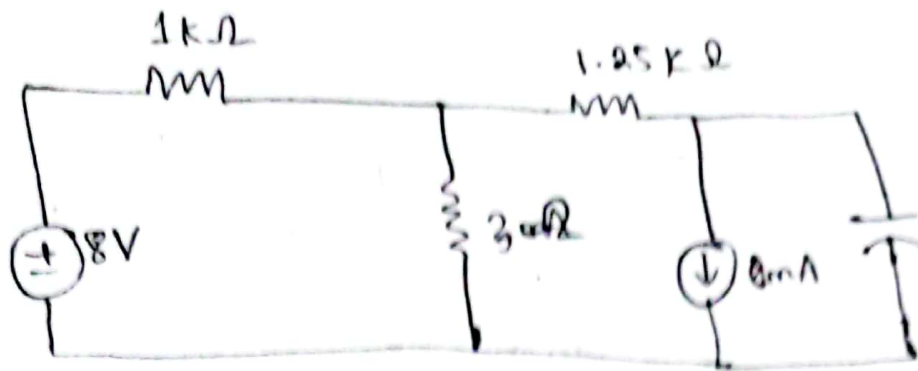

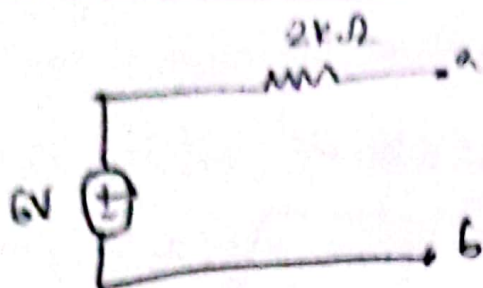

$$V = 6V$$

$$R = 2k\Omega$$

$$i(0^+) = \frac{6}{2} = 3mA$$

$$\tau = R \times C$$

$$= 2 \times 1\mu$$

$$= 2 \times 10^{-3} \text{ sec}$$

$$i_{C2}(t) = i(\infty) + (i(0^+) - i(\infty)) e^{-\frac{t}{\tau}}$$

$$= 0 + (3 - 0) e^{-\frac{t}{2 \times 10^{-3}}}$$

$$= 3 e^{-500t}$$

$$\begin{aligned} \textcircled{4} \quad i_{C1}(t) + i_{C2}(t) &= -2 e^{-500t} + 3 e^{-500t} \\ &= e^{-500t} \\ &= i_C(t) \end{aligned}$$

Yes, the superposition principle work in case of time varying current also.