

Experiment name:

Verification of superposition principle.

Objective:


To verify experimentally the superposition theorem which is an analytical technique of determining currents in a circuit with more than one emf source.

Apparatus:


- i) Two DC power supplies.
- ii) One multimeter etc.

Circuit Diagram:


for circuit - I,

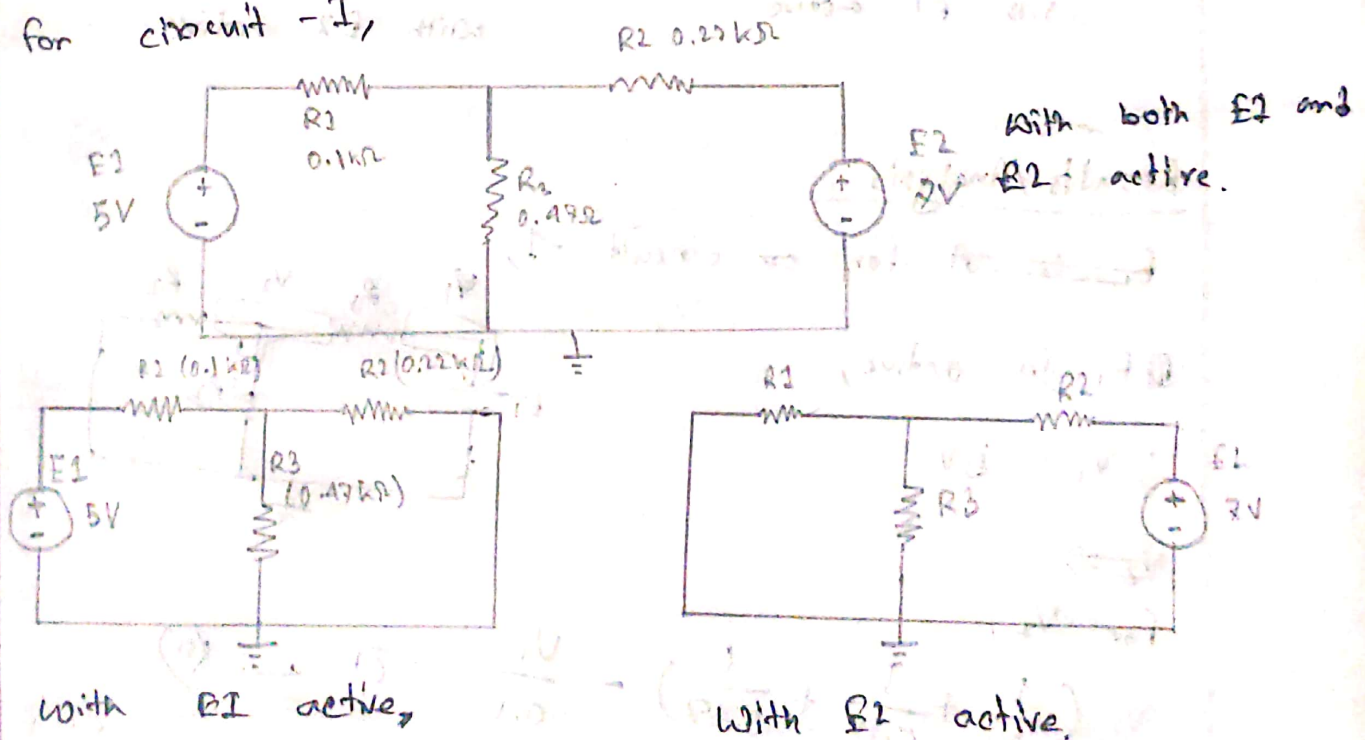


For circuit - 2,

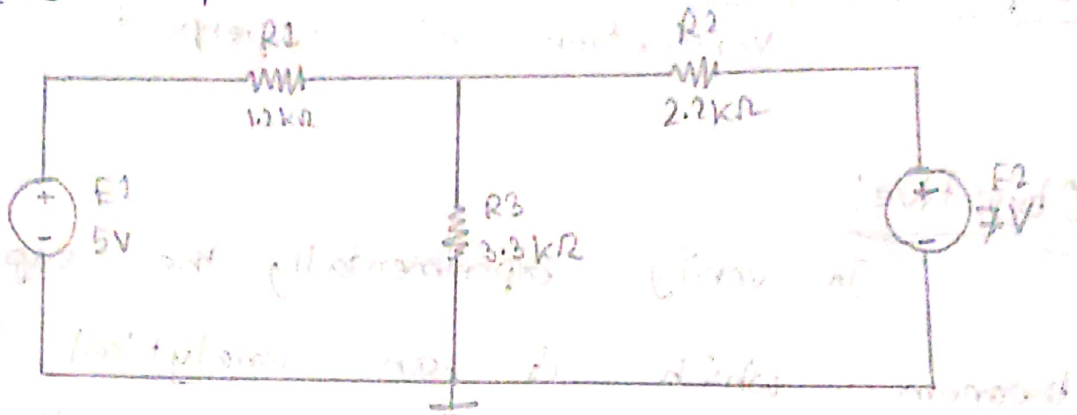

With both  $E_1$  and  $E_2$  active,

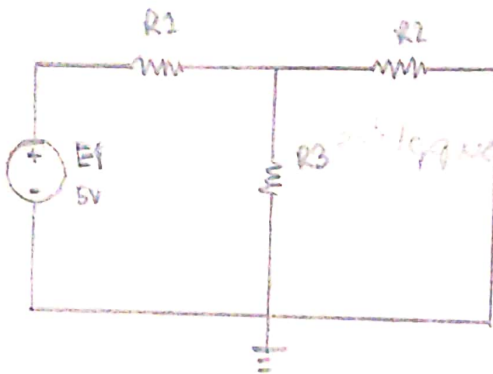

With  $E_1$  active

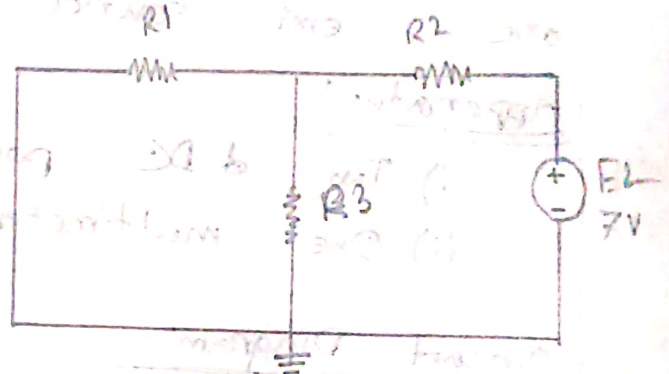

With  $E_2$  active.

Results/Analysis:

~~$E_1$  is~~ A for circuit - 1,


$E_1$  is active,

$$\therefore V_1 = 5V$$

$V_2 \Rightarrow$

For  $V_2$ ,
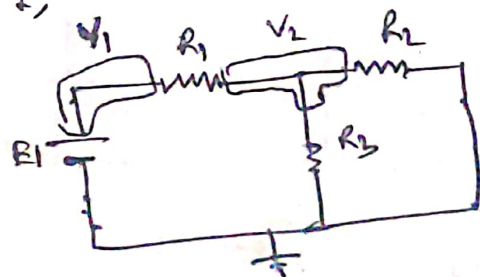
$$V_2 \left( \frac{1}{0.1} + \frac{1}{0.22} + \frac{1}{0.47} \right) - \frac{V_1}{0.1} = 0 \quad \text{--- (1)}$$



Putting  $V_1$  in eq<sup>n</sup>(11),

$$V_2 = \left( \frac{8620}{517} \right) = 16.67$$

or,  $V_2 = \cancel{2.998} \quad 2.999$

$I_3 =$


Hence,

$$I_3 = \frac{V_2 - V_3}{R_3}$$

$$= \frac{V_2 - 0}{0.47}$$

$$= \frac{2.999}{0.47} = 6.38051 \text{ A}$$

Again,  $E_2$  is active

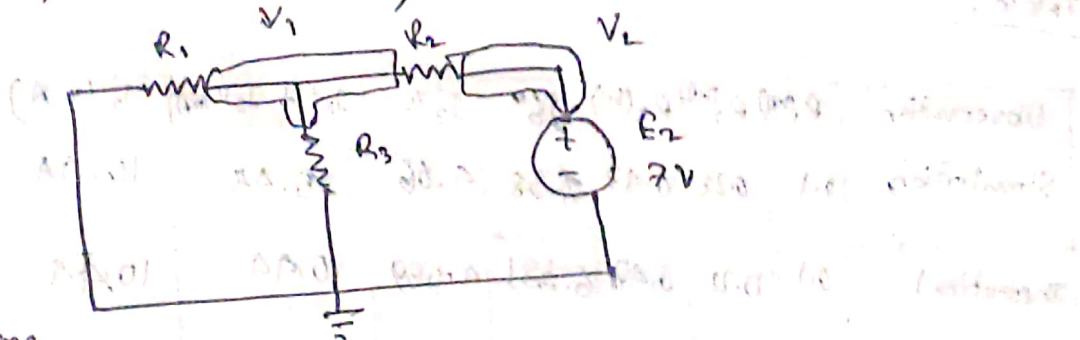

Hence,

$$V_2 = 7 \text{ V}$$

For  $V_1$ ,

$$V_1 \left( \frac{1}{0.1} + \frac{1}{0.22} + \frac{1}{0.47} \right) - \frac{V_2}{0.22} = 0$$

$$\text{or, } V_1 = \frac{e \ 517}{8620} \times \frac{7}{0.22} = 1.908 \text{ V}$$

Now,

$$I_3'' = \frac{V_1 - V_3}{R_3}$$

$$= \frac{V_1 - 0}{0.47}$$

$$= 4.0596 \text{ A.}$$

According to superposition theorem,

$$\therefore I_3 = I_3' + I_3''$$

$$= 6.381 + 4.059$$

$$= 10.44 \text{ A}$$


Table!

Observation	$R_1(\text{M})$	$R_2(\text{K})$	$R_3(\text{K})$	$I_3'$	$I_3''$	$I_3' + I_3'' (\text{mA})$	$I_3 (\text{mA})$
Simulation	0.1	0.22	0.47	6.38	4.06	10.44	10.44
Theoretical	0.1	0.22	0.47	6.381	4.059	10.44	10.44



For circuit - 2,

Q. Hence,  $E_1$  is active,

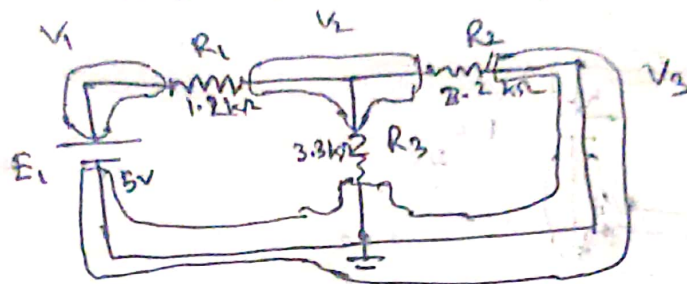

$$V_1 = 5V, \quad V_3 = 0$$

For  $V_2$ ,

$$V_2 \left( \frac{1}{1.2} + \frac{1}{2.2} + \frac{1}{3.3} \right) - \frac{V_1}{1.2} = 0$$

$$V_2 = \frac{V_1}{1.2} \div \left( \frac{1}{1.2} + \frac{1}{2.2} + \frac{1}{3.3} \right)$$

$$= \frac{5}{1.2} \div 1.58$$


$$= 2.61904$$

Now,

$$I_3' = \frac{V_2 - V_3}{R_3} = \frac{2.619}{3.3} = 0.79364$$

Again,

$E_2$  is active,

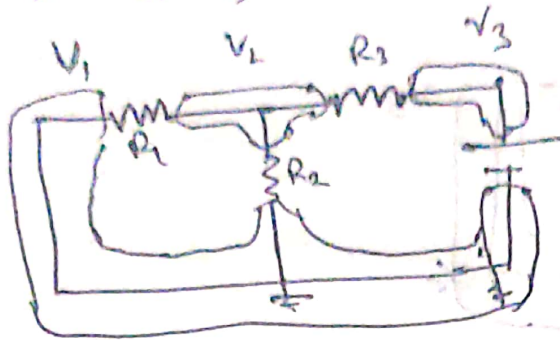

Now,

$$V_3 = 2V, \quad V_1 = 0$$

For  $V_2$ ,

$$V_2 \left( \frac{1}{1.2} + \frac{1}{2.2} + \frac{1}{3.3} \right) - \frac{V_3}{1.2} = 0$$

$$\text{or, } V_2 = \frac{V_3}{2.2} \div \left( \frac{1}{1.2} + \frac{1}{2.2} + \frac{1}{3.3} \right)$$

$$= \frac{2}{3.667} = 0.545$$

Now,

$$I_3'' = \frac{V_2 - V_1}{R_3} = 0.606A$$

At superposition principle

$$I_3 = I_3' + I_3''$$

$$= 0.793 + 0.606$$

$$= 1.4A$$

Observation	$R_1$ (k $\Omega$ )	$R_2$ (k $\Omega$ )	$R_3$ (k $\Omega$ )	$I_{3'}$ (mA)	$I_{3''}$ (mA)	$I_3 = I_{3'} + I_{3''}$ (mA)	$I_3$ (mA)
Simulation	1.2	2.2	3.3	0.79	0.61	1.4	1.4
Theoretical	1.2	2.2	3.3	0.794	0.606	1.4	1.4

### Discussion:

Hence, we analyzed the ~~to~~ superposition principle by by both theoretical and simulated calculation and found that both are equal. So, it can be called as the superposition theorem and it is a successful experiment.