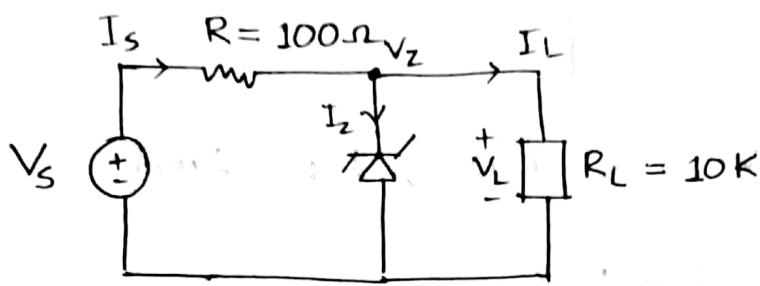


# 1. Week 6 Problem



Given,  $V_{z_0} = 3V$ ,  $r_z = 0\Omega$ ,  $I_{ZK} = 1mA$

worst case:

$$I_z = I_{ZK} = 1mA$$

$$\therefore V_L = V_z = V_{z_0} + I_z r_z$$

$$= 3 + 1 \times 0$$

$$= 3V$$

$$\therefore I_L = \frac{V_L}{R_L} = \frac{3}{10k} = 0.3mA$$

$$\therefore I_s = I_z + I_L = (1 + 0.3)mA = 1.3mA$$

$$\text{Now, } I_s = \frac{V_s - V_z}{R}$$


$$R = 100\Omega$$

$$= 0.1k\Omega$$

$$\Rightarrow V_s = V_z + I_s R$$

$$= 3 + 1.3 \times 0.1 = 3.13V$$

2.

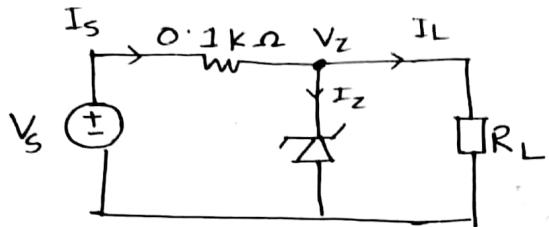

Given,  $V_{z0} = 3V$ ,  $r_z = 0\Omega$ ,  $I_{zk} = 1mA$

$$V_s = 5V \pm 5 \times 10\%$$

$$R_L = ? \quad (\text{worst case})$$

Answer: worst case scenario,

$$I_z = I_{zk} = 1mA$$

$$\therefore V_L = V_z = V_{z0} + I_z r_z = 3 + 1 \times 0 = 3V$$

$$V_s = V_s(\min) \quad [\text{for worst case}]$$

$$= 5 - 5 \times 10\%$$

$$= 4.5V$$


$$\therefore I_s = \frac{V_s - V_z}{0.1k\Omega} = \frac{4.5 - 3}{0.1} = 15mA$$

$$\therefore I_L = I_s - I_z = 15 - 1 = 14mA$$

$$\therefore R_L = \frac{V_L}{I_L} = \frac{V_Z}{I_L} = \frac{3V}{14mA} = 0.214 \text{ k}\Omega \quad [Ans]$$

3. NAND gate truth Table:

A	B	OUT
0	0	1
0	1	1
1	0	1
1	1	0

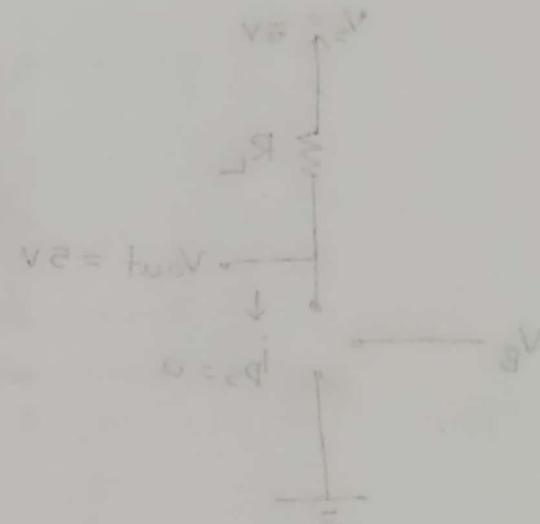

When A = 0

B	OUT
0	1
1	1

When A = 1

B	OUT
0	1
1	0



⇒ For this particular problem, we need this.

Because we can see, when one input is high, the gate will behave like an inverter


For S-Model: Given,  $V_T = 1V$

$$V_B < V_T$$

$$V_B \geq V_T$$

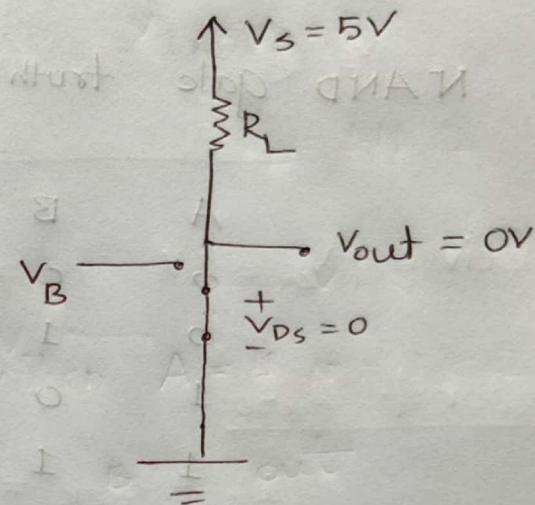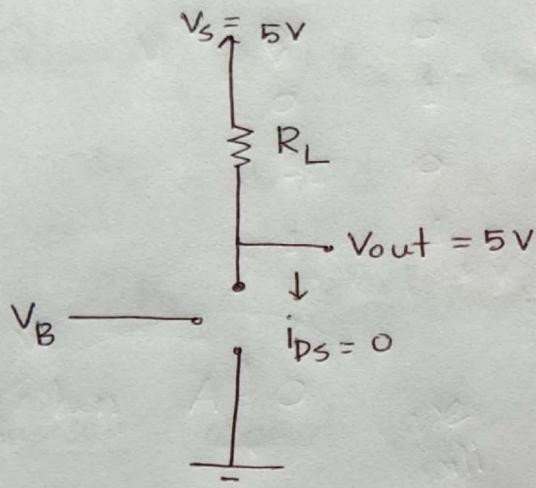


∴ Transfer characteristics graph:

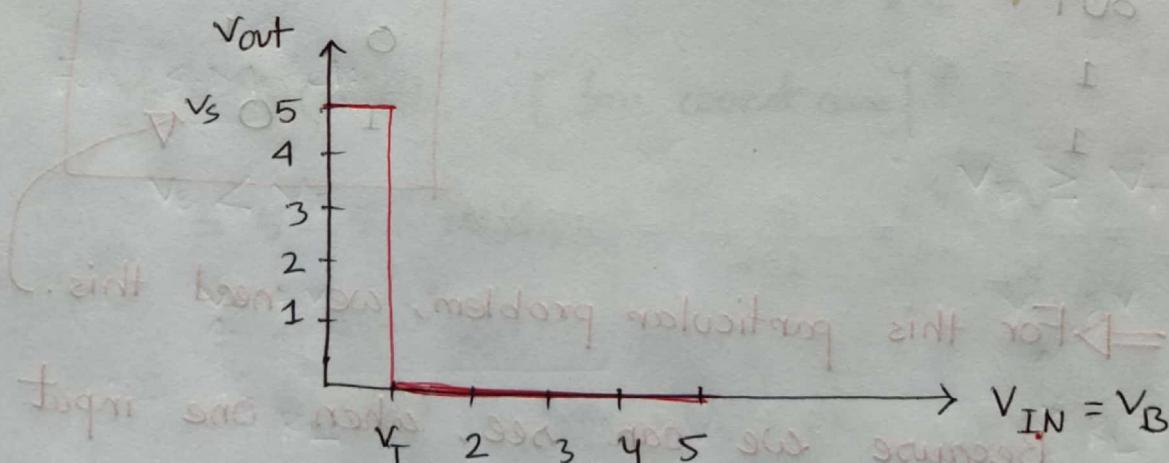

as shown no shift occurs if we stop at the input as

Given,
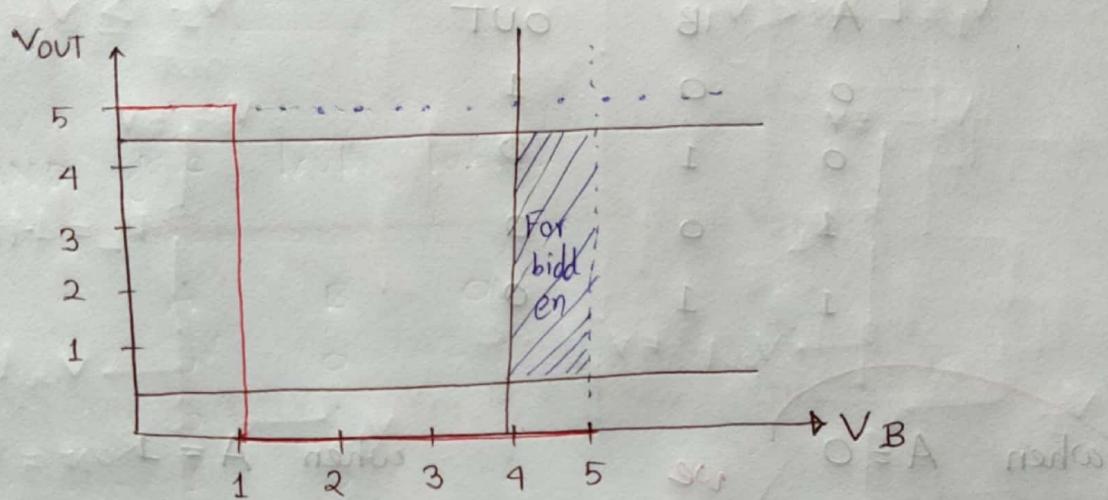
$$V_{OH} = 4.4V, V_{OL} = 0.5V, V_{IH} = 3.9V$$



From the figure, we can clearly see, the maximum value of  $V_{IL}$  can be

$$V_{IL} \leq V_T$$

$$V_T \leq V_{IL} \Rightarrow V_{IL} \leq 1V$$


Also, for static discipline, we know,  $V_{IL} > V_{OL}$ .

$$V_{OL} < V_{IL} < V_T$$

$$0.5 < V_{IL} < 1V$$

4. NOR gate Truth Table:

A	B	OUT
0	0	1
0	1	0
1	0	0
1	1	0

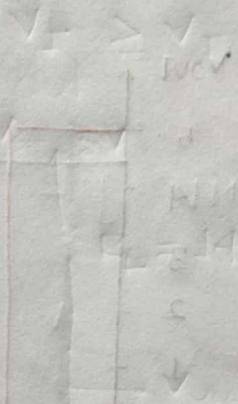

when  $A = 0$

B	OUT
0	1
1	0


we will take this

when  $A = 1$


B	out
0	0
1	0

For S-Model:


$$V_B < V_T$$

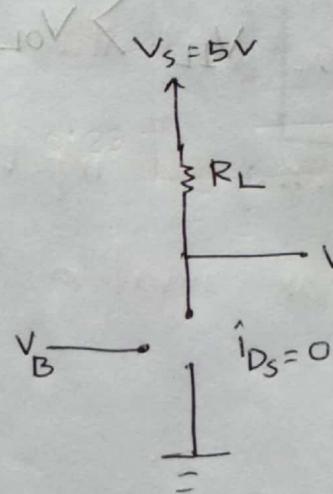


$$V_B \geq V_T$$

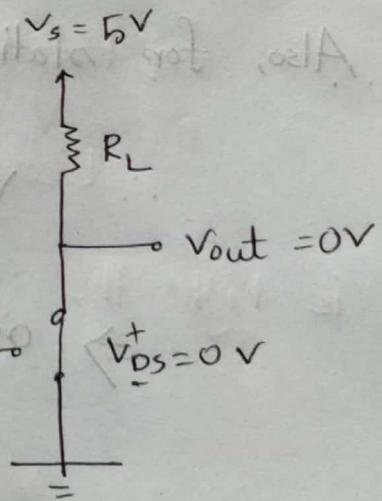

Transfer characteristics:

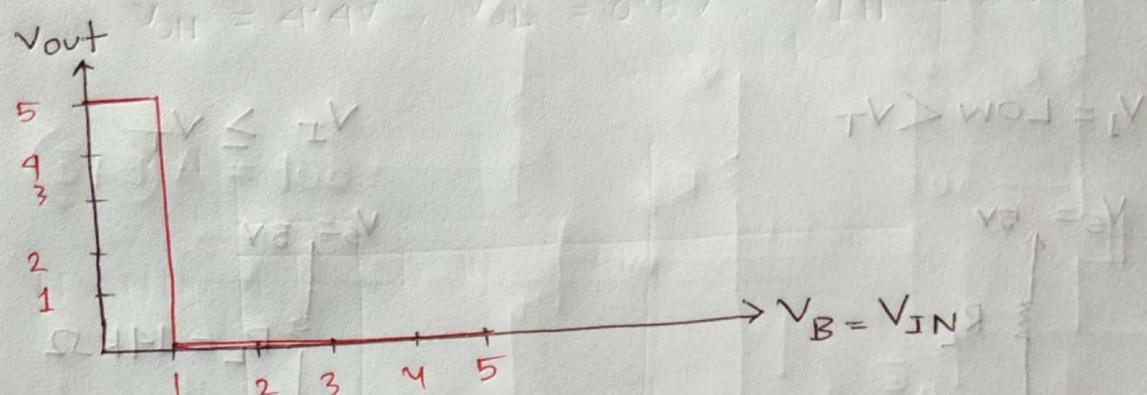

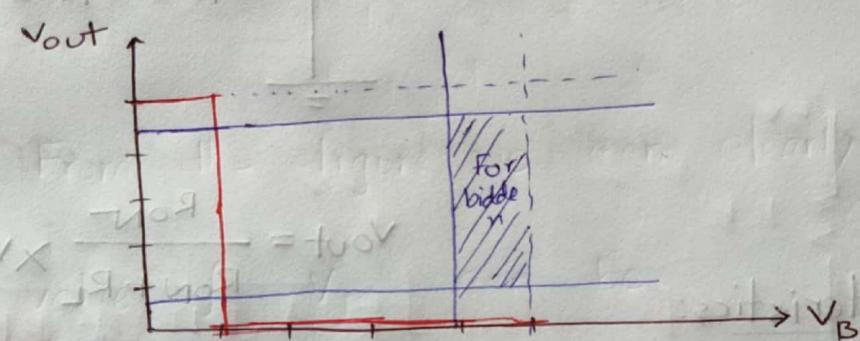Given,  $V_{OH} = 4.4V$ ,  $V_{OL} = 0.5V$ ,  $V_{IH} = 3.9V$



To avoid invalid region,  $V_{IL} < V_T$


To meet tighter restrictions,  $V_{IL} > V_{OL}$

Also,  $\therefore V_{OL} < V_{IL} < V_T$


$$\Rightarrow 0.5 < V_{IL} < 1$$

5. For SR model:


$$V_I = \text{LOW} < V_T$$

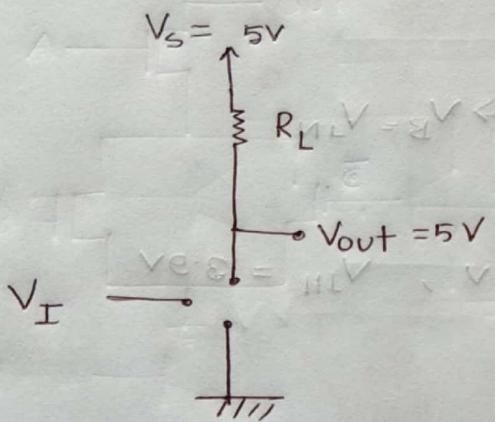

$$V_I \geq V_T$$

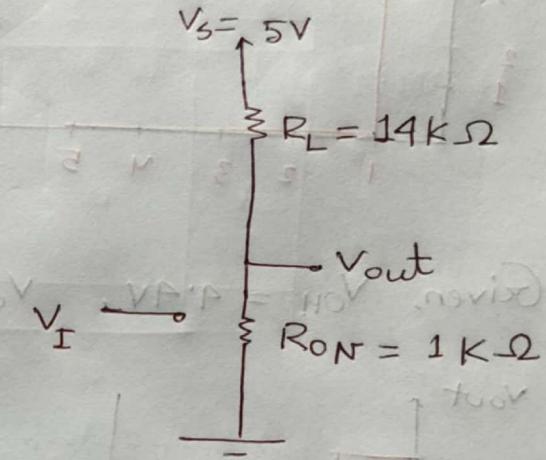


Transfer Characteristics:

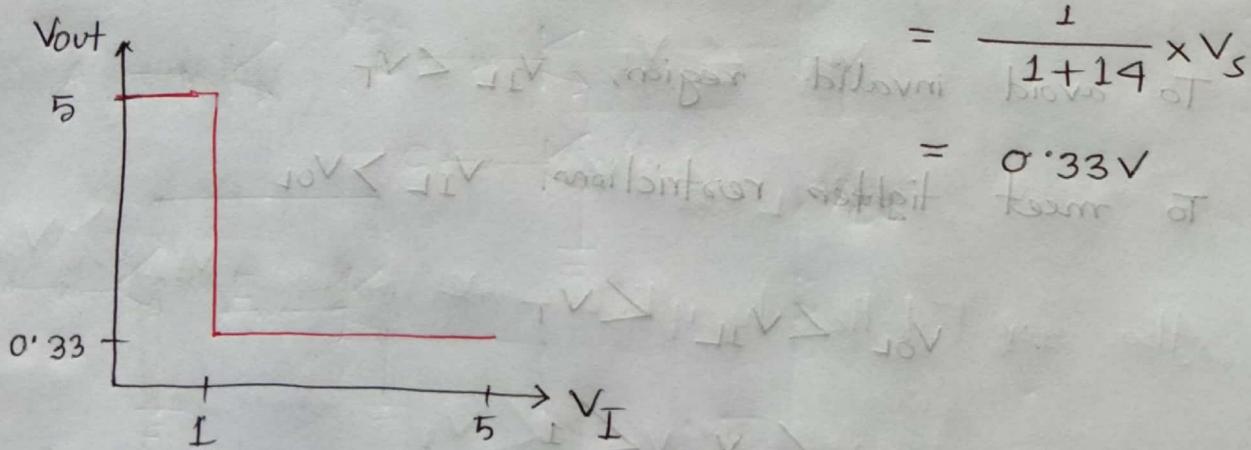

Given,
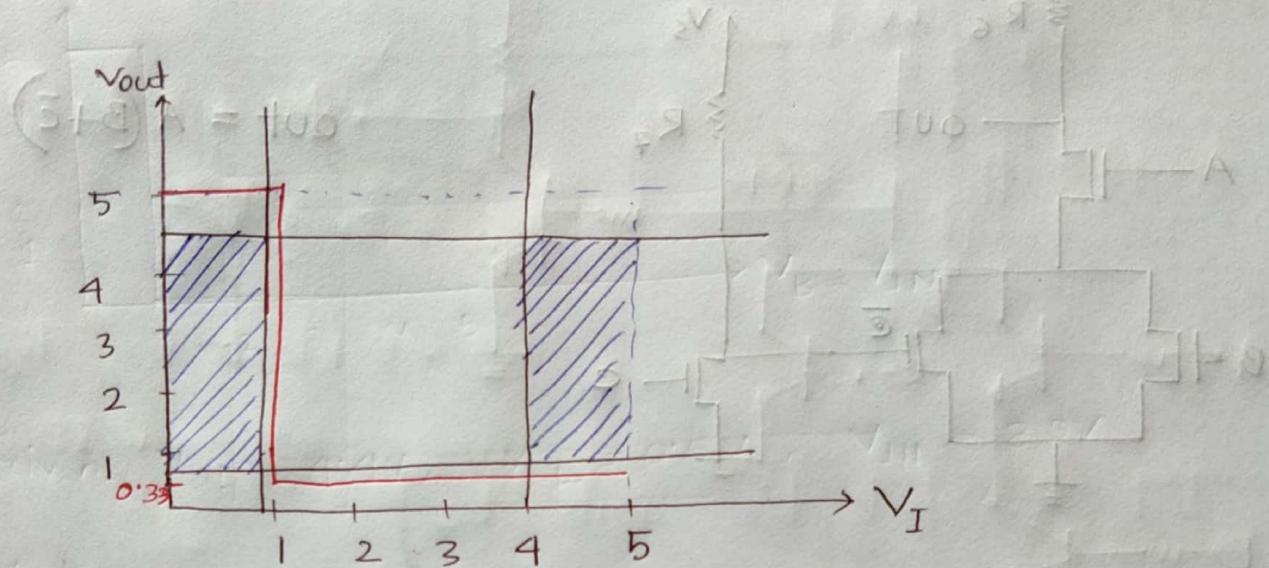
$$V_{OH} = 4.5V, V_{OL} = 0.5V, V_{IH} = 4V, V_{IL} = 0.9V$$



Yes, the specification follows static discipline.

\*\* If the specification does not work:  $\Rightarrow$


design condition:

$$\frac{R_{ON}}{R_L + R_{ON}} \times V_S < V_{OL}$$

$$\text{If for } R_L : \Rightarrow R_L > \frac{V_S}{V_{OL}} \times R_{ON} - R_{ON}$$


$$\text{If for } R_{ON} \Rightarrow R_{ON} < \frac{V_{OL}}{V_S - V_{OL}} \times R_L$$
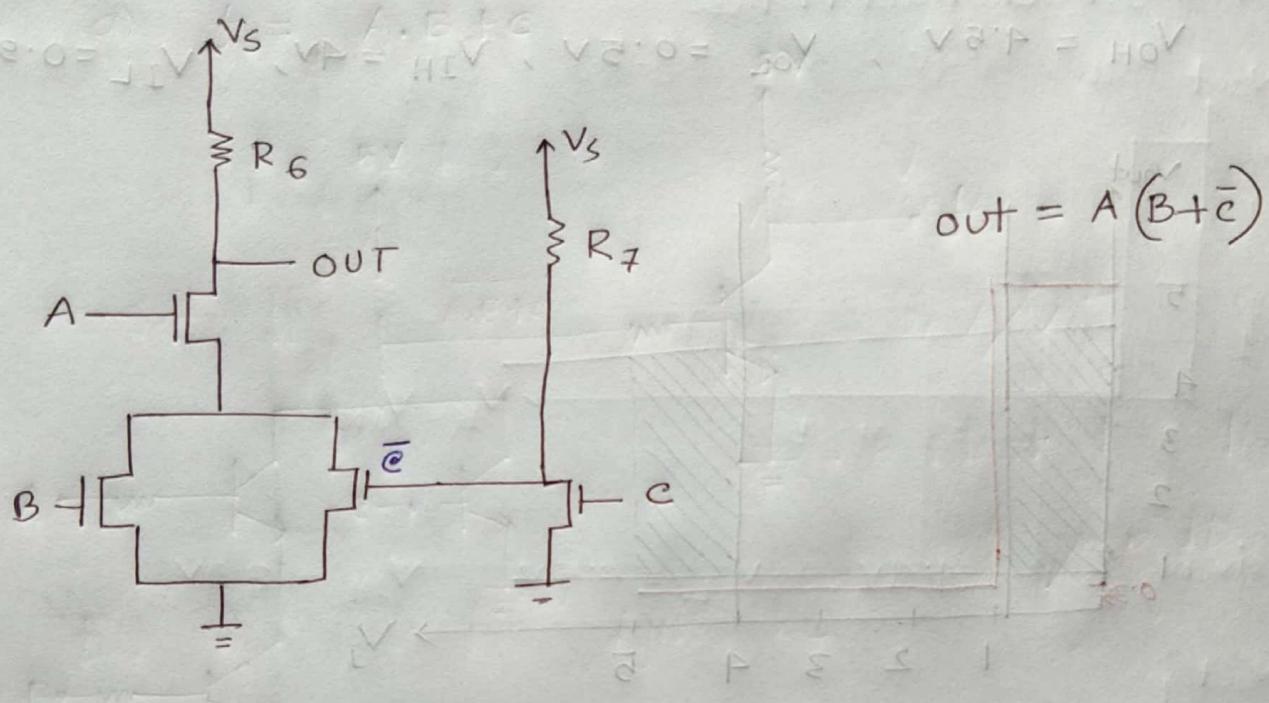
$$6. V_o = V_s - V_p = 1V \quad V_p = 1V \quad V_{oH} = 0.5V \quad V_{oL} = 0V$$




7.

(a)

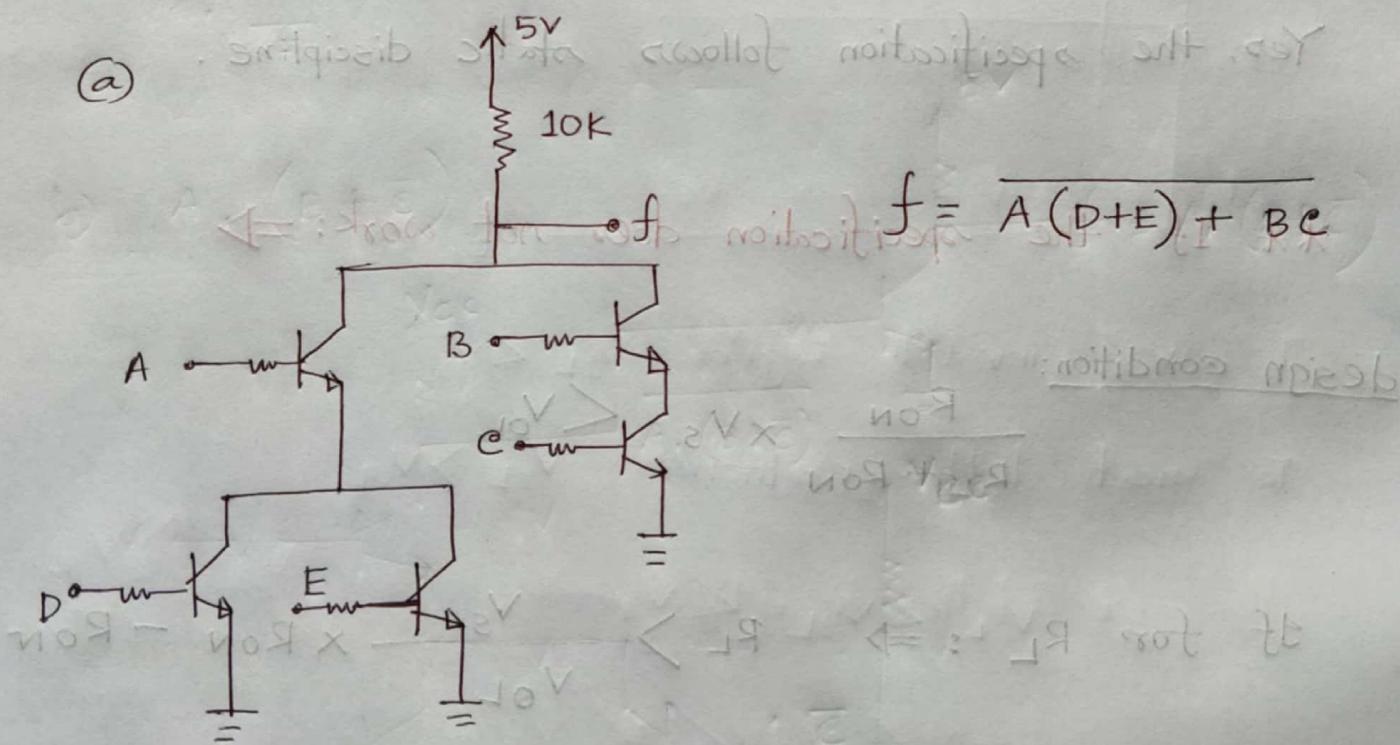


(b)

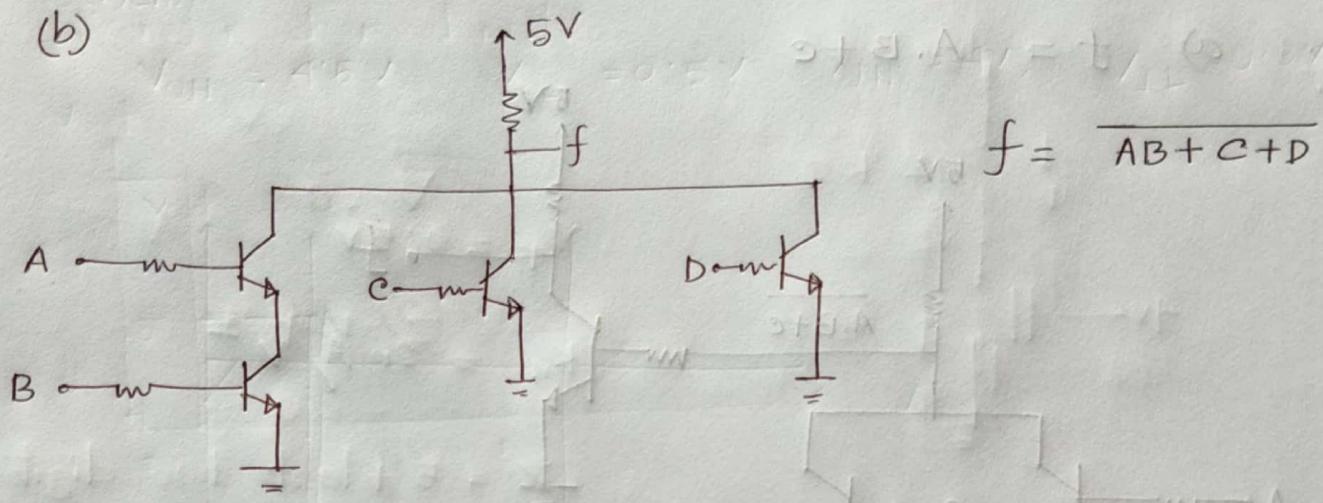


$$f = \overline{AB + C + D}$$

(c)

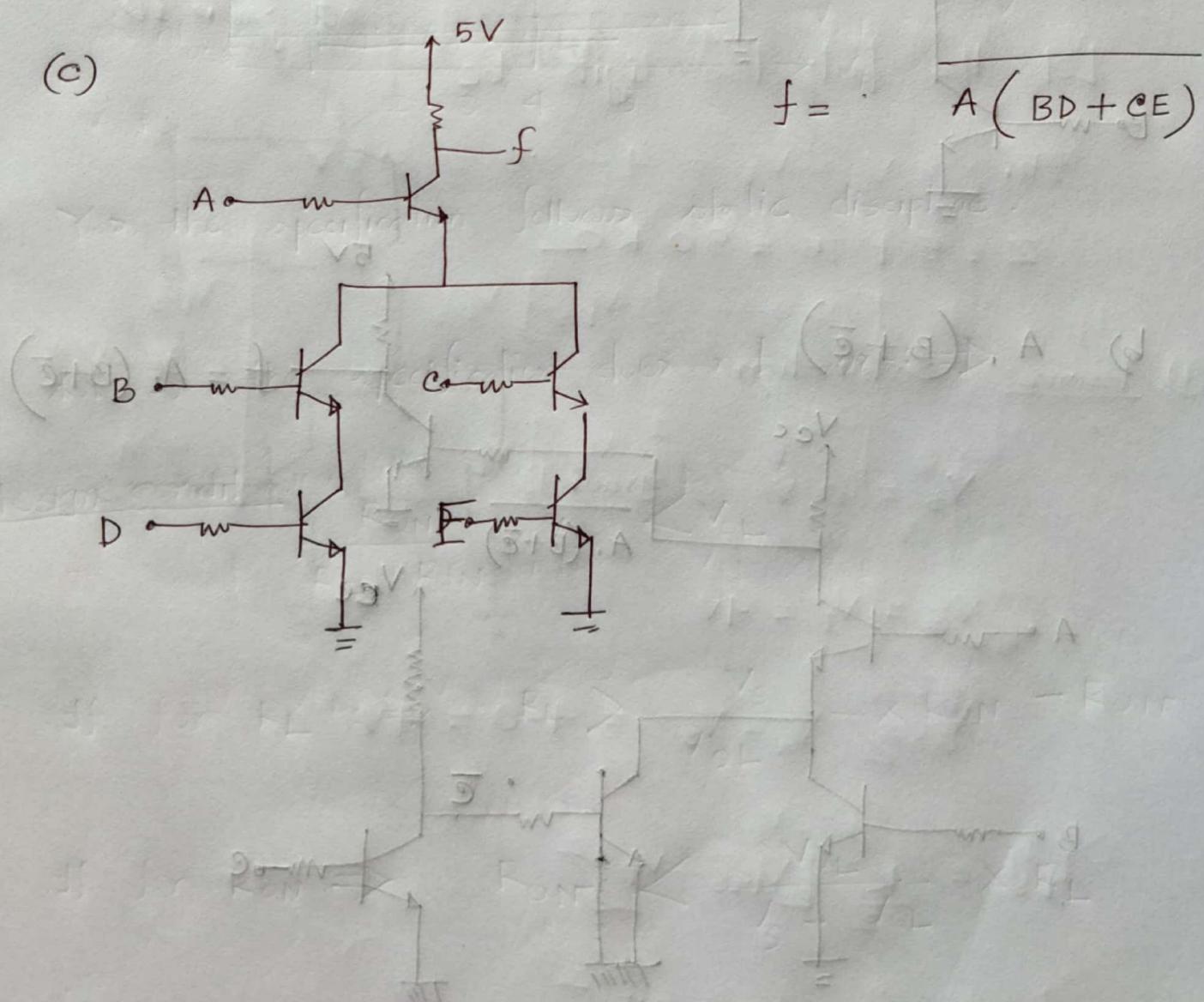


$$f = \overline{A(BD + CE)}$$

8. a)  $f = A \cdot B + C$

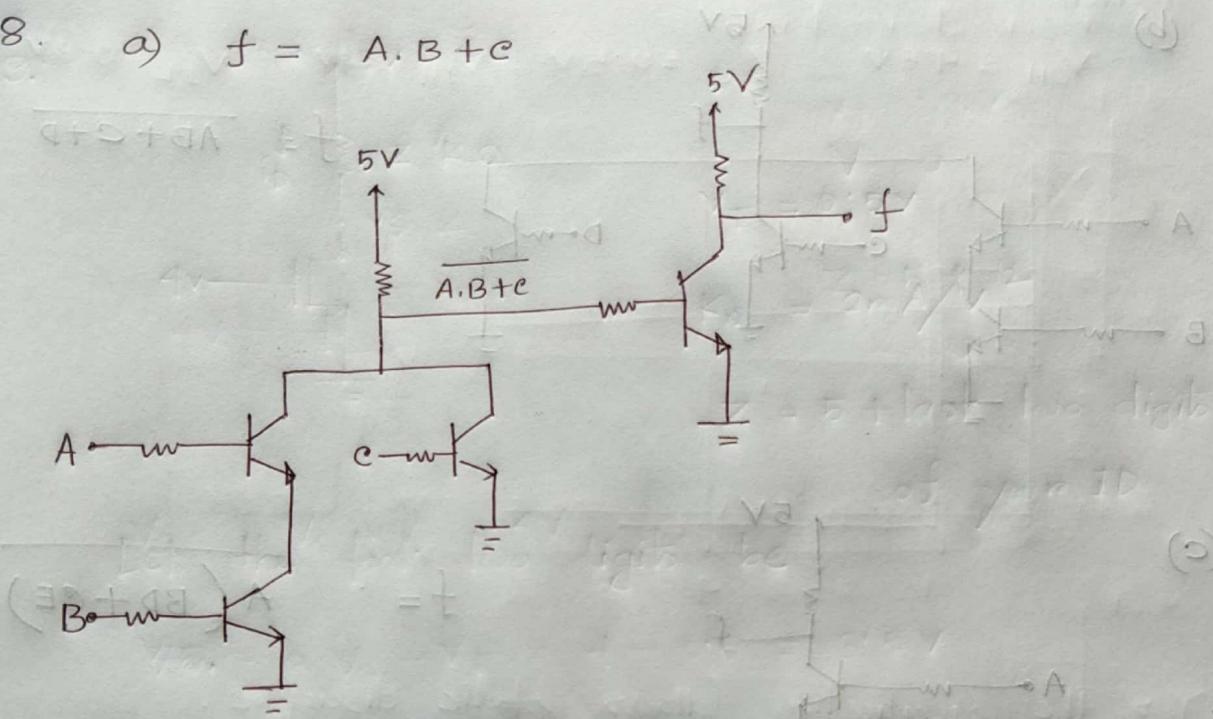



b)  $f = A \cdot (B + \bar{C})$

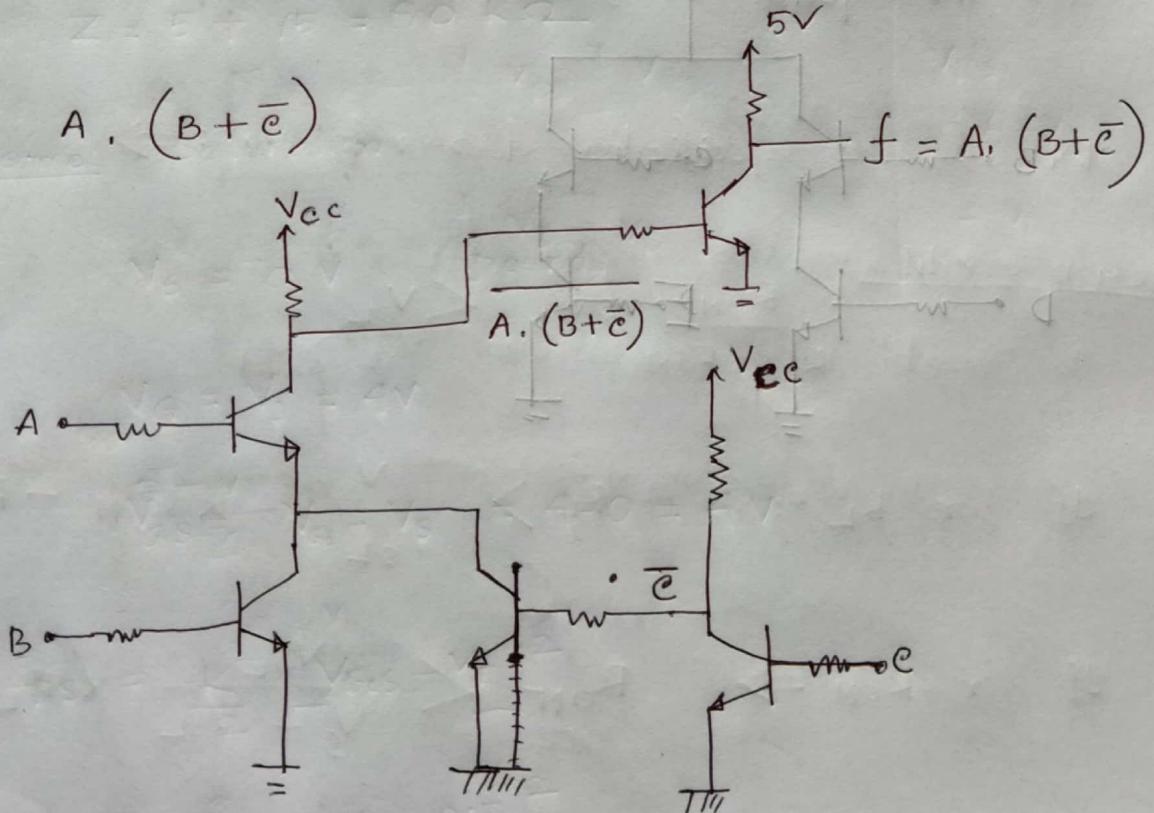

$$c) f = \overline{\overline{AB}} + \overline{\overline{C+D}}$$

$$= \overline{\overline{AB}} \cdot \overline{\overline{C+D}}$$

$$= AB(C+D)$$

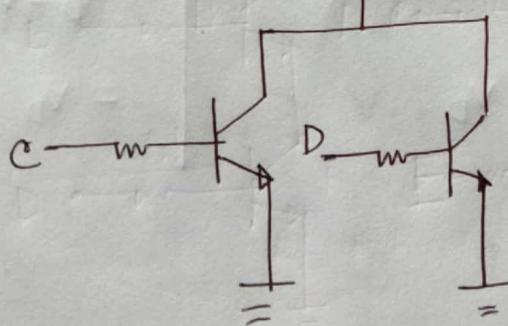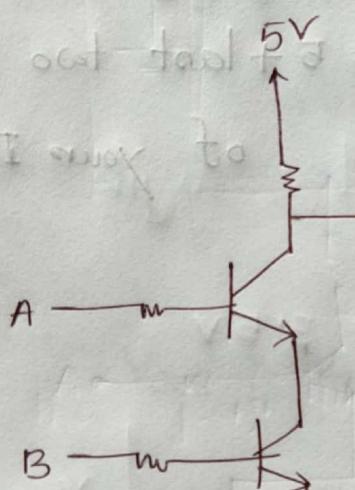

$$\overline{AB(C+D)}$$

5V

$$f = AB(C+D)$$



$$V_{BE} = 0.7V$$


$$V_B = V = 5V$$

$$V_P = 0 - 0.7V = 0V - 0.7V = -0.7V$$

$$[5V - 0.7V] \cdot \frac{1}{2} = 2.1V$$

$$[5V - 0] \cdot \frac{1}{2} = 2.5V$$

9.

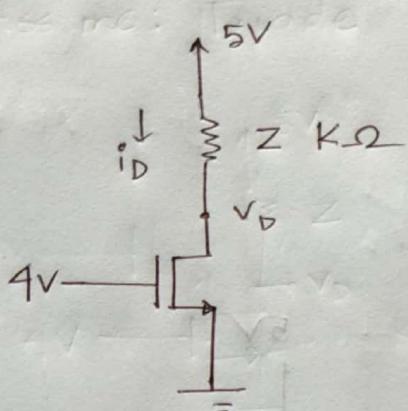

$$\frac{4+5}{4+5+2k} = \frac{9}{11+2k}$$

$$V_T = 0.5V$$

$$K_n = 2mA/V^2$$

$Z = 5 + \text{last two digits}$   
of yours ID

Let the last two digits be

75.

$$\therefore Z = 5 + 75 = 80 k\Omega$$

① Assume: Saturation

$$V_S = 0V \quad (\text{ground})$$

$$V_G = V_I = 4V$$

$$V_{GS} = V_G - V_S = 4 - 0 = 4V$$

$$I_{DS} = \frac{k}{2} [V_{GS} - V_T]^2$$

$$= \frac{2}{2} [4 - 0.5]^2$$

$$= 12.25 mA$$

$$I_{DS} = \frac{5 - V_D}{Z}$$

$$\Rightarrow 12.25 = \frac{5 - V_D}{80}$$

$$\Rightarrow V_D = 5 - 80 \times 12.25 \\ = -975 \text{ V}$$

$$V_{DS} = V_D - V_S = -975 - 0 = -975 \text{ V}$$

Verify:

$$V_{GS} \geq V_T$$


$$\Rightarrow 4 > 0.5 \text{ V}$$

$$4 - V_{DS} \geq V_{GS} + V_T$$

$$\Rightarrow -975 \neq 4 - 0.5$$

$\therefore$  Assumption wrong

(11) Assume: Triode.

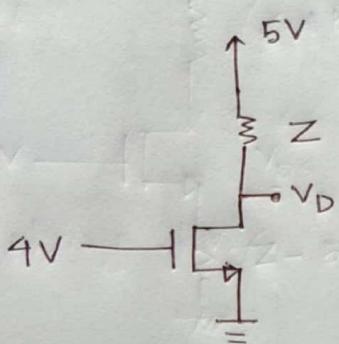

$$V_T = 0.5V$$

$$V_S = 0$$

$$Z = 5 + 75$$

$$V_{GS} = V_G - V_S = 4V$$

$$V_{OV} = V_G - V_T = 4 - 0.5 = 3.5V$$

$$I_{DS} = k \left[ V_{OV} - \frac{1}{2} V_{DS} \right] V_{DS}$$

$V_{DS} = V_D - V_S$

$$= 2 \left[ 3.5 - \frac{1}{2} V_D \right] V_D$$

$V_D = V_D$

$$I_{DS} = \frac{5 - V_D}{Z}$$

$$\Rightarrow I_{DS} = \frac{5 - V_D}{80}$$

$$\Rightarrow V_D = 5 - (I_{DS}) \times 80$$

$$\Rightarrow V_D = 5 - 2 \left[ 3.5 - \frac{1}{2}V_D \right] V_D \times 80$$

$$\Rightarrow V_D = 5 - 560 V_D + 80 V_D^2$$

$$\Rightarrow 80 V_D^2 - V_D - 560 V_D + 5 = 0$$

$$\Rightarrow 80 V_D^2 - 561 V_D + 5 = 0$$

Verify:

$$\Rightarrow V_D = 7.02 V$$

$$= 0.009 V$$

Taking the smaller root  $V_D = 0.009 V$

Verify:  $V_{GS} \geq V_T$


$$\Rightarrow 4V > 0.5V$$

$$V_{DS} < V_{GS} - V_T$$


$$\Rightarrow 0.009 < 3.5 V$$

$\therefore$  Assumption right

10.

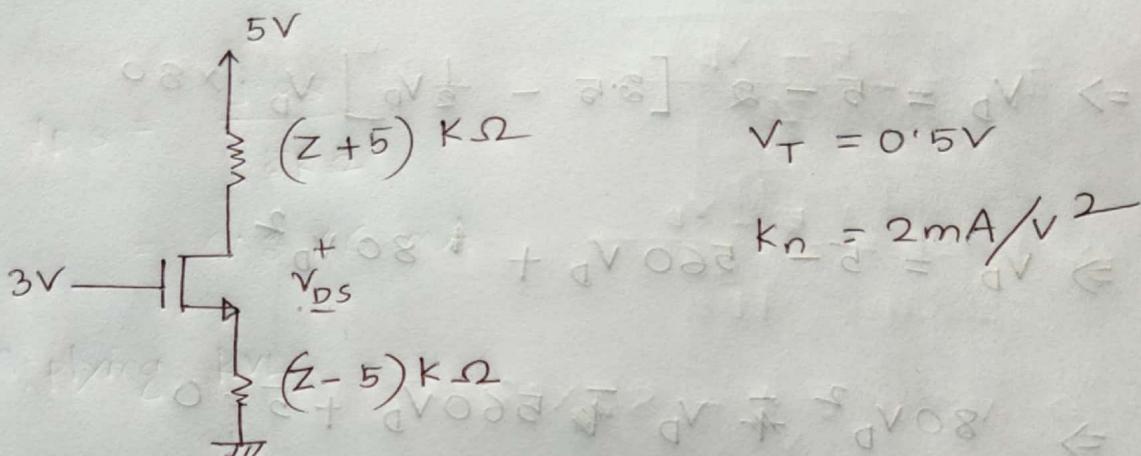
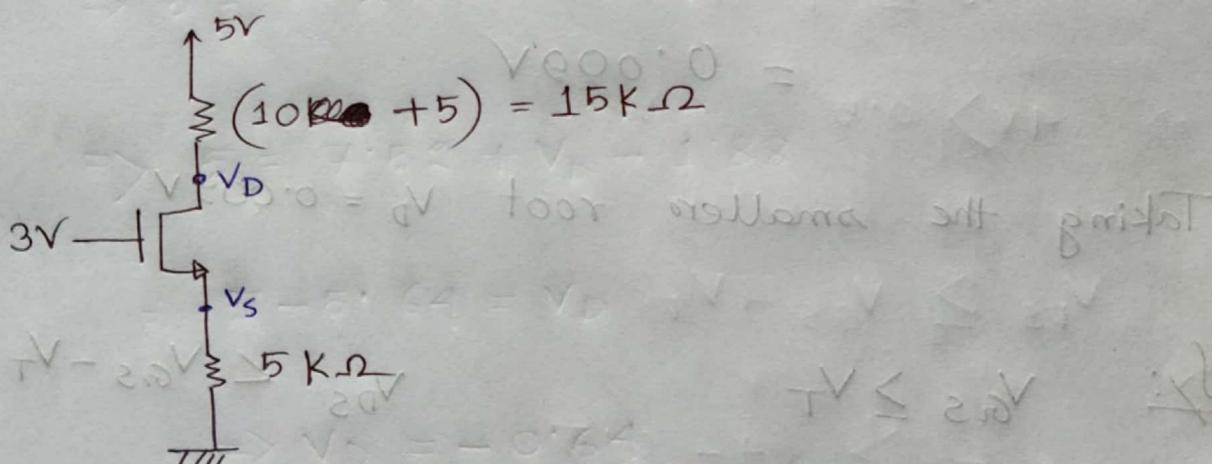
$$Z = 5 + 05 \rightarrow \text{last two digits} \\ = 10 \text{ k}\Omega$$



Assume: Saturation

$$V_{GS} = V_G - V_S$$

$$= 3 - \sqrt{s}$$

$$I_{DS} = \frac{k}{2} [V_{GS} - V_T]^2$$

$$= \frac{2}{2} [3 - V_S - 0.5]^2$$

$$= [2.5 - V_S]^2$$

$$I_{DS} = \frac{V_S - 0}{5}$$

$$\Rightarrow V_S = I_{DS} \times 5$$

$$\Rightarrow V_S = [2.5 - V_S]^2 \times 5$$

$$\Rightarrow V_S = [6.25 - 5V_S + V_S^2]^5$$

$$\Rightarrow V_S = 31.25 - 25V_S + 5V_S^2$$

$$\Rightarrow V_S + 5V_S^2 + 25V_S + 31.25 = 0$$

$$\Rightarrow 5V_S^2 + 26V_S + 31.25 = 0$$

$$\therefore V_S = 3.31V$$

$1.88V$

smaller root

$$\therefore I_{DS} = \frac{1.88}{5k\Omega}$$

$$= 0.376 \text{ mA}$$

Applying KVL

$$5 = 15 \times I_{DS} + V_{DS} + 5 \times I_{DS} - 1.88$$

$$\Rightarrow 5 = 20 I_{DS} + V_D - V_S$$

$$\Rightarrow 5 = 20 \times 0.376 + V_D - 1.88$$

$$\Rightarrow 5 = 7.52 + V_D - 1.88$$

$$\Rightarrow 5 - 5.64 = V_D$$

$$\Rightarrow V_D = -0.64$$

$$\therefore V_{DS} = V_D - V_S = -0.64 - 1.88$$

$$= -2.52$$

answ  
book

$$V_{DS} = -2.52$$

Verify:

$$V_{GS} > V_T$$

$$V_{DS} \geq V_{GS} - V_T$$

$$\Rightarrow V_G - V_S > V_T$$

$$\Rightarrow -2.52 \not> 1.12 - 0.5$$


$$\Rightarrow 3 - 1.88 > 0.5$$

X

$$\Rightarrow 1.12 > 0.5 \checkmark$$

∴ Assumption wrong

11.

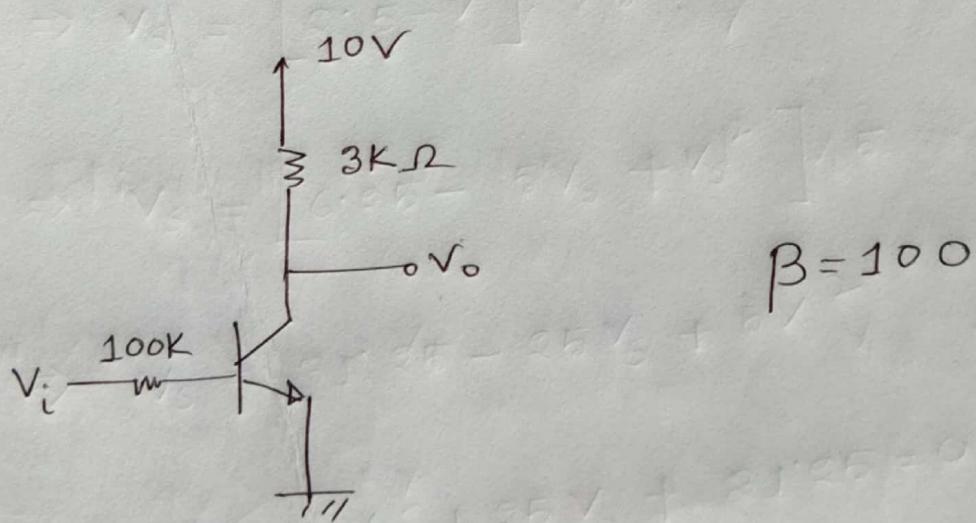

①  $V_i = 1V$

Assume: Active

$$V_B - V_E = 0.7 \text{ V}$$
$$V_{BE} = 0.7 \text{ V}$$
$$I_C = \beta I_B$$

$$V_{BE} = 0.7$$

$$\Rightarrow V_B - V_E = 0.7$$

$$\Rightarrow V_B = 0.7$$

$$I_B = \frac{V_i - V_B}{R_B} = \frac{10 - 0.7}{100} = 0.003 \text{ mA}$$

$$I_C = \beta I_B$$

$$= 100 \times 0.003$$

$$= 0.3 \text{ mA}$$

$$I_C = \frac{V_{CE} - V_C}{R_C} = \frac{10 - V_C}{3}$$

$$\Rightarrow V_C = 9.1 \text{ V}$$

$$I_E = I_C + I_B = 0.3 + 0.003 = 0.303 \text{ mA}$$


Verify:

$$\begin{aligned}V_{CE} &= V_C - V_E \\&= 9.1 - 0 \\&= 9.1\end{aligned}$$

$$V_{CE} > 0.2V$$

∴ Assumption right

⑪  $V_i = 5V$

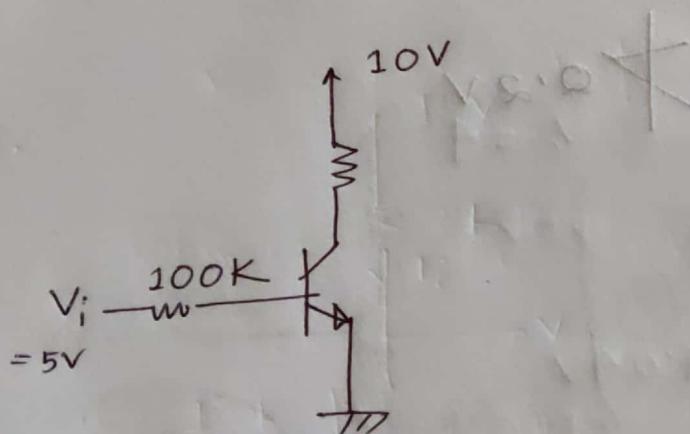

Assume: Active

$$V_{BE} = 0.7V$$

$$\Rightarrow V_B = 0.7V$$

$$I_B = \frac{V_i - V_B}{R_B}$$

$$= \frac{5 - 0.7}{100}$$

$$= 0.043mA$$

$$I_c = \beta I_B$$

$$= 100 \times 0.043$$

$$= 4.3 \text{ mA}$$

$$I_c = \frac{10 - V_C}{3}$$

$$\Rightarrow V_C = -2.9 \text{ V}$$

Verify:  $V_{CE} = V_C - V_E$

$$= -2.9 \text{ V} \neq 2.2 \text{ V}$$

$\therefore$  Assumption wrong

Assume: Saturation

$$V_{BE} = 0.8 \text{ V}$$

$$V_{CE} = 0.2 \text{ V}$$

$$V_{BE} = 0.8$$

$$\Rightarrow V_B = 0.8$$

$$V_{CE} = 0.2$$

$$\Rightarrow V_C = 0.2 \text{ V} = V_0$$


$$I_B = \frac{5 - 0.8}{100} = 0.042 \text{ mA}$$

$$I_C = \frac{10 - V_E}{R_C} = \frac{10 - 9.8}{3} = \frac{0.2}{3} = 0.067 \text{ mA}$$

$$\frac{I_C}{I_B} = \frac{0.067}{0.042} = 1.59 < \beta$$

Assumption right.

12.

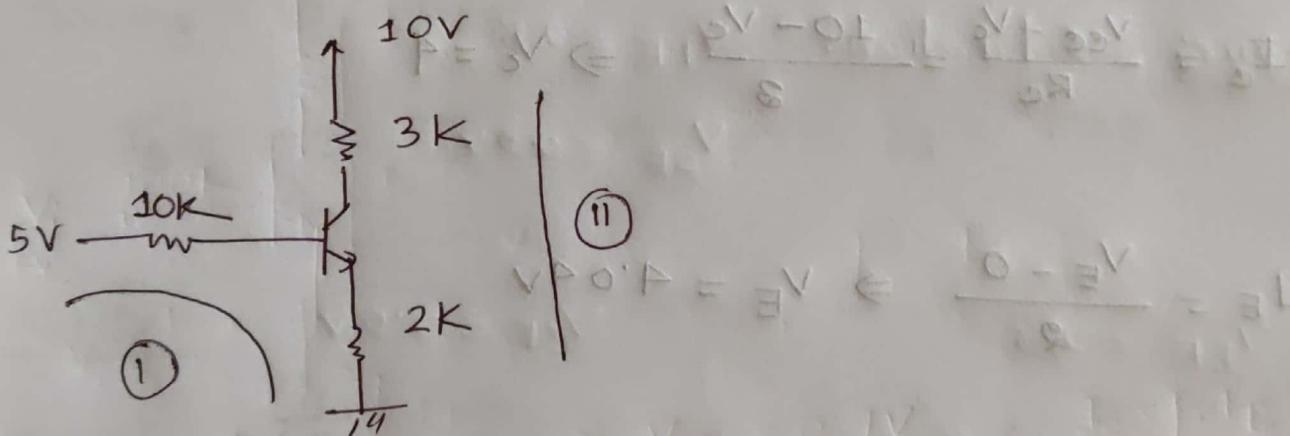

Assume: Active  $\rightarrow V_{BE} = 0.7 \text{ V}$

$$I_C = \beta I_B \quad \text{--- (1)}$$

$$I_C = \alpha I_E \quad \text{--- (2)}$$

① ÷ ②

$$I_E = \frac{\beta}{\alpha} I_B$$

KVL  $\rightarrow$  ① line

$$5 = 10I_B + 0.7 + 2I_E$$

$$\Rightarrow 5 = 10I_B + 0.7 + 2\frac{\beta}{2}I_B$$

$$\Rightarrow I_B = 0.02 \text{ mA}$$

$$I_C = \beta I_B = 100 \times 0.02 = 2 \text{ mA}$$

$$I_E = I_C + I_B = 2.02 \text{ mA}$$

$$I_C = \frac{V_{EE} - V_C}{R_C} = \frac{10 - V_C}{3} \Rightarrow V_C = 9$$

$$I_E = \frac{V_E - 0}{2} \Rightarrow V_E = 4.09 \text{ V}$$

$$\therefore V_{CE} = V_C - V_E$$

$$= 4 - 4.09$$

$$= -0.09$$

∴ wrong

Assume: Saturation:  $V_{BE} = 0.8V$   $V_{CE} = 0.2V$

$$KCL: I_E = I_C + I_B \quad \text{--- (1)}$$

$$KVL \text{ Line (1): } 5 = 10I_B + V_{BE} + 2I_E$$

$$= 10I_B + 0.8 + 2I_E \quad \text{--- (2)}$$

$$\text{line (2): } 10 = 3I_C + 0.2V_{CE} + 2I_E$$

$$= 3I_C + 0.2 + 2I_E \quad \text{--- (3)}$$

Solving (1), (2), (3)

$$I_B = 0.03 \quad I_C = 1.95 \quad I_E = 1.98$$


Verify:

$$\frac{I_C}{I_B} < \beta$$

$$\Rightarrow \frac{1.95}{0.03} < \beta$$

$$\Rightarrow 65 < 100$$

$\therefore$  right

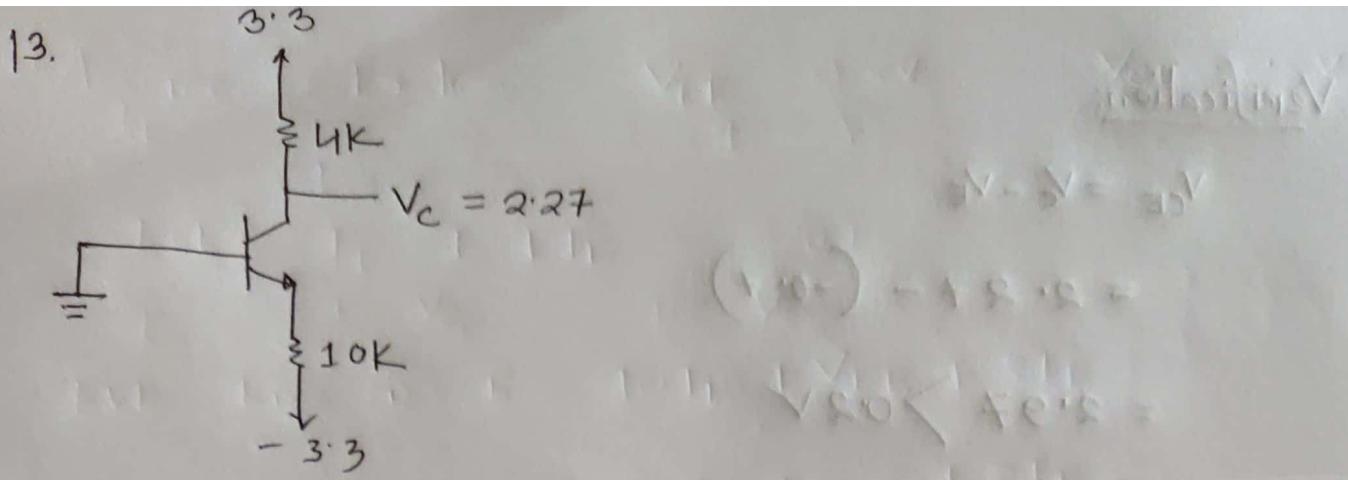

Assume: Active

$$V_{BE} = 0.7$$

$$I_C = \beta I_B$$

$$I_C = \alpha I_E$$

$$I_C = \frac{3.3 - 2.27}{4} = 0.257$$

$$V_{BE} = 0.7 \Rightarrow V_E = -0.7$$

$$I_E = \frac{-0.7 - (-3.3)}{10} = 0.26$$

$$I_B = I_E - I_C = 0.26 - 0.257 = 0.0025 \text{ mA}$$

$$\beta = \frac{I_C}{I_B} = 103$$

$$\alpha = \frac{I_C}{I_E} = 0.99$$

Verification:

$$\begin{aligned}V_{CE} &= V_C - V_E \\&= 2.27 - (-0.7) \\&= 2.97 > 0.2 \text{ V}\end{aligned}$$

$\therefore$  right