

⇒ Superposition ⇐

Am no.1

### Superposition Principle:

According to superposition principle, if there are more than one voltage or current source in a circuit, ~~the~~ each voltage or current source will act independently and then the sum of it and the current to it will give us the voltage drop across each components. Here, each sub-circuit will have only one independent source. This principle won't be valid for power because it supports linear quantity ~~at~~ while power is a non-linear quantity.

Am no.2

"For the superposition principle method, some sources have to be ON and some have to be off

while performing nodal analysis."

Here, in this technique, in a circuit we turn off all the voltage and

current source except one, and then perform



Here, solving the equations,

$$V_2 = 21.569 \text{ V}$$


$$V_3 = 15.686 \text{ V}$$

$$V_4 = 11.765 \text{ V}$$

$$\therefore V_{01} = V_2 - V_3 = 5.883 \text{ V}$$

Am no. 9

Here, keep  $I = 20 \text{ A}$  active,

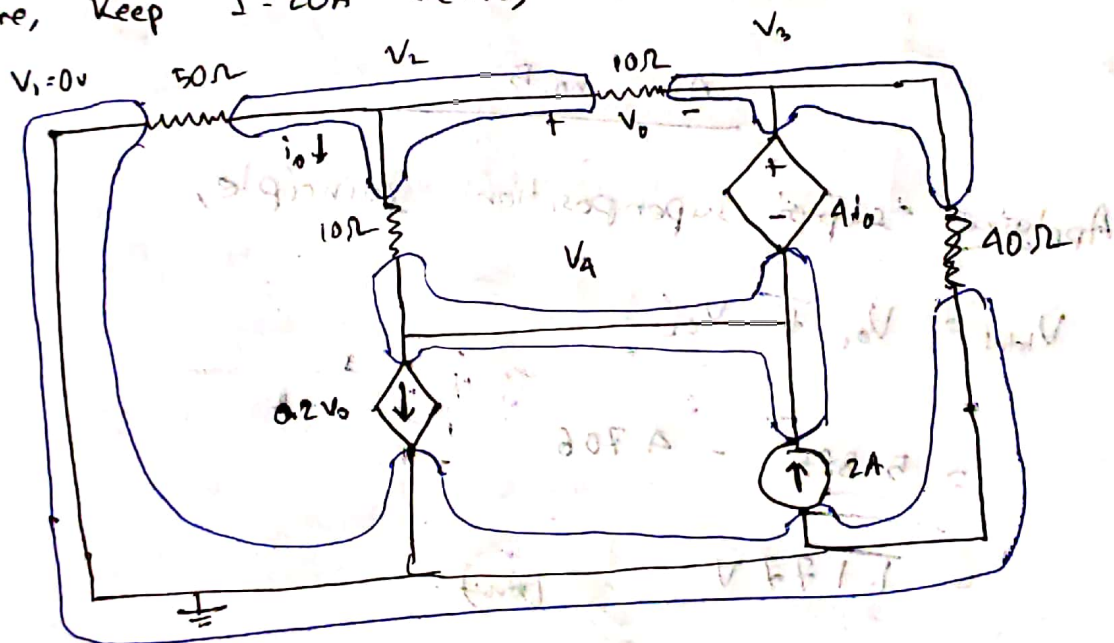

Here,  $V_0 = V_2 - V_3$

$$V_3 - V_4 = 4 \left( \frac{V_2 - V_4}{10} \right)$$

or,  $10V_3 - 6V_4 - 4V_2 = 0 \quad (1)$

$$V_2 \left( \frac{1}{50} + \frac{1}{10} + \frac{1}{10} \right) - \frac{V_3}{10} - \frac{V_4}{10} = 0 \quad (11)$$

$$V_3 \left( \frac{1}{10} + \frac{1}{40} \right) - \frac{V_2}{10} + \frac{V_4}{10} - \frac{V_2}{10} + 0.2(V_2 - V_3) - 2 = 0 \quad (11)$$

$\therefore V_1 = 0 \text{ V}$  [Ground]



Solving the following equation,

$$V_1 = 0$$

$$V_2 = 62.745 \text{ V}$$

$$V_3 = 67.451$$

$$V_A = 70.538 \text{ V}$$

Now,

$$\therefore V_{02} = V_2 - V_3$$

$$= -4.706 \text{ V}$$


Applying ~~supp~~ superposition principle,

$$V_{\text{total}} = V_{01} + V_{02}$$

$$= 5.883 - 4.706$$

$$= 1.177 \text{ V}$$

(Ans)

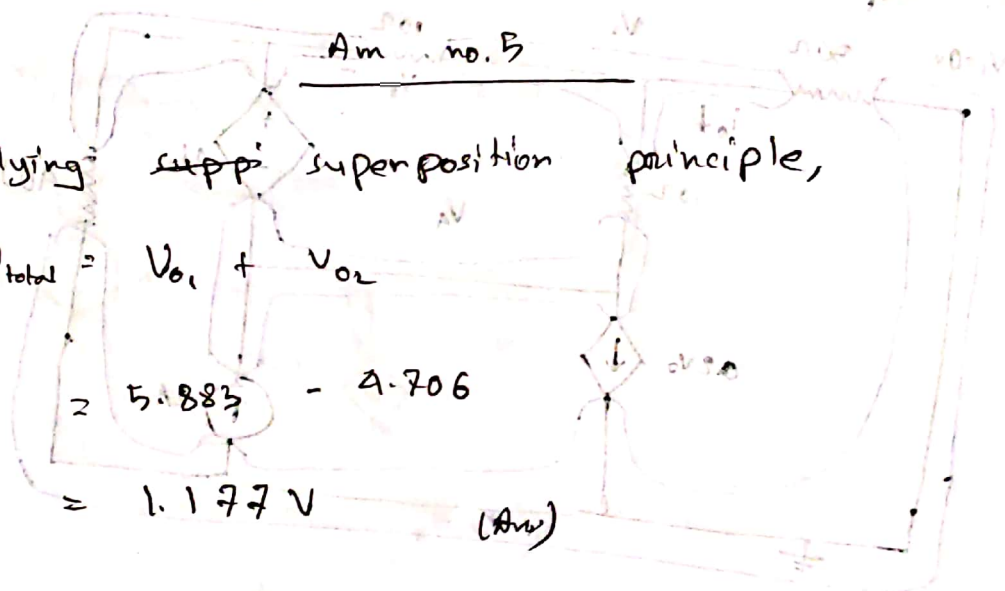

$$\left( \frac{10 \text{ V} - 20 \text{ V}}{10} \right) \text{ A} = 1 \text{ A} - 2 \text{ A}$$

$$(1) - 0 = 20 \text{ V} - 10 \text{ V} - 20 \text{ V} + 10 \text{ V} = 0$$


$$\frac{10 \text{ V}}{10} - \frac{20 \text{ V}}{10} = \left( \frac{1}{10} - \frac{1}{10} + \frac{1}{10} \right) 20 \text{ V}$$

$$\frac{10 \text{ V}}{10} - \frac{20 \text{ V}}{10} = \left( \frac{1}{10} - \frac{1}{10} + \frac{1}{10} \right) 20 \text{ V}$$


[Answer]

# ⇒ Transient Analysis ⇐


Ans. no. 1

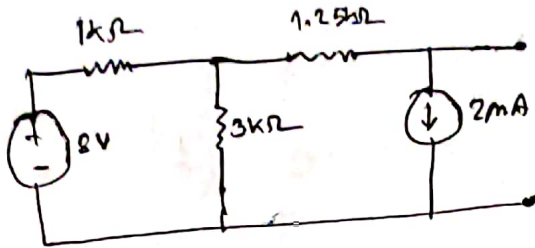


i)

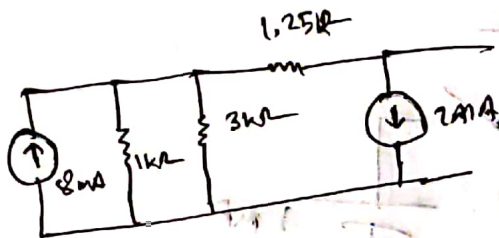


ii)



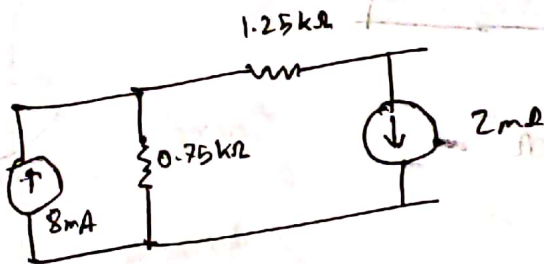


iii)

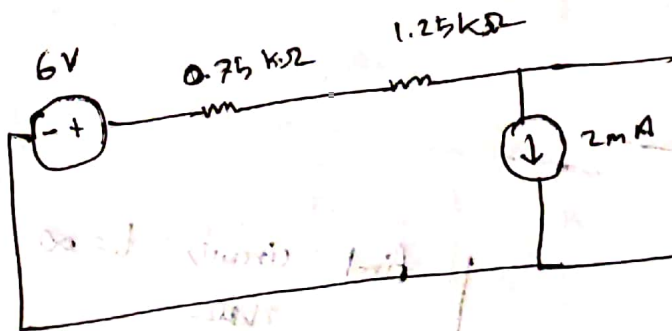

iv)

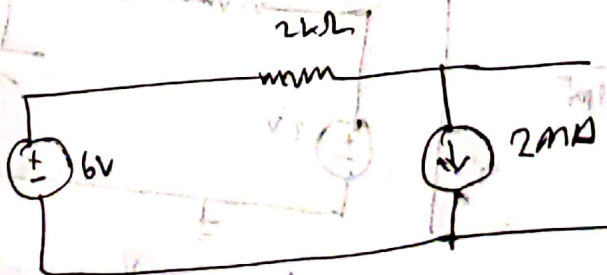

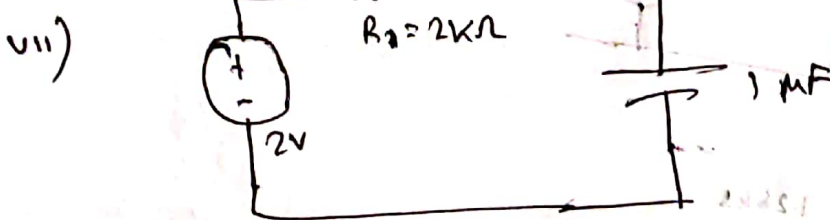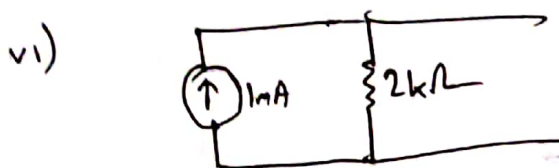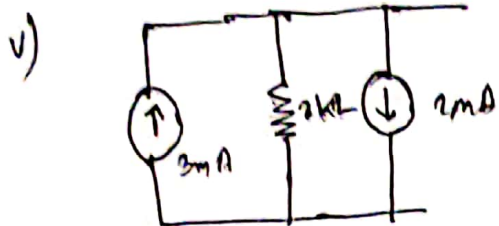


$\therefore V_1 = 2V, R_1 = 2k\Omega$

Now,

at  $t=0$ ,


Hence,

Initial circuit,  $t=0$

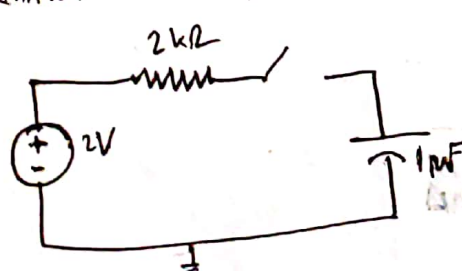

$i_0 = \frac{V_1}{R_1} = 1mA$


final circuit,  $t=\infty$

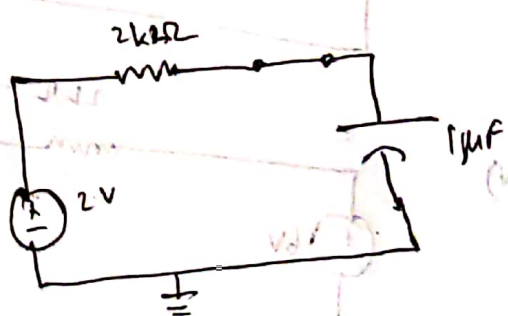

$i_{\infty} = 0mA$


Now, [ ]
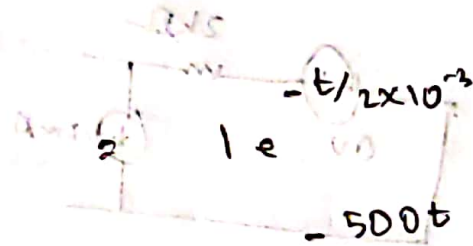
$$i(t) = 0 + (1 - 0)e^{-t/2 \times 10^{-3}}$$





$$= 1e^{-t/2 \times 10^{-3}}$$

(Am.)

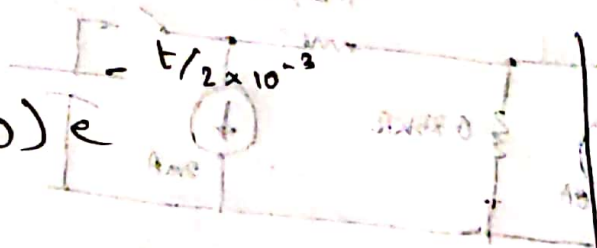

Hence,



$$\tau = RC = 2 \times 10^{-3}$$

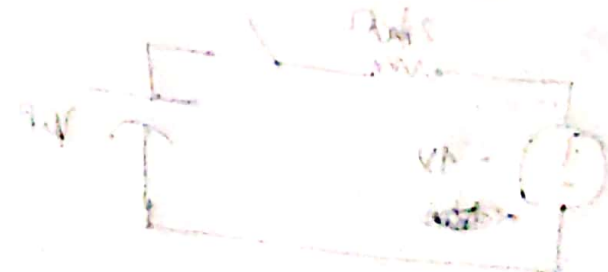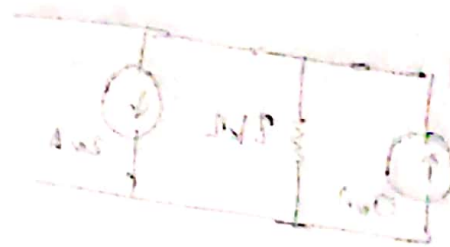







Am no. 2

Driver

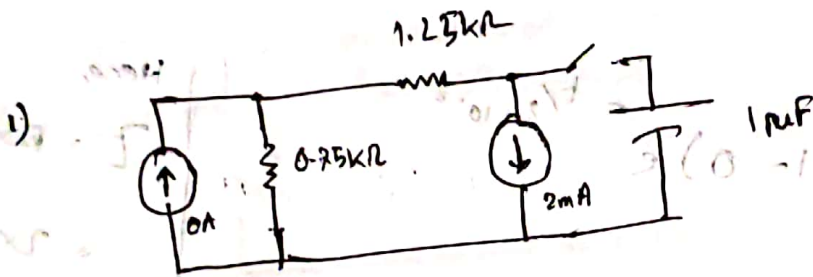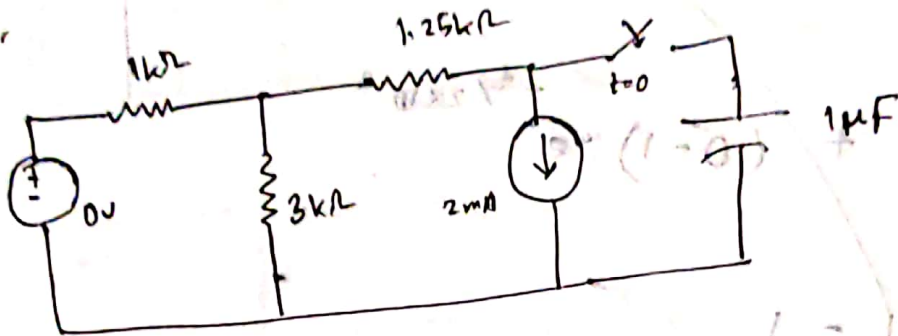

$1k\Omega$  &  $3k\Omega$  parallel

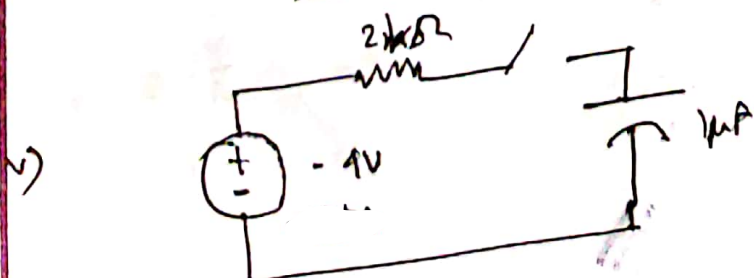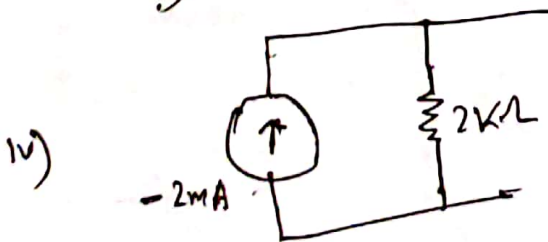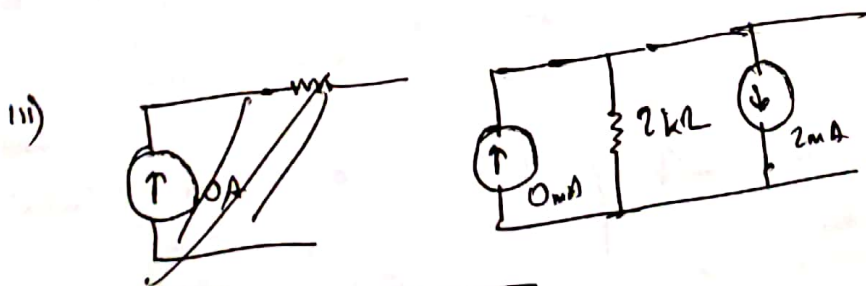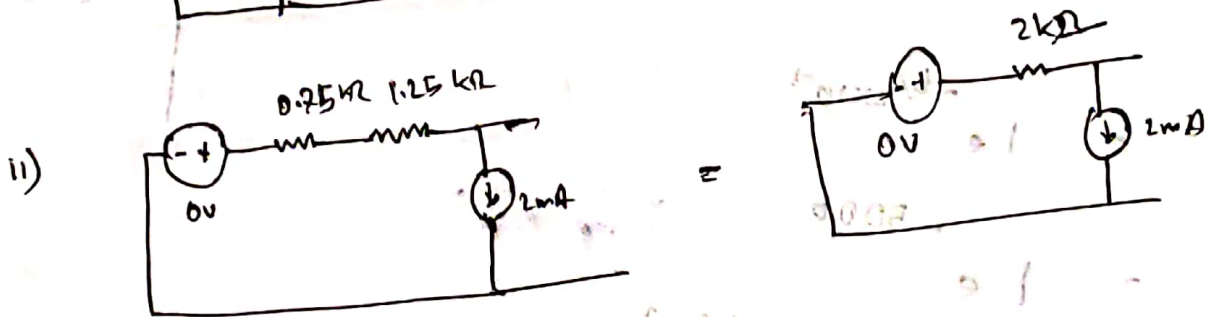




Now,


Initial circuit,

$t = 0$

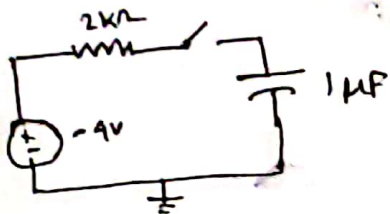

$$i_0 = -2 \text{ mA}$$

Final circuit,

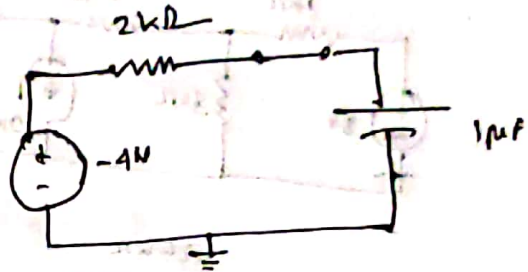

$$i_\infty = 0 \text{ mA}$$

$$\tau = R \times C = 2 \times 10^{-3} \text{ s}$$

Here,

$$i_c(t) = i_\infty + (i_0 - i_\infty) e^{-t/\tau}$$

$$= 0 + (-2 - 0) e^{-500t}$$





$$= -2 e^{-500t}$$


Am no. 13

P.T.O

Ans no. 3


Given,

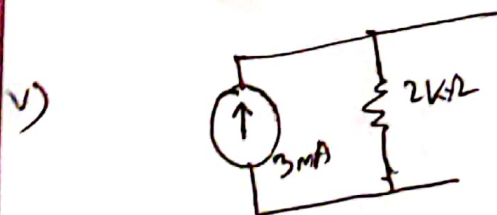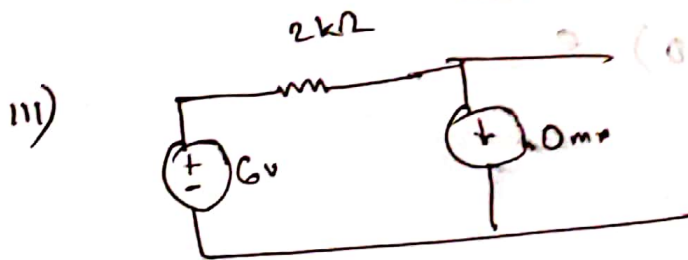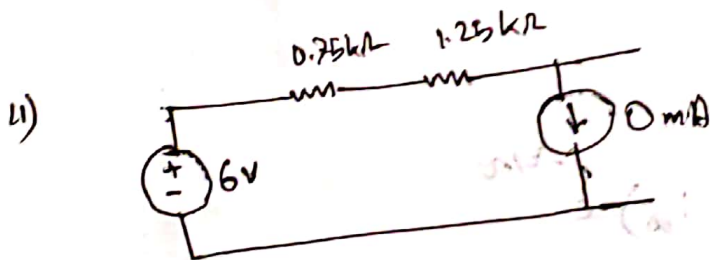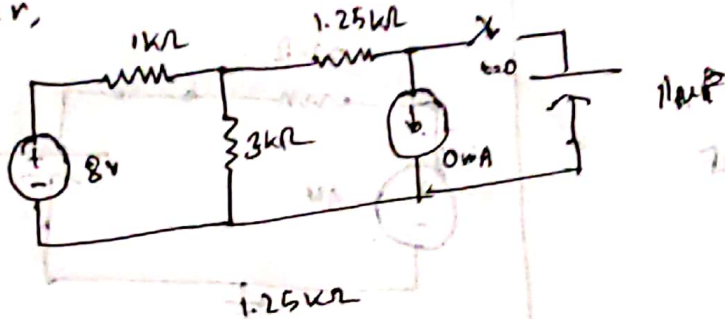

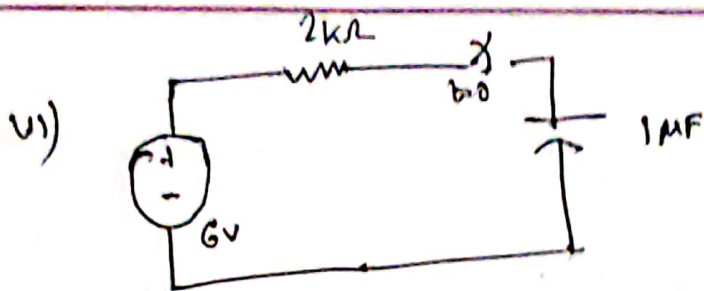

Now

Initial circuit,  $t = 0^+$

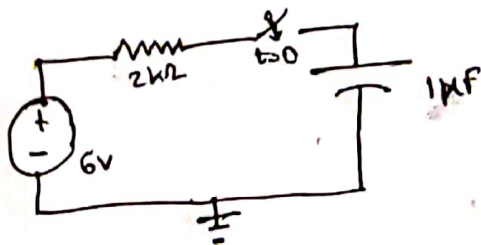

$$i_0 = 3 \text{ mA}$$

Now  $\tau = R \times C = 2 \times 10^{-3}$

Let


$$\begin{aligned}
 \text{Now,} \\
 i_{c2}(t) &= i_{\infty} + (i_0 - i_{\infty}) e^{-t/\tau} \\
 &= 0 + (3 - 0) e^{-500t} \\
 &= 3 e^{-500t}
 \end{aligned}$$

Am no 4

$$\begin{aligned}
 i_c(t) &= i_{c1}(t) + i_{c2}(t) \\
 &= -2e^{-500t} + 3e^{-500t} \\
 &= 1e^{-500t} = i_{c1}(t) + i_{c2}(t)
 \end{aligned}$$

∴ Superposition principle is working for the circuit.

Final circuit,  $t = \infty$

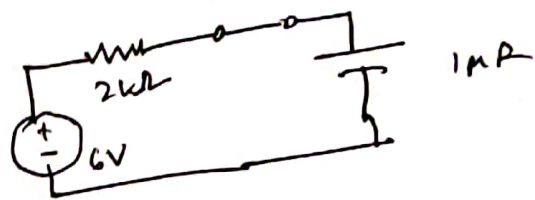

$$i_{\infty} = 0 \text{ mA}$$