

CSE 250

Lab-02

Husne Mubarak

Section: CSE09

ID: 20101336


## Experiment 2:


Name of the experiment: Introduction to series and parallel circuits

Objective: The experiment is to acquaint the students with series-parallel circuits and to give them the idea about how to connect different circuits in breadboard.

Apparatus: DC voltage source, resistors, multimeter

Procedure:

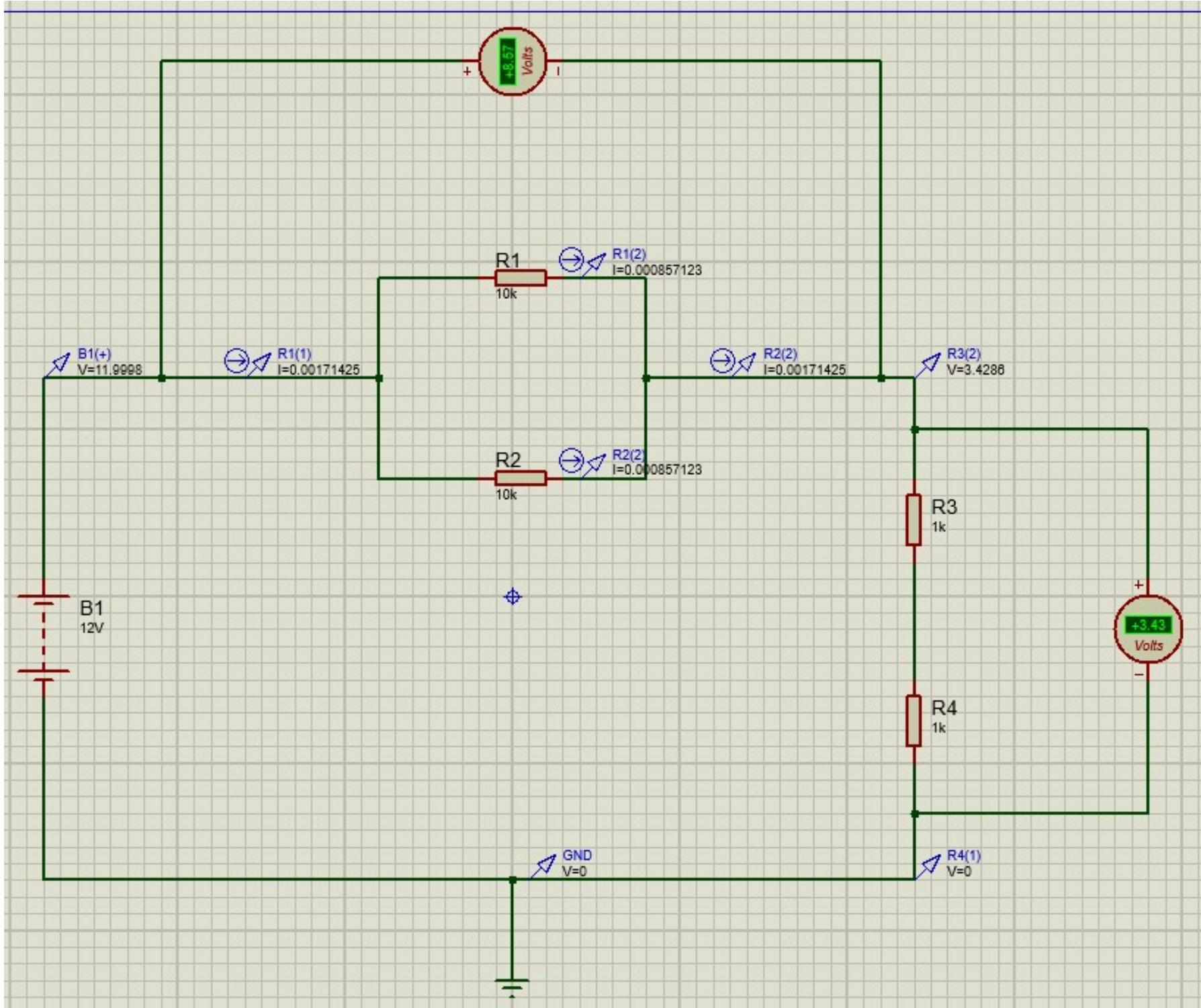

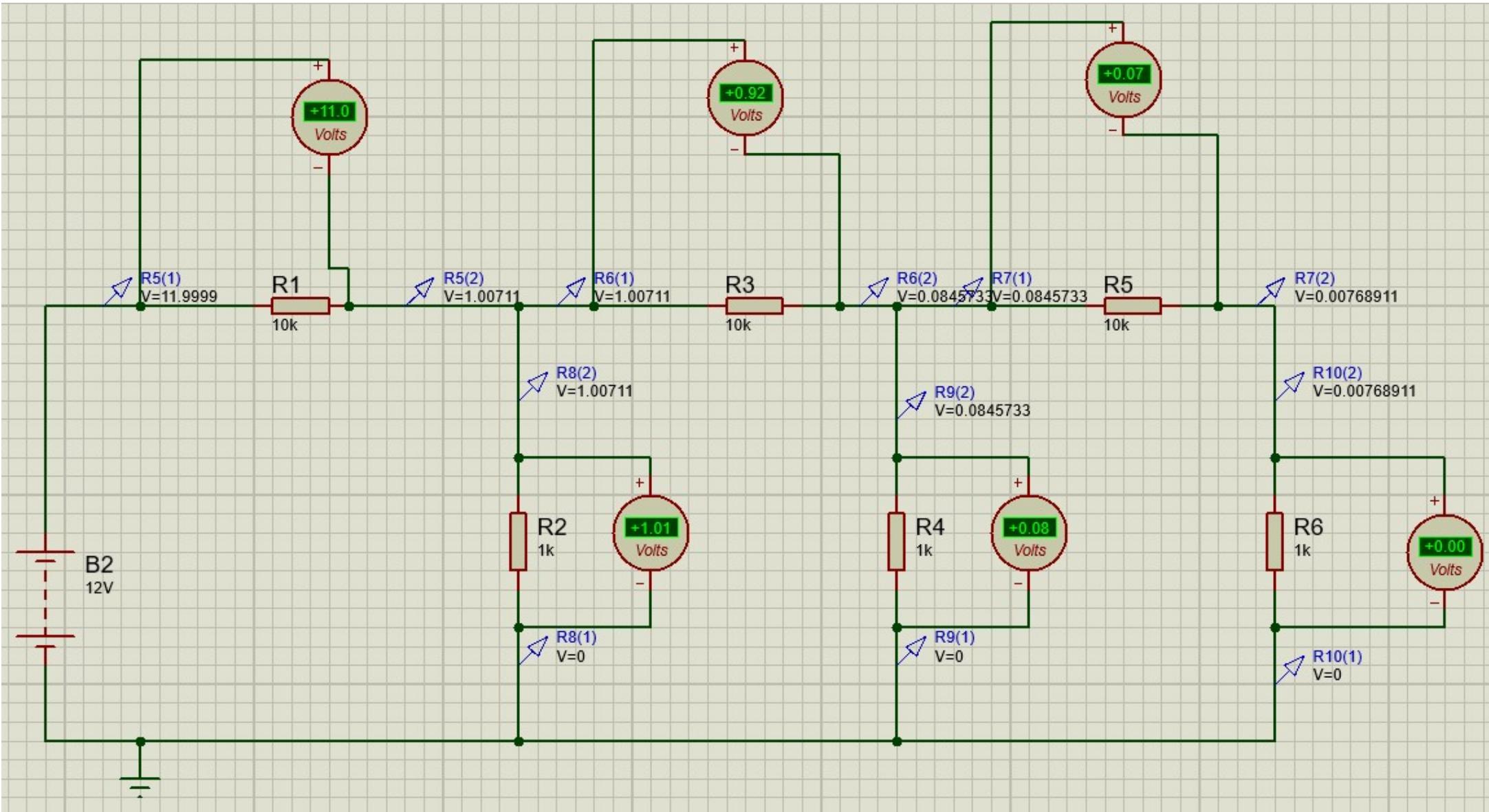

# Reports:

## For circuit 1:

$$V = 12 \text{ V}$$

$$R_1 = 10 \text{ k} \Omega$$

$$R_2 = 10 \text{ k} \Omega$$

$$R_B = 1 \text{ k} \Omega$$

$$R_4 = 1 \text{ k} \Omega$$

$V_1$	$V_2$	$V_1 + V_2 = V$	$I_1$	$I_2$	$I_1 + I_2 = I$
8.57 V	3.43 V	12 V	$857123 \times 10^{-9}$	$857123 \times 10^{-9}$	$1714246 \times 10^{-9}$

~~4th question~~  
For circuit 2:

$$V = 12V$$

$$R_1 = 10K\Omega = 10000 \text{ ohm}$$

$$R_2 = 1K\Omega = 1000 \text{ ohm}$$

$$R_3 = 10K\Omega = 10000 \text{ ohm}$$

$$R_4 = 1K\Omega = 1000 \text{ ohm}$$

$$R_5 = 10K\Omega = 10000 \text{ ohm}$$

$$R_6 = 1K\Omega = 1000 \text{ ohm}$$

$V_1$	$V_2$	$V_B$	$V_4$	$V_5$	$V_6$	$I_1(A)$	$I_2(A)$	$I_3(A)$	$I_4(A)$	$I_5(A)$	$I_6(A)$
11V	1.01	0.92	0.08	0.07	0.007	$2.2 \times 10^{-5}$	$1.0 \times 10^{-5}$	$2.2 \times 10^{-6}$	$8.0 \times 10^{-6}$	$4.7 \times 10^{-6}$	$4.7 \times 10^{-6}$

One of the discrepancies are that from the circuit, the value measured using multimeter is 13.087V but initially the value of the DC cell source is 12V. This happened during the partial errors during the calculation.

### Question:

1. The instruments using in circuit 1 are:

$$V=12V$$

$$R_1 = 10k\Omega$$

$$R_2 = 10k\Omega$$

$$R_3 = 1k\Omega$$

$$R_4 = 1k\Omega$$

$$R_P = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$= (1/10)^{-1} k\Omega = 5k\Omega$$

$$R_{eq} = R_P + R_3 + R_4$$

$$= 5 + 1 + 1 = 7k\Omega = 7000 \text{ ohm}$$

$$I = \frac{V}{R}$$

$$= \frac{12}{7000} = 1714285714 \times 10^{-12} \text{ A}$$

The instrument used in circuit - 2

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 1 \text{ k}\Omega$$

$$R_3 = 10 \text{ k}\Omega$$

$$R_4 = 1 \text{ k}\Omega$$

$$R_5 = 10 \text{ k}\Omega$$

$$R_6 = 1 \text{ k}\Omega$$

$$V = 12 \text{ V}$$

$$R_{PA} = (R_5 + R_6)$$

$$R_{PA} = 11 \text{ k}\Omega$$

$$R_{PB} = \left( \frac{1}{R_{PA}} + \frac{1}{R_4} \right)^{-1}$$

$$= 11/12 \text{ k}\Omega$$

$$R_{Pc} = (R_3 + R_{Pb})$$

$$= 10 + 1/12 \Omega = \frac{131}{12} \Omega$$

$$R_{Pd} = \left( \frac{1}{R_{Pc}} + \frac{1}{R_2} \right)^{-1}$$

$$= \left( \frac{12}{131} + 1 \right)^{-1}$$

$$= \frac{131}{143} \text{ k}\Omega$$

$$Req = (R_1 + R_{Pd}) \text{ k}\Omega$$

$$= \left( 10 + \frac{131}{143} \right) \text{ k}\Omega$$


$$= \frac{1561}{143} \text{ k}\Omega = 10916.08392 \text{ }\Omega$$

$$I = \frac{V}{Req} = \frac{12}{10916.08392} \text{ A}$$

$$= 1.099295323 \times 10^{-3} \text{ A}$$

By calculating, the current ~~ment~~  
 calculated by Ohm's law which  
 is  $V = IR$  is similar to values  
 obtained by the multimeter in the  
 circuit.

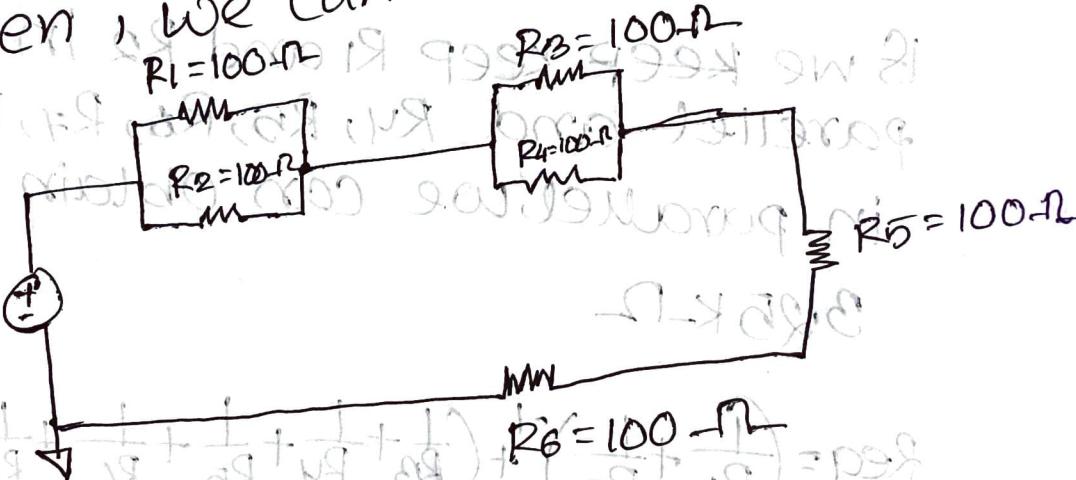2. If we keep 4 resistors in parallel,  
 then we can have 300 ohm.



$$R_{\text{req}} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} + \left( \frac{1}{R_3} + \frac{1}{R_4} \right)^{-1} + R_5 + R_6$$

$$= \left( \frac{1}{50} \right)^{-1} + \left( \frac{1}{50} \right)^{-1} + 100 + 100 \\ = 300 \Omega$$

3.

Given,

$$R_1 = 1.5 \text{ k}\Omega$$

$$R_2 = 1.5 \text{ k}\Omega$$

$$R_3 = 15 \text{ k}\Omega$$

$$R_4 = 15 \text{ k}\Omega$$

$$R_5 = 15 \text{ k}\Omega$$

$$R_6 = 15 \text{ k}\Omega$$

$$R_7 = 15 \text{ k}\Omega$$

$$R_8 = 15 \text{ k}\Omega$$

If we keep  $R_1$  and  $R_2$  in parallel and  $R_4, R_5, R_6, R_7, R_8$  in parallel, we can obtain

$$3.25 \text{ k}\Omega$$


$$\text{Req} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} + \left( \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6} + \frac{1}{R_7} + \frac{1}{R_8} \right)^{-1}$$

$$= \left( \frac{1}{1.5} + \frac{1}{1.5} \right)^{-1} + \left( \frac{1}{15} + \frac{1}{15} + \frac{1}{15} + \frac{1}{15} + \frac{1}{15} + \frac{1}{15} \right)^{-1}$$

$$= \frac{3}{4} + \frac{6}{5/2} = 13/4 \text{ k}\Omega$$

$$= 3.25 \text{ k}\Omega$$

Figure:

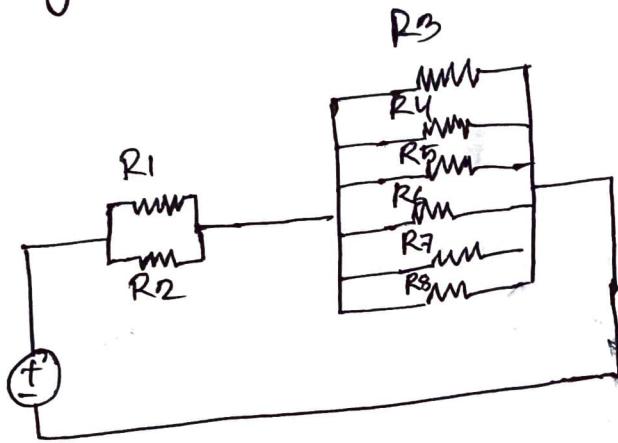

Discussion: After the completion of the experiment, we get to learn the physical application of Ohm's law and the devices to create the circuit. It shows us how to determine and measure the value of current, resistance and voltage.