

LAB 2
CSB250

Name: Fahim Irfan Ahmed

ID: 20101508

Section: 01

CSE250

Name of the Experiment: Introduction to series and parallel circuits.

Objective: The experiment is to acquaint the students with series-parallel circuits and to give them the idea about how to connect different circuits in bread board.

Apparatus:

DC power supplies


Resistors


Bread board/Trainer board

Multimeter

Circuits and Procedure:

	1 I (9mA)	5V + 1V = V (240V)	5V (240V)	1V (240V)
	Am 15.1	Am 28.0	Am 28.0	V 2.8

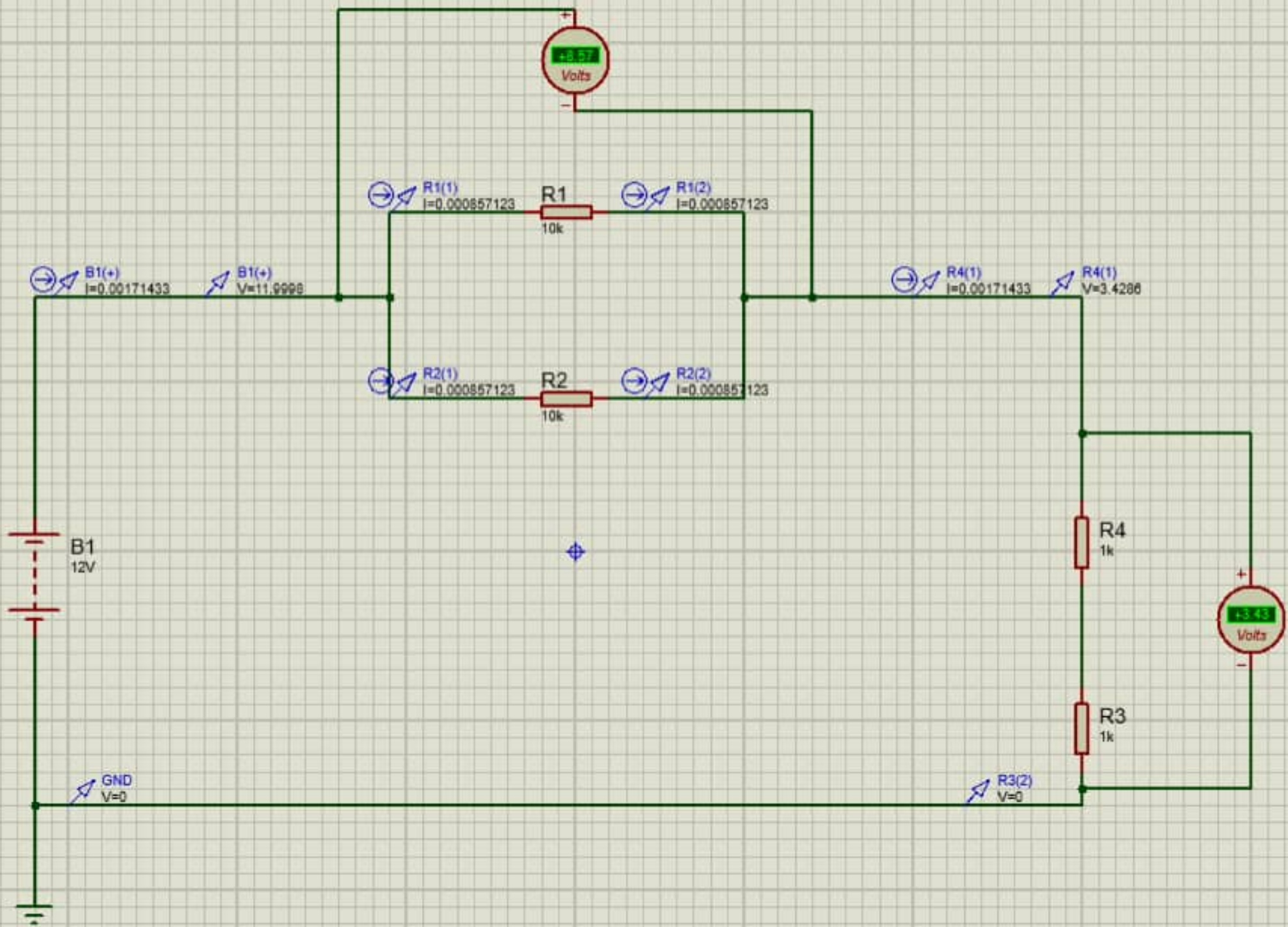

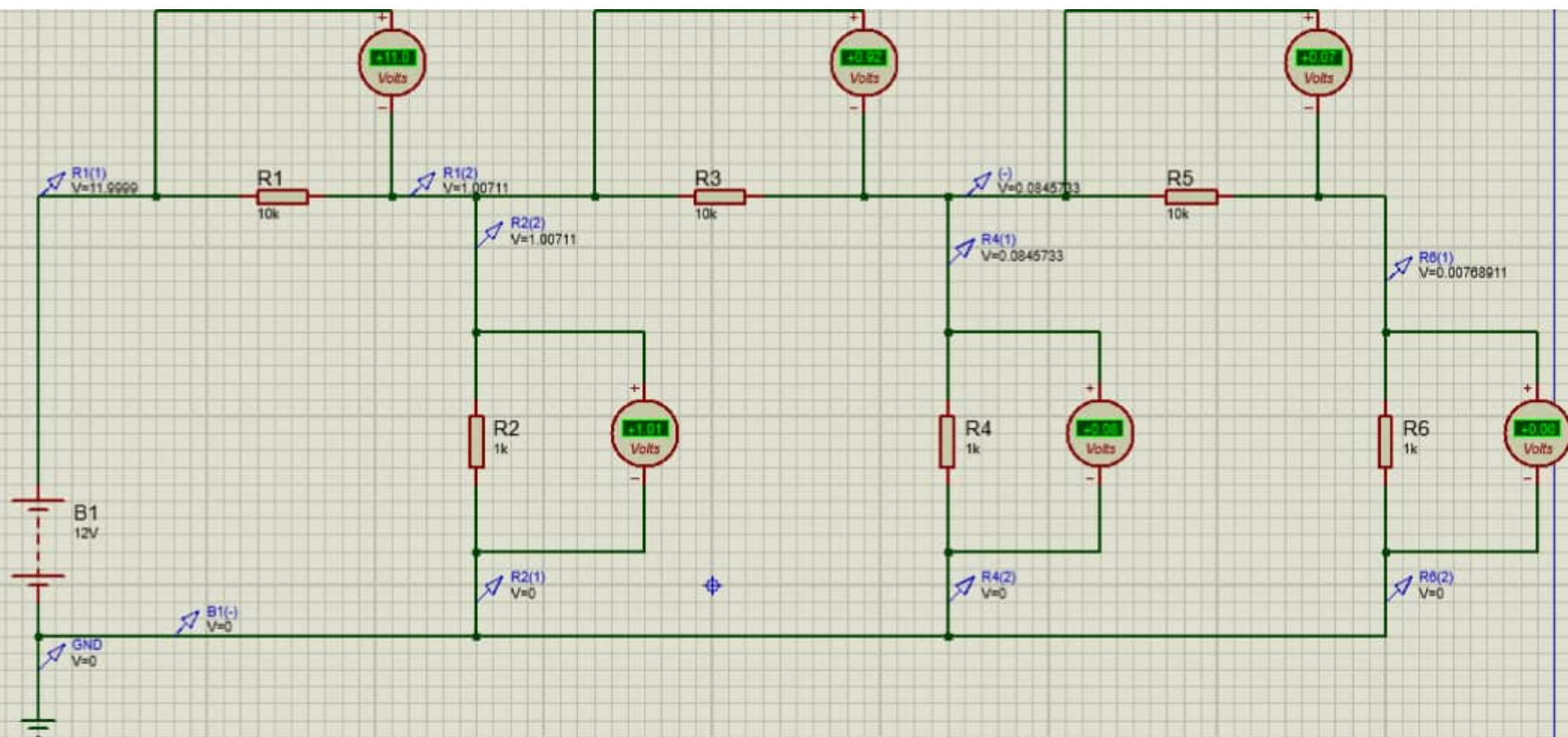

Reports:

For circuit 1:

Here,

$$V = 12V$$

$$R_1 = 10k\Omega$$

$$R_2 = 10k\Omega$$

$$R_3 = 1k\Omega$$

$$R_4 = 1k\Omega$$

$$I_1 = \frac{V_1}{R_1} = \frac{8.57}{10} \text{ mA}$$

$$= 0.857 \text{ mA}$$

$$I_2 = \frac{V_2}{R_2} = \frac{8.57}{10}$$

$$= 0.857 \text{ mA}$$

V_1 (volts)	V_2 (volts)	$V = V_1 + V_2$ (volts)	I_1 (mA)	I_2 (mA)	$I = I_1 + I_2$ (mA)
8.57V	3.43V	12V	0.857mA	0.857mA	1.714mA

For circuit 2:

$$V = 12V$$

$$R_1 = 10k\Omega$$

$$R_2 = 1k\Omega$$

$$R_3 = 10k\Omega$$

$$R_4 = 1k\Omega$$

$$R_5 = 10k\Omega$$

$$R_6 = 1k\Omega$$

$$I_1 = \frac{V_1}{R_1} = \frac{11}{10} = 1.1mA$$

$$I_2 = \frac{V_2}{R_2} = \frac{1.01}{1} = 1.01mA$$

$$I_3 = \frac{V_3}{R_3} = \frac{0.92}{10} = 0.092mA$$

$$I_4 = \frac{V_4}{R_4} = \frac{0.08}{1} = 0.08mA$$

$$I_5 = \frac{V_5}{R_5} = \frac{0.07}{10} = 0.007mA$$

$$I_6 = \frac{V_6}{R_6} = \frac{0.007}{1} = 0.007mA$$

V_1	V_2	V_3	V_4	V_5	V_6	$I_1(A)$	$I_2(A)$	$I_3(A)$	$I_4(A)$	$I_5(A)$	$I_6(A)$
11V	1.01V	0.92V	0.08V	0.07V	0.007V	1.1mA	1.01mA	0.092mA	0.08mA	0.007mA	0.007mA

$$V_{Total} = 13.087V$$

$$V_{given} = 12V$$

The calculated value from the circuit using multimeter is not same as the given one. So, this is one of the discrepancies I came up to.

$$A_m = \frac{P}{T}$$

Ans. to the question no. 1

2 figures not

In circuit 1,
Here, $V = 12V$

$$R_1 = 10k\Omega$$

$$R_2 = 10k\Omega$$

$$R_3 = 1k\Omega$$

$$R_4 = 1k\Omega$$

For $R_1, R_2 \Rightarrow$

$$R_p = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$= \left(\frac{1}{10} + \frac{1}{10} \right)^{-1} k\Omega$$

$$= \left(\frac{1}{5} \right)^{-1} k\Omega$$

$$= 5k\Omega$$

$$R_{eq} = R_p + R_3 + R_4$$

$$= 5 + 1 + 1$$

$$= 7k\Omega$$

Now

$$I = \frac{V}{R}$$

$$= \frac{12}{7} mA$$

$$= 1.714 mA$$

$$I_{mL1} = \frac{11}{0.1} = \frac{1V}{1.9} = 1A$$

$$I_{mL2} = \frac{10.1}{1} = \frac{1V}{2.9} = 1A$$

$$I_{mL3} = \frac{10.0}{0.1} = \frac{1V}{2.9} = 1A$$

$$I_{mL4} = \frac{10.0}{1} = \frac{1V}{1.9} = 1A$$

$$I_{mL5} = \frac{10.0}{0.1} = \frac{1V}{2.9} = 1A$$

$$I_{mL6} = \frac{10.0}{1} = \frac{1V}{2.9} = 1A$$

$$V_{S1} = V$$

$$R_{X1} = 1.9$$

$$R_{X2} = 2.9$$

$$R_{X3} = 2.9$$

$$R_{X4} = 1.9$$

$$R_{X5} = 2.9$$

$$R_{X6} = 2.9$$

$$V_{S1} = 12V$$

$$V_{S2} = 12V$$

2 figures not

for circuit-2,

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 1 \text{ k}\Omega$$

$$R_3 = 10 \text{ k}\Omega$$

$$R_4 = 1 \text{ k}\Omega$$

$$R_5 = 10 \text{ k}\Omega$$

$$R_6 = 1 \text{ k}\Omega$$

$$V = 12 \text{ V}$$

$$R_{eqv} = (R_1 + R_{pd}) \text{ k}\Omega$$

$$= \left(10 + \frac{131}{143} \right) \text{ k}\Omega$$

$$= \left(\frac{1430 + 131}{143} \right) \text{ k}\Omega$$

$$= \frac{1561}{143} \text{ k}\Omega$$

$$= 10.91 \text{ k}\Omega$$


Here,

$$R_{pa} = (R_3 + R_6)$$

$$R_{pb} = \left(\frac{1}{R_{pa}} + \frac{1}{R_4} \right)^{-1}$$

$$= \left(\frac{1}{11} + \frac{1}{1} \right)^{-1}$$
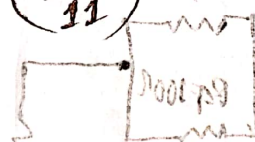
$$= \left(\frac{12}{11} \right)^{-1} = \frac{11}{12} \text{ k}\Omega$$



$$R_{pc} = (R_3 + R_6)$$

$$= \left(10 + \frac{11}{12} \right) \text{ k}\Omega$$

$$= \left(\frac{120 + 11}{12} \right) \text{ k}\Omega$$

$$= \frac{131}{12} \text{ k}\Omega$$

$$R_{pd} = \left(\frac{1}{R_{pc}} + \frac{1}{R_2} \right)^{-1}$$

$$= \left(\frac{1}{\frac{131}{12}} + \frac{1}{1} \right)^{-1}$$

$$= \left(\frac{12}{131} + 1 \right)^{-1}$$

$$= \left(\frac{12 + 131}{131} \right)^{-1}$$

$$= \left(\frac{143}{131} \right)^{-1} = \frac{131}{143}$$

ground

$$\frac{1}{10} + \frac{1}{10} + \frac{1}{1} - \left(\frac{1}{10} + \frac{1}{10} \right) + \frac{1}{1} - \left(\frac{1}{10} + \frac{1}{10} \right) = \frac{1}{10}$$

$$\frac{1}{100} + \frac{1}{100} + \frac{1}{100} - \left(\frac{1}{100} + \frac{1}{100} \right) + \frac{1}{100} - \left(\frac{1}{100} + \frac{1}{100} \right) = \frac{1}{100}$$

$$\frac{1}{100} + \frac{1}{100} + \frac{1}{100} + \frac{1}{100} = \frac{4}{100}$$


$$I = \frac{V}{R_{eq}} = \frac{12}{10.91} \text{ mA}$$

$$= 1.099 \text{ mA}$$

So, we can see that the calculated value of the current is the same as the multimeter gave in the circuit.

Ans. to the question no. 2

We can have 300 ohm , if we connect $(R_1 || R_2)$ ^{series with} $(R_3 || R_4)$ series with R_5 and R_6 .

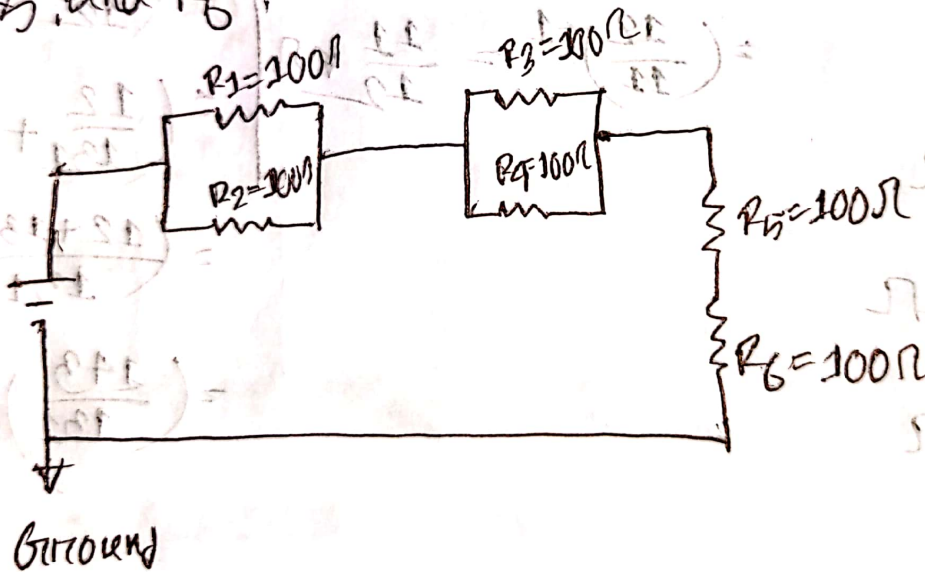

$$\begin{aligned} R_{eq} &= \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} + \left(\frac{1}{R_3} + \frac{1}{R_4} \right)^{-1} + R_5 + R_6 \\ &= \left(\frac{1}{100} + \frac{1}{100} \right)^{-1} + \left(\frac{1}{100} + \frac{1}{100} \right)^{-1} + 100 + 100 \\ &= 50 + 50 + 100 + 100 \\ &= 300 \Omega \text{ (Ans)} \end{aligned}$$

Ans. to the question no. 3

Here, ~~R_1~~ $R_3 = R_4 = R_5 = R_6 = R_7 = R_8 = 15 \text{ k}\Omega$


$$R_1 = R_2 = 1.5 \text{ k}\Omega$$

Now, $(R_1 \parallel R_2) \text{ in series } (R_3 \parallel R_4 \parallel R_5 \parallel R_6 \parallel R_7 \parallel R_8)$

$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} + \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6} + \frac{1}{R_7} + \frac{1}{R_8} \right)^{-1}$$

$$= \left(\frac{1}{1.5} + \frac{1}{1.5} \right)^{-1} + \left(\frac{1}{15} + \frac{1}{15} + \frac{1}{15} + \frac{1}{15} + \frac{1}{15} + \frac{1}{15} \right)^{-1}$$
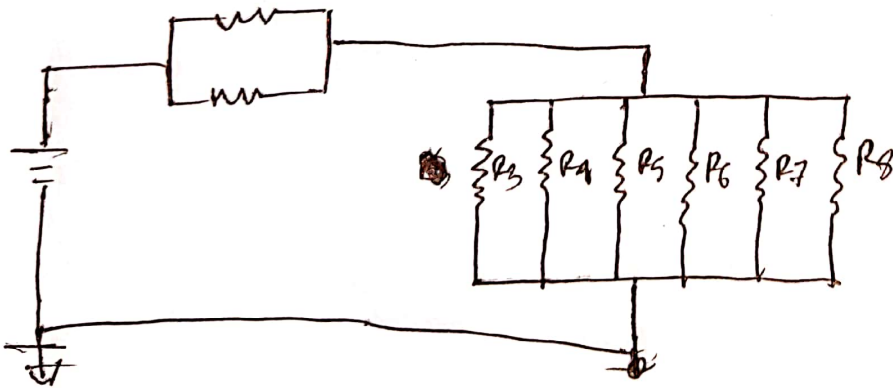
$$= \frac{3}{4} + \frac{5}{2} = \frac{13}{4} = 3.25 \text{ k}\Omega$$



Discussion: Applying the circuits like this, we achieve the value of $3.25 \text{ k}\Omega$.