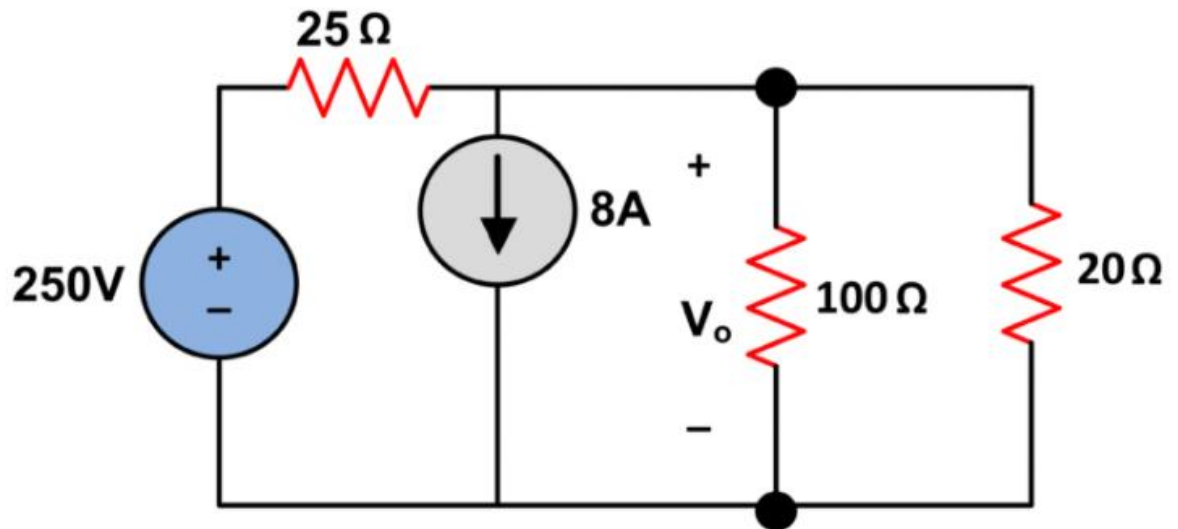


Source Transformation

1.


Find V_o using source Transformation



(soln: $V_o = 20V$)

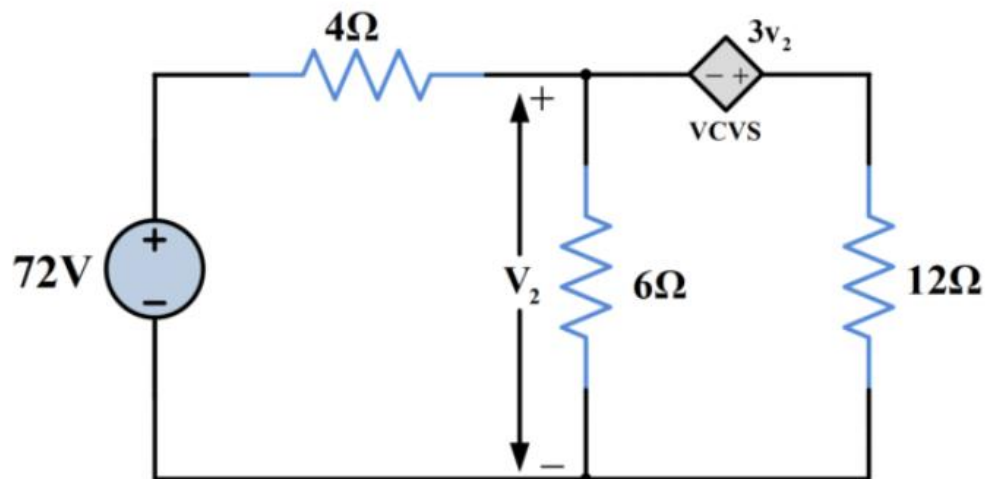
2.

Let's find v_2 in the following circuit using source transformation.



(soln: $V_2 = 24V$)

3. Find the value of V_m :

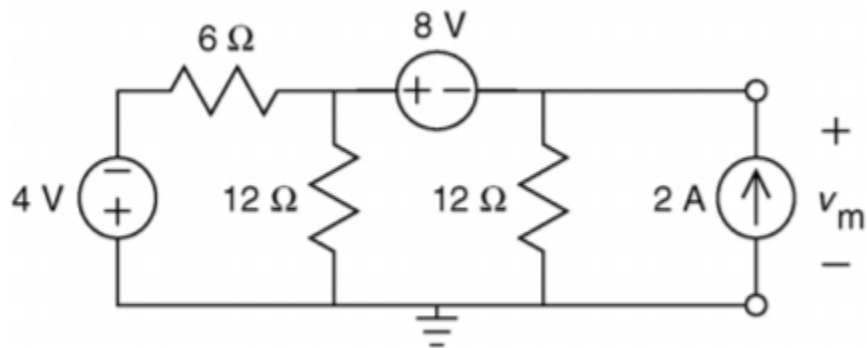

(soln: $V_m = -2V$)

4. Find the value of i_s :

