

Here, there are 4 nodes,

Node 1

$$V_1 \left(\frac{1}{80} \right) - \frac{V_2}{80} = 0$$

Node 2

$$V_2 \left(\frac{1}{80} + \frac{1}{-j40} + \frac{1}{j60} \right) - \frac{V_1}{80} - \frac{V_3}{j60} = 0$$

Node 3

$$V_3 \left(\frac{1}{j60} + \frac{1}{-j40} + \frac{1}{20} \right) - \frac{V_2}{j60} - \frac{V_4}{20} = 0$$

Node 4

$$V_4 \left(\frac{1}{20} \right) - \frac{V_3}{20} = 0$$

Here,


$$V_1 - 0 = 100 \angle 120^\circ$$

or $V_1 = 100 \angle 120^\circ$

Again

$$V_A - 0 = 60 \angle -30^\circ$$

$$\therefore V_A = 60 \angle -30^\circ$$

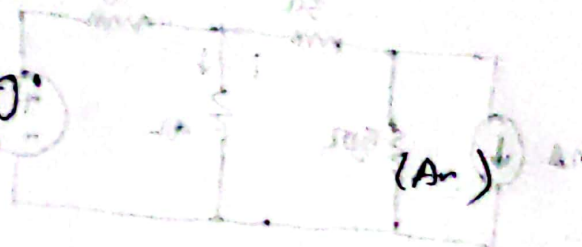


superposition theorem



$$\frac{0.5 \times 20}{10 + 20}$$

Am no. 2

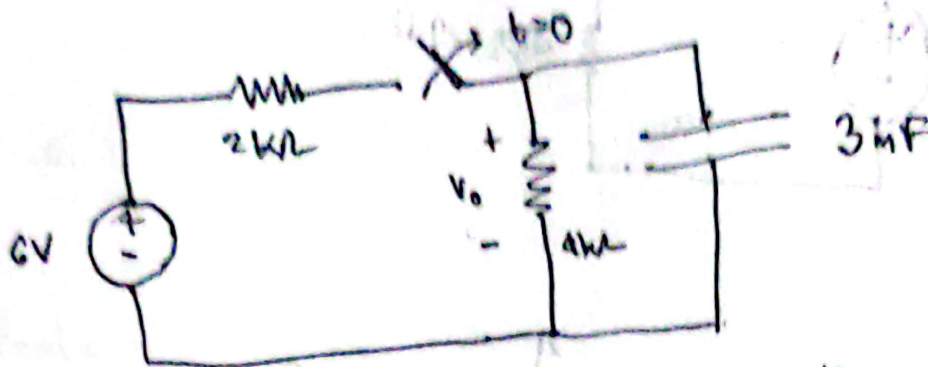

Here,


for $t < 0$,

Here,

$$\tau = R \times C$$

$$= 4 \times 10^3 \times 3 \times 10^{-3}$$

$$= 125$$

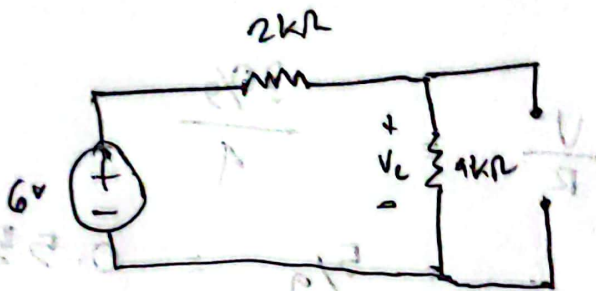


$$V_c = \frac{4}{2+4} \times 6$$

$$= \frac{4}{6} \times 6$$

$$= 4V$$

for,

$t > 0$

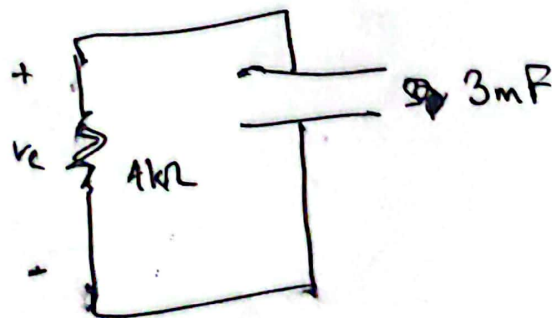


$$\therefore V_c = 0V$$





$$\therefore \text{At } t > 0, V_c = 0V.$$

(wh.)

Am no. 3

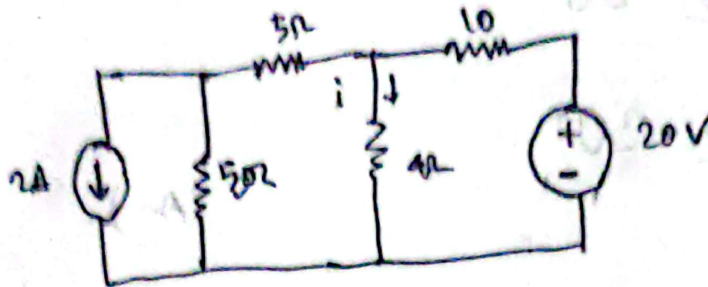


Performing Source transformation

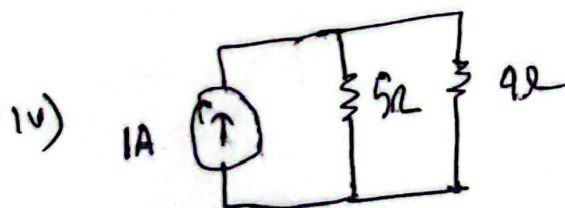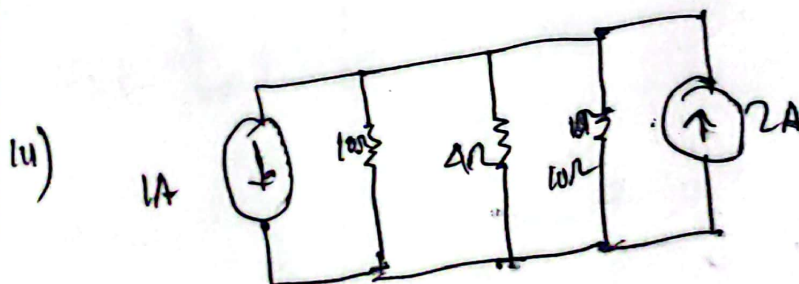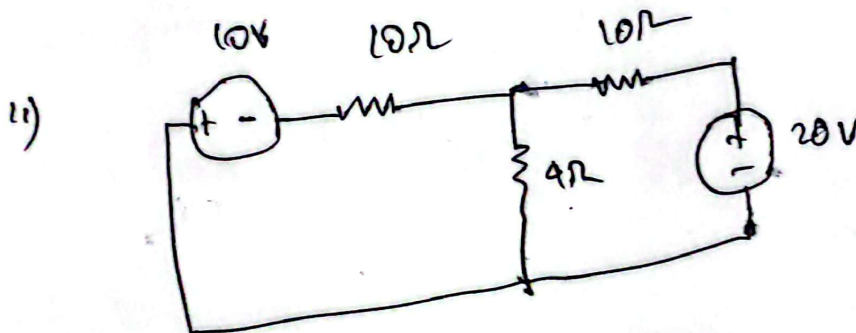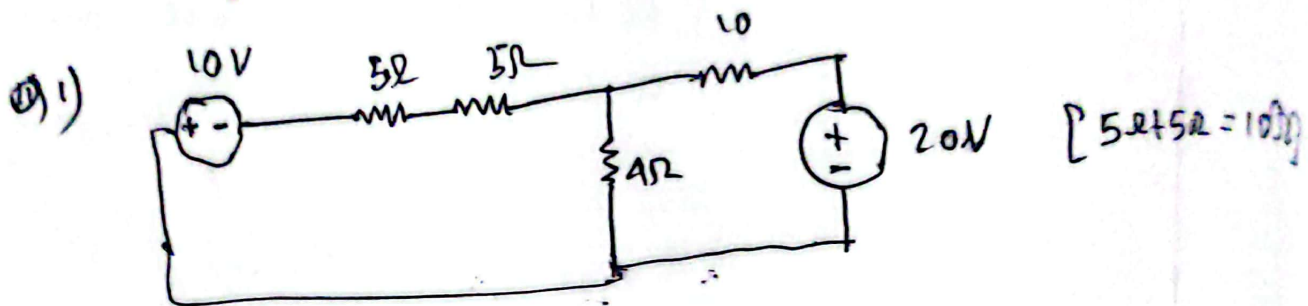

$[2A \text{ as passive}]$
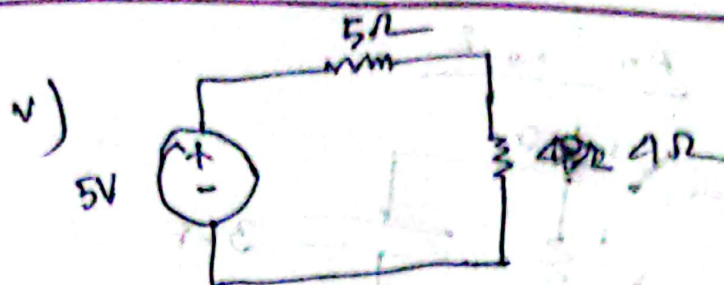
$$[\frac{I}{A_p} = \frac{10 \times 10}{10 + 10}]$$



Now

$$V_{at\ 4\Omega} = \frac{4}{5+4} \times 5$$

$$= \frac{20}{9}$$

Now $\frac{P}{A \cdot s} = V$

$$i_{at\ 4\Omega} =$$

$$\frac{V}{R} = \frac{\frac{20}{9}}{4} = 0.556\text{ A}$$


$$= 556\text{ mA}$$

$$V_P =$$



$$V_D = 5V, 0 < t < 1A$$

$$V_D = 5V$$

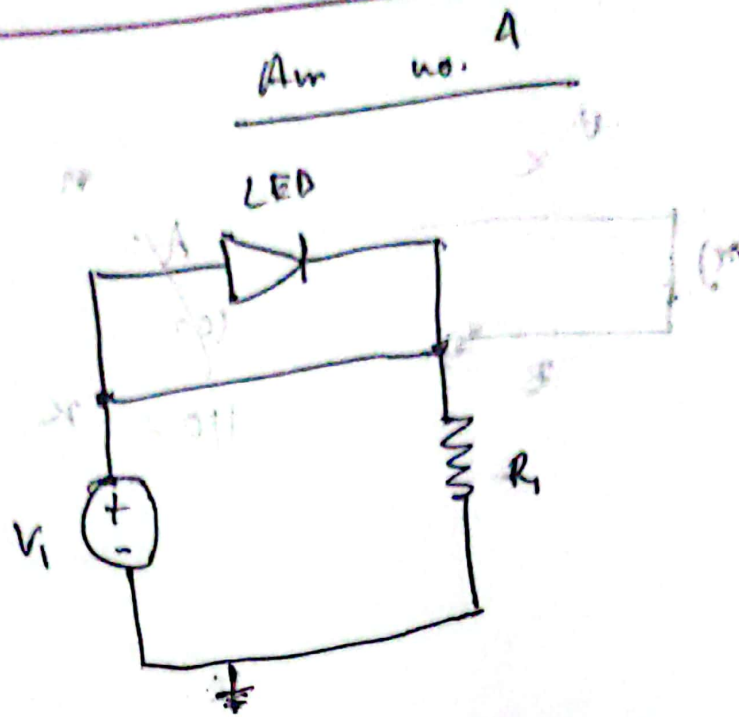

\therefore Since, the current has found an alternative way to go without any resistance, and LED is a passive element like resistors. No current will flow through it.


$$\therefore P = V \cdot I$$

$$= V \cdot 0$$

$$[I = 0]$$

$$= 0 \text{ W}$$

(Ans)

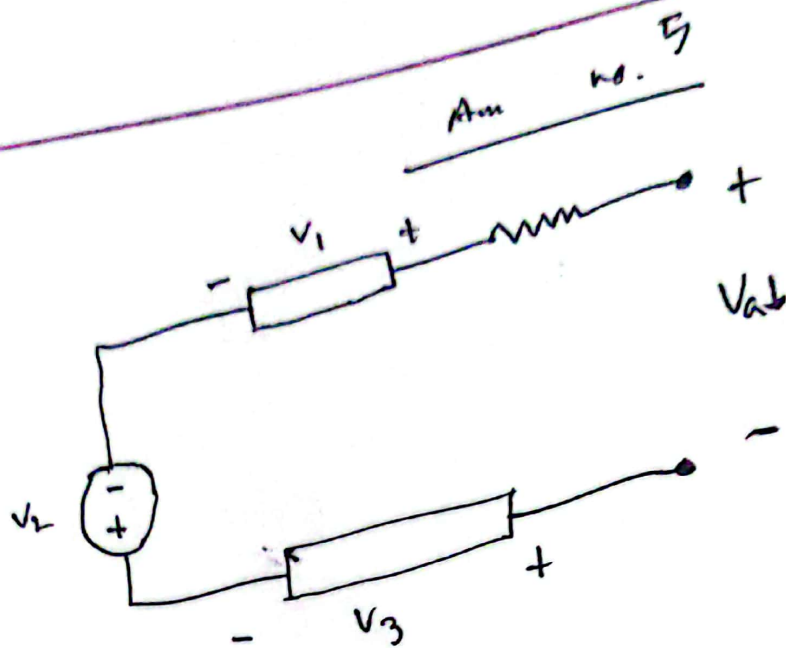

Here,
 $V_1 = 100$, $V_2 = 60V$, $V_3 = 50V$, $V_{ab} = ?$
 in an open circuit

Here,
 $V_{ab} = V_1 + V_2 + V_3 = 0$
 or $V_{ab} = V_1 - V_2 - V_3$

$$= 100 - 60 - 50$$

$$= -10V$$

(Ans)

[following passive convention]