

Q1: 5 marks

Slot 1

Using superposition theorem, calculate the value of V in the figure 1. You must use superposition. Otherwise, no mark will be given.

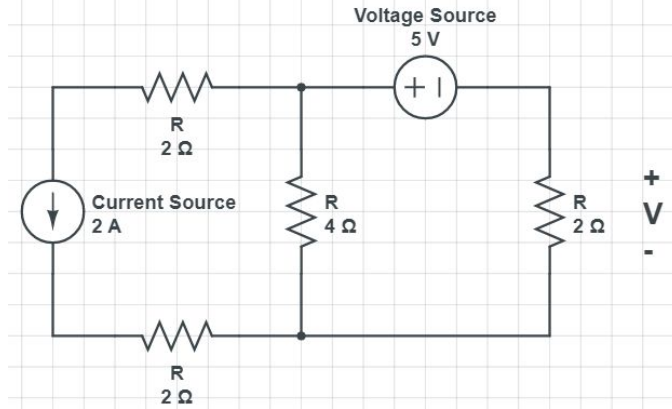


Figure 1

Q2: 10 marks

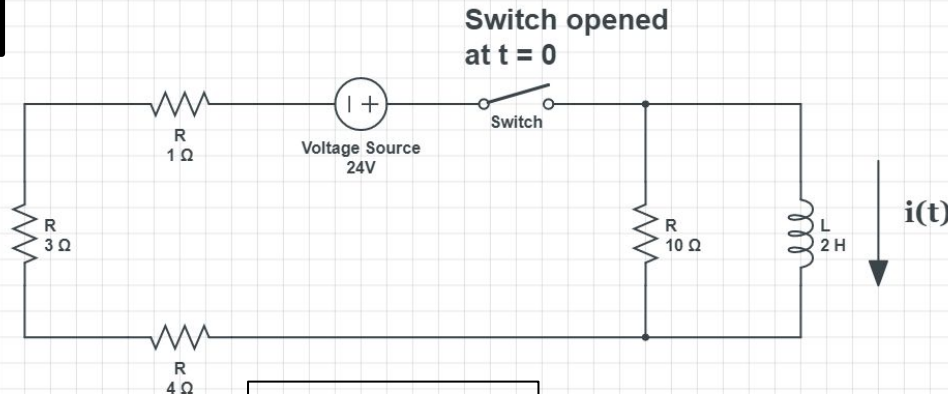


Figure 2

- (i) What do you know about Time Constant? How do you measure it?
- (ii) From figure 2 calculate $i(t)$ for $t > 0$. What will be the value of $i(t)$ at $t = 10\text{ ms}$?

Q1

Using superposition theorem, calculate the value of i in the Figure 1. You must use superposition. Otherwise, no mark will be given.


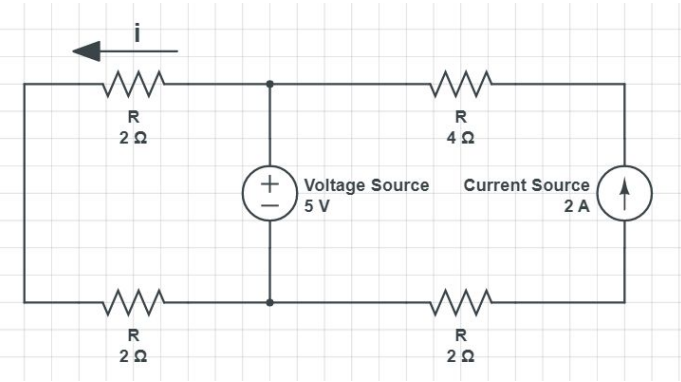


Figure 1

Q2

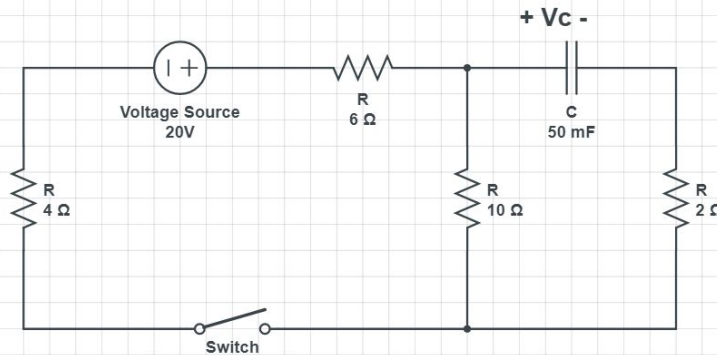

Switch opened after $t = 0$


Figure 2

- (i) Why is a source free RC circuit called a “First Order” circuit?
- (ii) From Figure 2 calculate $v(t)$ for $t > 0$. What will be the value of $v(t)$ at $t = 25\text{ms}$?

Slot 1


①

5V source short:

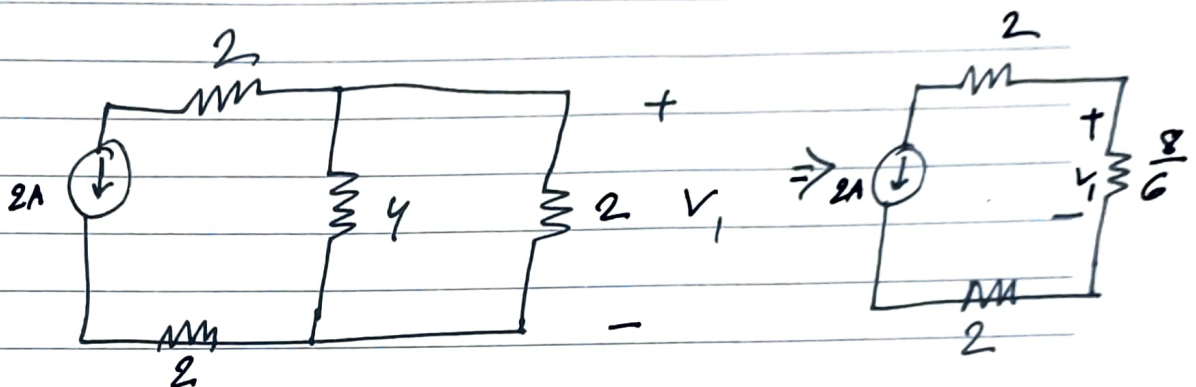

$$\therefore V_1 = IR = -2 \times \frac{8}{6} = -\frac{8}{3} = -2.667V$$

2A source open:

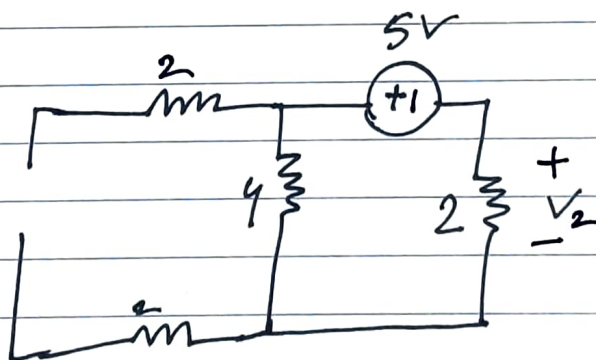


$$\begin{aligned} V_2 &= \frac{2}{6} (-5) \\ &= -\frac{10}{6} \\ &= -1.667V \end{aligned}$$


$$\therefore V = V_1 + V_2 = -4.333V$$

② i) $\tau = RC$ or $\tau = \frac{L}{R}$. So two ways to measure for a first order ckt.

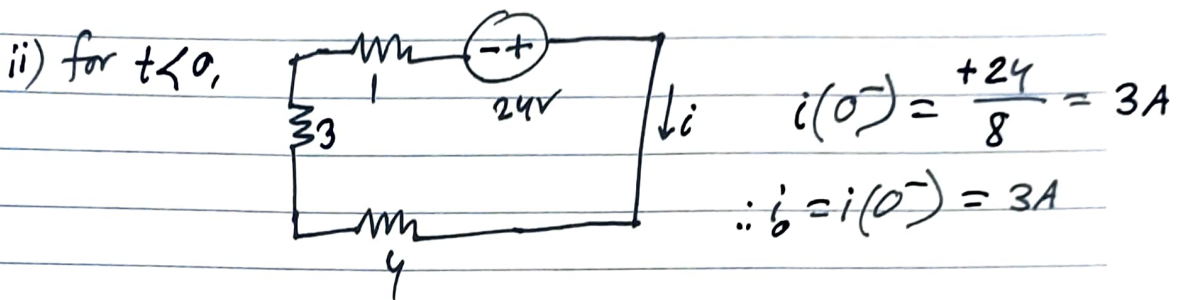τ is the time required for a i/v to reach 63.2% of its starting strength.



for $t > 0$

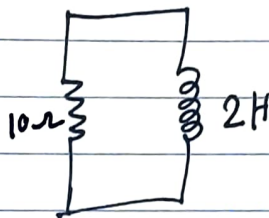

$$R = 10$$

$$\therefore \tau = \frac{L}{R} = \frac{2}{10}$$

$$\therefore i(t) = i_0 e^{-t/\tau} = 3 e^{-\frac{10}{2}t} = 3 e^{-5t} \text{ A}$$

$$\therefore i(t) \Big|_{t=10\text{ms}} = 3 e^{-0.05} = 2.853 \text{ A.}$$


Slot 2

① 5V short:

the branch will not have any current flow.

$$\therefore i_1 = 0$$

2A open:

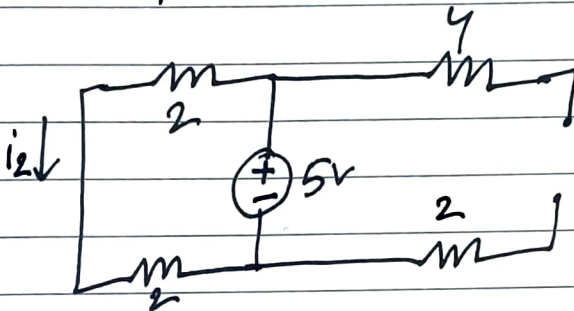


$$\therefore i_2 = \frac{5}{4} = 1.25$$

$$\therefore i = i_1 + i_2 = 1.25 \text{ A.}$$

② i) because analyzing the circuit of a RC or RL ckt, we can come up with a first order differential equation.


11) $t < 0$,

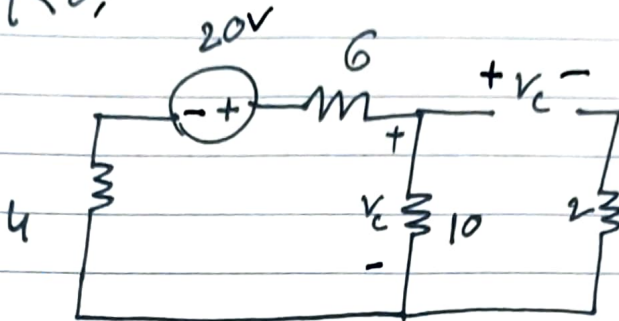

$$v_c = \frac{10}{20} \times 20 = 10V$$

$$\therefore v_c(0) = 10V$$

$t > 0$,

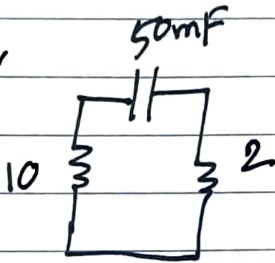

$$R = 10 + 2 = 12\Omega$$

$$C = 50mF$$

$$\therefore \tau = RC = 600m = 0.6 = \frac{6}{10} s$$

$$\therefore v(t) = 10e^{-\frac{10}{6}t} = 10e^{-1.6667t} V$$

$$v(t) \Big|_{t=25ms} = 10e^{-1.6667 \times 0.025} = 9.59189V$$